

- SPECIFICATION OF PROGRAMMABLE COMBINATIONAL AND SEQUENTIAL MODULES
 1. PSA
 2. ROM
 3. FPGA
- THE WAY THE MODULES ARE PROGRAMMED
- NETWORKS OF PROGRAMMABLE MODULES
- EXAMPLES OF USES

PROGRAMMABLE SEQUENTIAL ARRAYS (PSA)

2

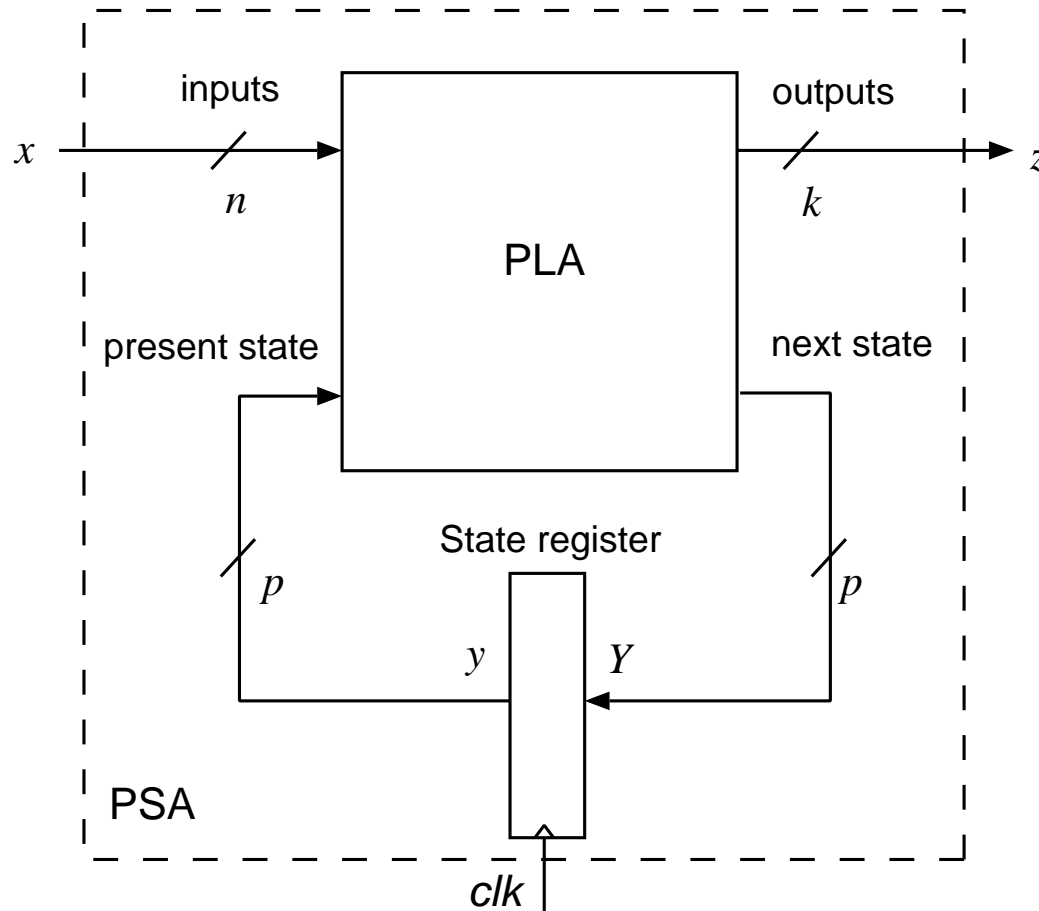


Figure 12.1: PROGRAMMABLE SEQUENTIAL ARRAY (PSA).

Example 12.1: IMPLEMENTATION OF SEQUENTIAL SYSTEMS³ USING PSAs

- SEQUENCE GENERATOR

INPUTS: $x \in \{0, 1\}$

OUTPUTS: $z \in \{0, 1, 3, 6, 7, 10, 14\}$

FUNCTION: The transition and output functions

$$x = 0 : z = 0 \rightarrow 10 \rightarrow 14 \rightarrow 7 \rightarrow 0 \dots$$
$$x = 1 : z = 1 \rightarrow 10 \rightarrow 3 \rightarrow 6 \rightarrow 1 \dots$$
$$x = 0 : z = 0000 \rightarrow 1010 \rightarrow 1110 \rightarrow 0111 \rightarrow 0000 \dots$$
$$x = 1 : z = 0001 \rightarrow 1010 \rightarrow 0011 \rightarrow 0110 \rightarrow 0001 \dots$$

 
 


Figure 12.2: TIMING SEQUENCES IN Example 12.1.

Example 12.1 (cont.)

y	$k = 0$	$k = 1$	
0	10	—	k
1	—	10	k
3	—	6	x
6	0	1	k
7	0	1	k
10	14	3	k
14	7	—	x
	Y		K

$y \in \{2, 4, 5, 8, 9, 11, 12, 13, 15\}$ – don't care states


$$K = xy_3y_2 + xy'_3y'_2y_1 + ky'_1 + ky'_3y_2 + ky_3y'_2$$

$$Y_3 = y'_1 + y'_2k'$$

$$Y_2 = y'_3y'_2y_1 + y_3k'$$

$$Y_1 = y'_2 + y_3$$

$$Y_0 = y_3k + y_2k + y_3y_2$$

 

READ-ONLY MEMORIES (ROM)

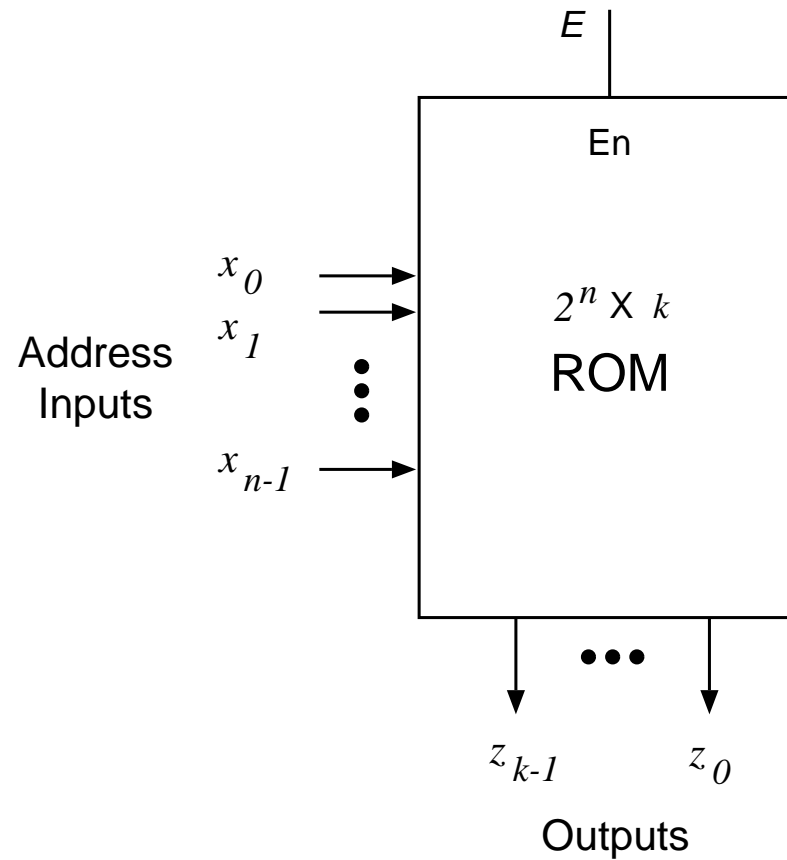


Figure 12.4: READ-ONLY MEMORY (ROM)

EXAMPLE 12.2

Address	Contents
\mathcal{x}	\mathcal{z}
000	1011
001	1101
010	0111
011	1000
100	0000
101	1111
110	1111
111	1011

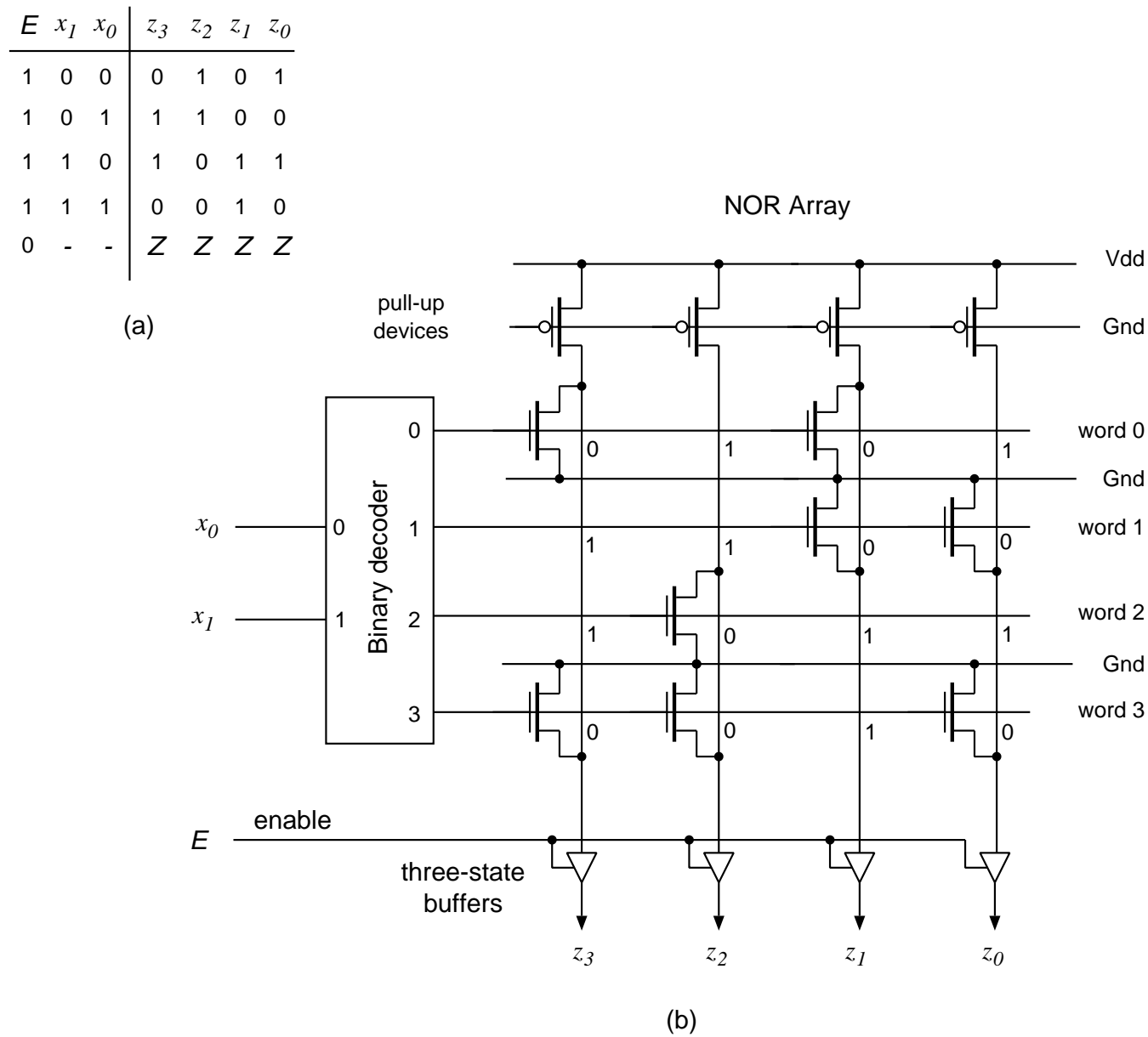


Figure 12.5: MOS IMPLEMENTATION OF A 4×4 READ-ONLY MEMORY: a) THE FUNCTION; b) THE CIRCUIT.

IMPLEMENTATION OF SWITCHING FUNCTIONS USING ROMS

11

 


Figure 12.6: ROM-BASED IMPLEMENTATION OF A 4-BIT ADDER.

IMPLEMENTATION OF SEQUENTIAL SYSTEMS USING ROMS¹²


INPUTS: $\underline{x} = (x_1, x_0), \quad x_i \in \{0, 1\}$

OUTPUTS: $z \in \{0, 1, \}$

STATE: $\underline{y} = (y_1, y_0), \quad y_i \in \{0, 1, \}$

FUNCTION: The transition and output function

PS y_1y_0	x_1x_0		
	01	10	11
00	01,0	10,1	10,0
01	00,0	11,1	11,0
10	11,0	10,0	00,1
11	10,0	00,0	11,1
	Y_1Y_0, z $NS, \text{ Output}$		

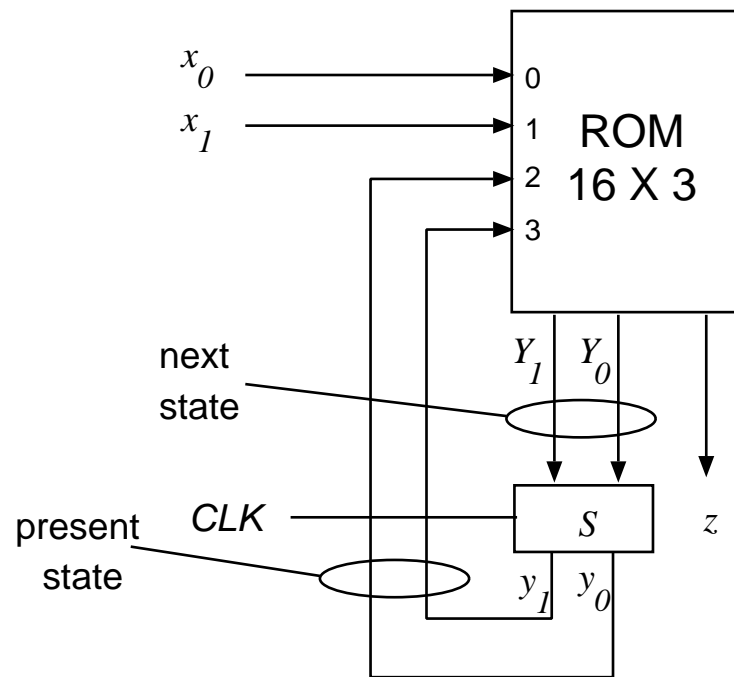

(a)

ROM address	ROM contents		
$y_1 y_0 x_1 x_0$	Y_1	Y_0	z
0000	-	-	-
0001	0	1	0
0010	1	0	1
0011	1	0	0
0100	-	-	-
0101	0	0	0
0110	1	1	1
0111	1	1	0
1000	-	-	-
1001	1	1	0
1010	1	0	0
1011	0	0	1
1100	-	-	-
1101	1	0	0
1110	0	0	0
1111	1	1	1

next state output

(b)

Figure 12.7: ROM-based implementation of a sequential system: a) network; b) ROM contents.

TYPES OF ROM MODULES

- MASK-PROGRAMMED ROM
- FIELD-PROGRAMMABLE ROM (PROM)
- ERASABLE ROM (EPROM)
- ELECTRICALLY ERASABLE ROM or EEPROM

$$f_1(x_4, x_3, x_2, x_1, x_0) = \text{one-set}(0, 3, 11, 12, 16, 23, 27)$$
$$f_0(x_4, x_3, x_2, x_1, x_0) = \text{one-set}(5, 7, 19, 21, 31)$$

ROM MODULE: 8×2

$$\underline{x} = (\underline{x}^{(0)}, \underline{x}^{(1)})$$
$$\underline{x}^{(0)} = (x_4, x_3)$$
$$\underline{x}^{(1)} = (x_2, x_1, x_0)$$

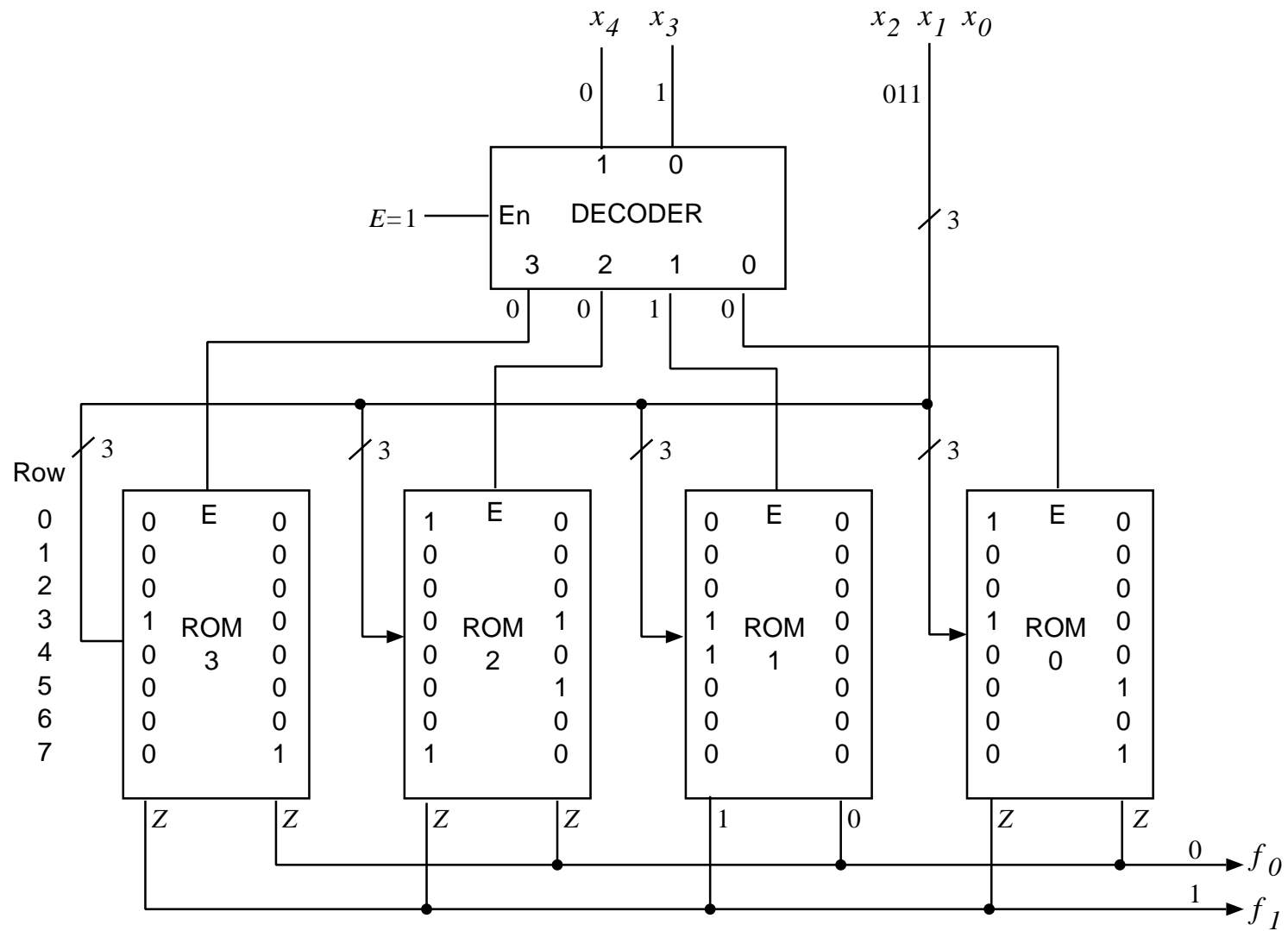


Figure 12.8: ROM-BASED NETWORK FOR THE IMPLEMENTATION OF TWO FUNCTIONS.

 


Figure 12.9: IMPLEMENTATIONS OF FUNCTIONS WITH n VARIABLES: a) ROMS AND DECODER; b) ROMS AND MULTIPLEXER

LARGE NUMBER OF SFs

 


Figure 12.10: ROM-BASED IMPLEMENTATION OF LARGE NUMBER OF SWITCHING FUNCTIONS.

FIELD PROGRAMMABLE GATE ARRAYS (FPGA)

 


Figure 12.11: ORGANIZATION OF AN FPGA CHIP.

- ON-CHIP STATIC RAM LOADED WITH CONFIGURATION BIT PATTERNS (SRAM-FPGA). (volatile)
- ANTIFUSE-PROGRAMMED DEVICES PROGRAMMED ELECTRICALLY TO PROVIDE CONNECTIONS THAT DEFINE CHIP CONFIGURATION
- ARRAY-STYLE EPROM and EEPROM PROGRAMMED DEVICES
USING SEVERAL PLAs AND A SHARED INTERCONNECT MECHANISM

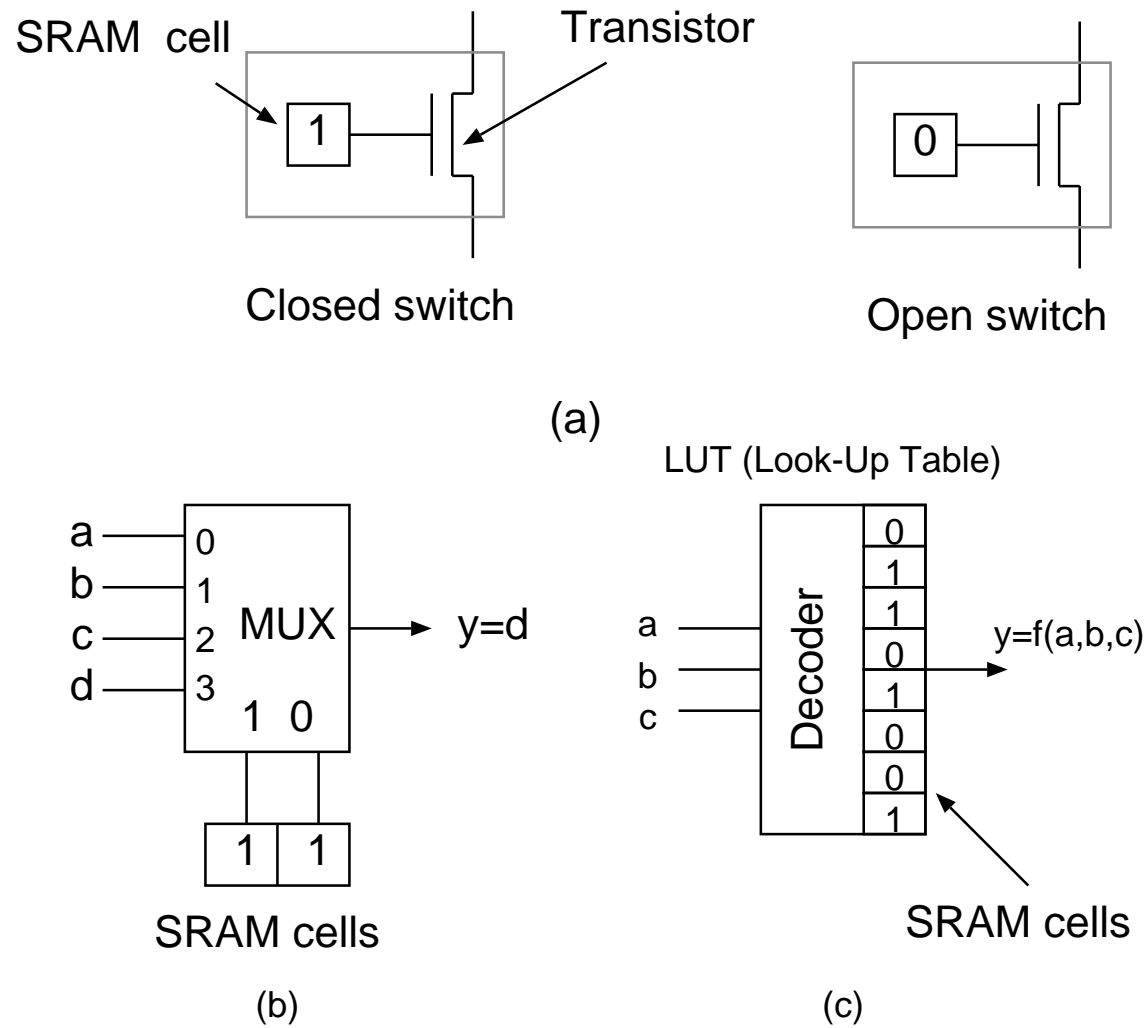


Figure 12.12: SRAM FPGA PROGRAMMABLE COMPONENTS: (a) Switch. (b) 4-input multiplexer. (c) Look-up table (LUT).

Example: XILINX XC2000

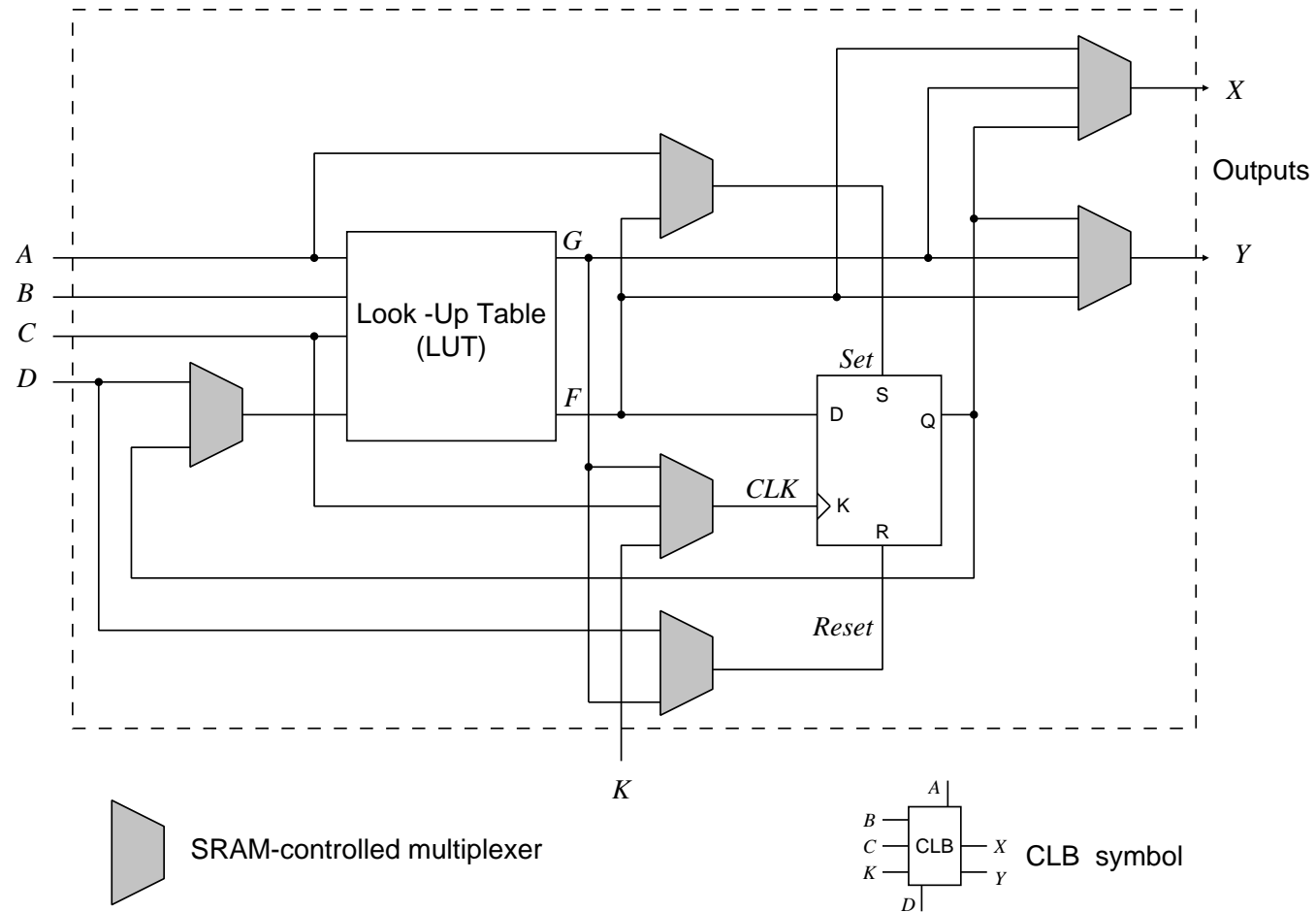


Figure 12.13: A CONFIGURABLE LOGIC BLOCK (CLB) (Courtesy of Xilinx, Inc.)

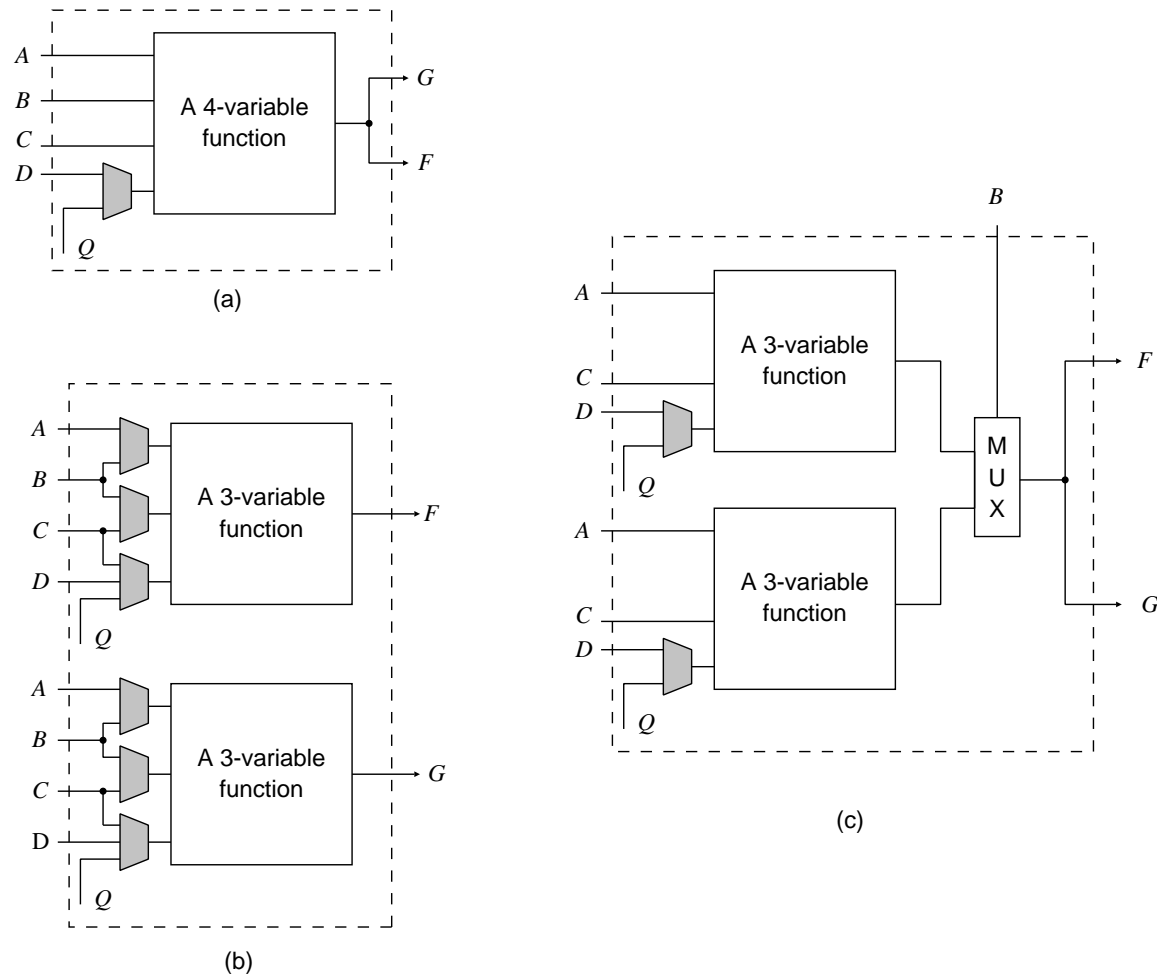


Figure 12.14: SRAM-FPGA options in generating functions: (a) One 4-variable function. (b) Two 3-variable functions. (c) Selection between two functions of 3 variables. (Courtesy of Xilinx, Inc.)

1. DIRECT INTERCONNECTIONS BETWEEN HORIZONTALLY AND VERTICALLY ADJACENT CLBS – PROVIDE FAST SIGNAL PATHS BETWEEN ADJACENT MODULES
2. GENERAL-PURPOSE INTERCONNECT CONSISTS OF VERTICAL AND HORIZONTAL WIRING SEGMENTS BETWEEN SWITCH MATRICES
3. LONG VERTICAL AND HORIZONTAL LINES SPAN THE WHOLE CLB ARRAY

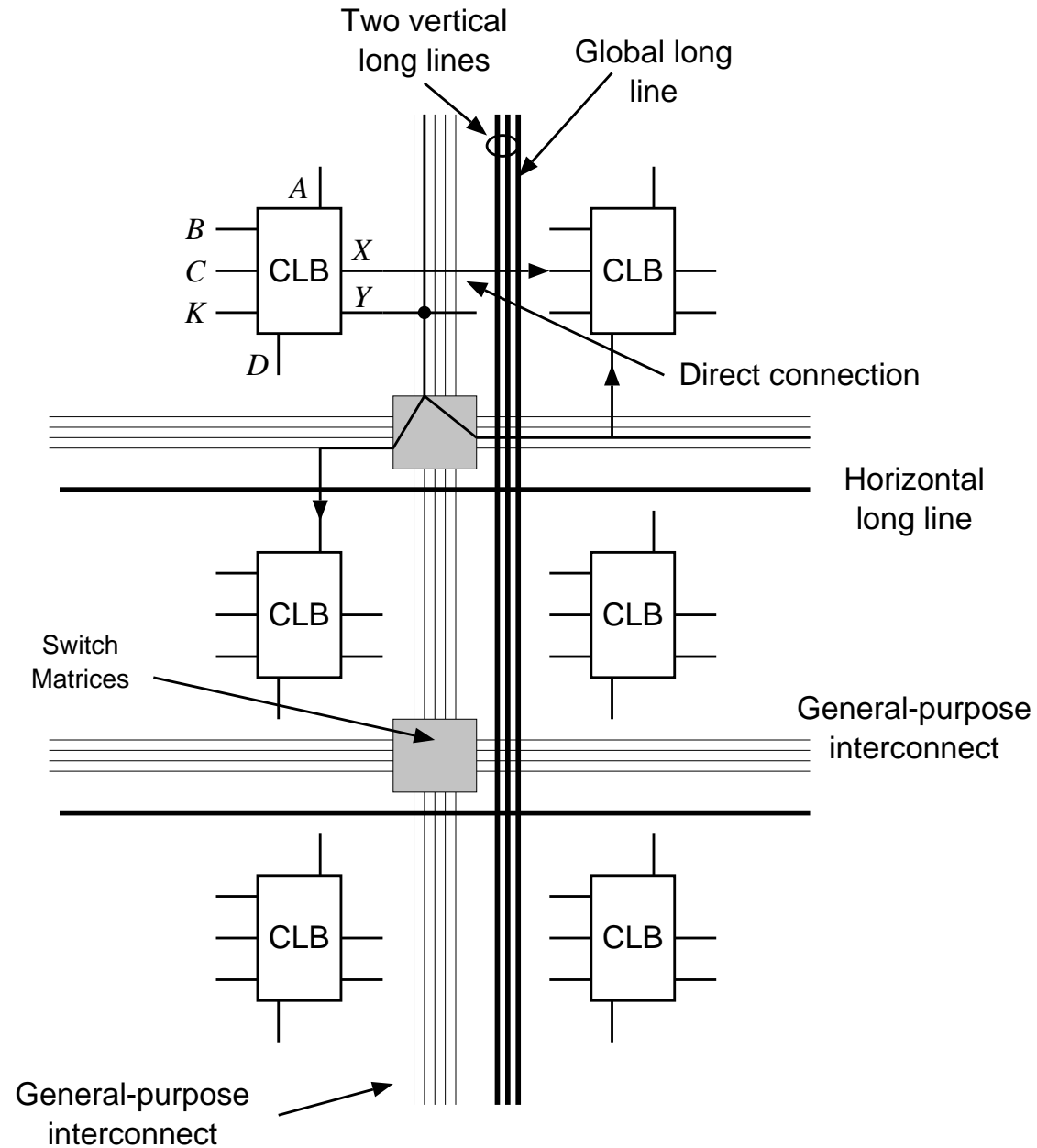


Figure 12.15: PROGRAMMABLE INTERCONNECT. (Courtesy of Xilinx, Inc.)

Example 12.5: BCD ADDER MODULE

- IMPLEMENT A ONE-DIGIT BCD ADDER USING A SRAM-FPGAMODULE OF XC2000 TYPE

INPUTS: $\underline{x} = (x_3, x_2, x_1, x_0), \quad x_j \in \{0, 1\}, \quad x \in \{0, \dots, 9\}$
 $\underline{y} = (y_3, y_2, y_1, y_0), \quad y_j \in \{0, 1\}, \quad y \in \{0, \dots, 9\}$
 $c_{in} \in \{0, 1\}$

OUTPUTS: $\underline{s} = (s_3, s_2, s_1, s_0), \quad s_j \in \{0, 1\}, \quad s \in \{0, \dots, 9\}$
 $c_{out} \in \{0, 1\}$

FUNCTION: $x + y + c_{in} = 10c_{out} + s$

- COMPUTE $16u + v = x + y + c_{in} \in \{0, \dots, 19\}$ using a 4-bit binary adder

Example 12.5 (cont.)

- THREE CASES:

$$u = 0 \quad v \leq 9 \quad s = v \quad c_{out} = 0$$

$$u = 0 \quad v > 9 \quad s = v - 10 = (v + 6) \bmod 16 \quad c_{out} = 1$$

$$u = 1 \quad s = v + 16 - 10 = v + 6 \quad c_{out} = 1$$

\Rightarrow BCD OUTPUT

$$s = \begin{cases} (v + 6) \bmod 16 & \text{if } u = 1 \text{ or } v \geq 10 \\ v & \text{otherwise} \end{cases}$$

$$c_{out} = \begin{cases} 1 & \text{if } u = 1 \text{ or } v \geq 10 \\ 0 & \text{otherwise} \end{cases}$$

THE CONDITION $u = 1$ or $v \geq 10$ CORRESPONDS TO SWITCHING EXPRESSION

$$t = u + v_3v_2 + v_3v_1$$

Example 12.5 (cont.)

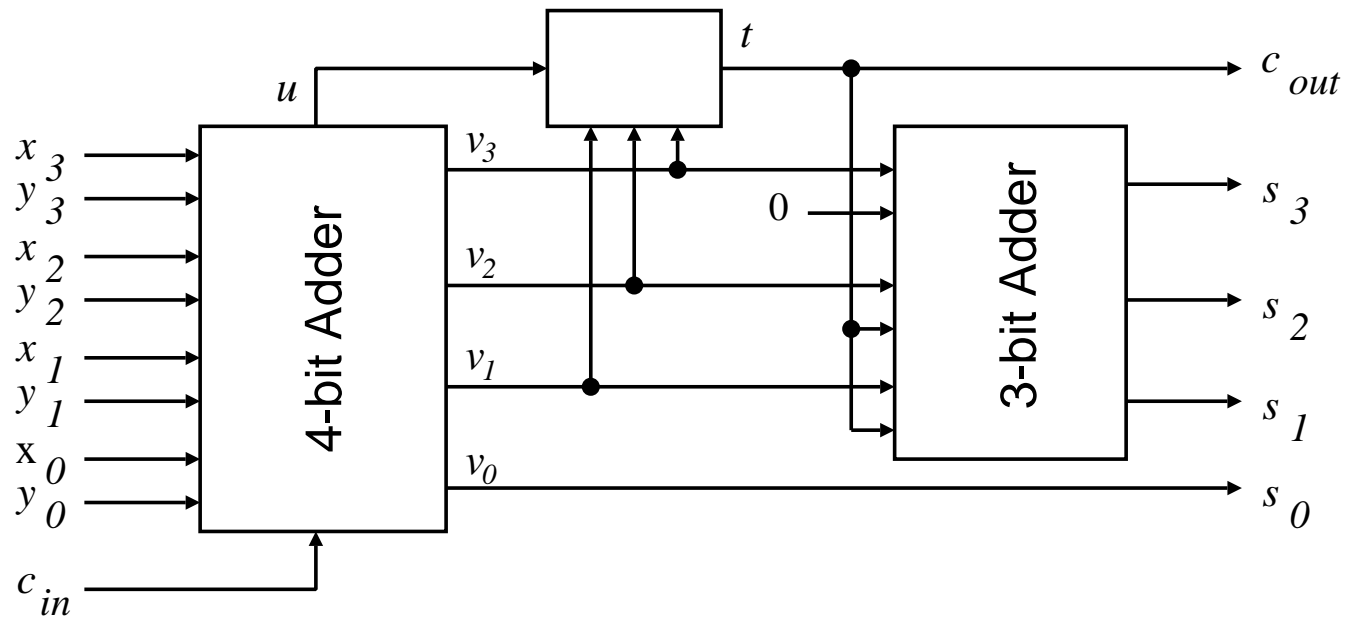


Figure 12.16: IMPLEMENTATION OF BCD ADDER MODULE

Example 12.5 (cont.)

- SIMPLIFICATION OF THE 3-BIT ADDER

$$s_3 = v_3 \oplus t(v_2 + v_1)$$


$$s_2 = v_2 \oplus tv'_1$$

$$s_1 = v_1 \oplus t$$

MOREOVER,

$$s_0 = v_0$$

$$c_{out} = t$$

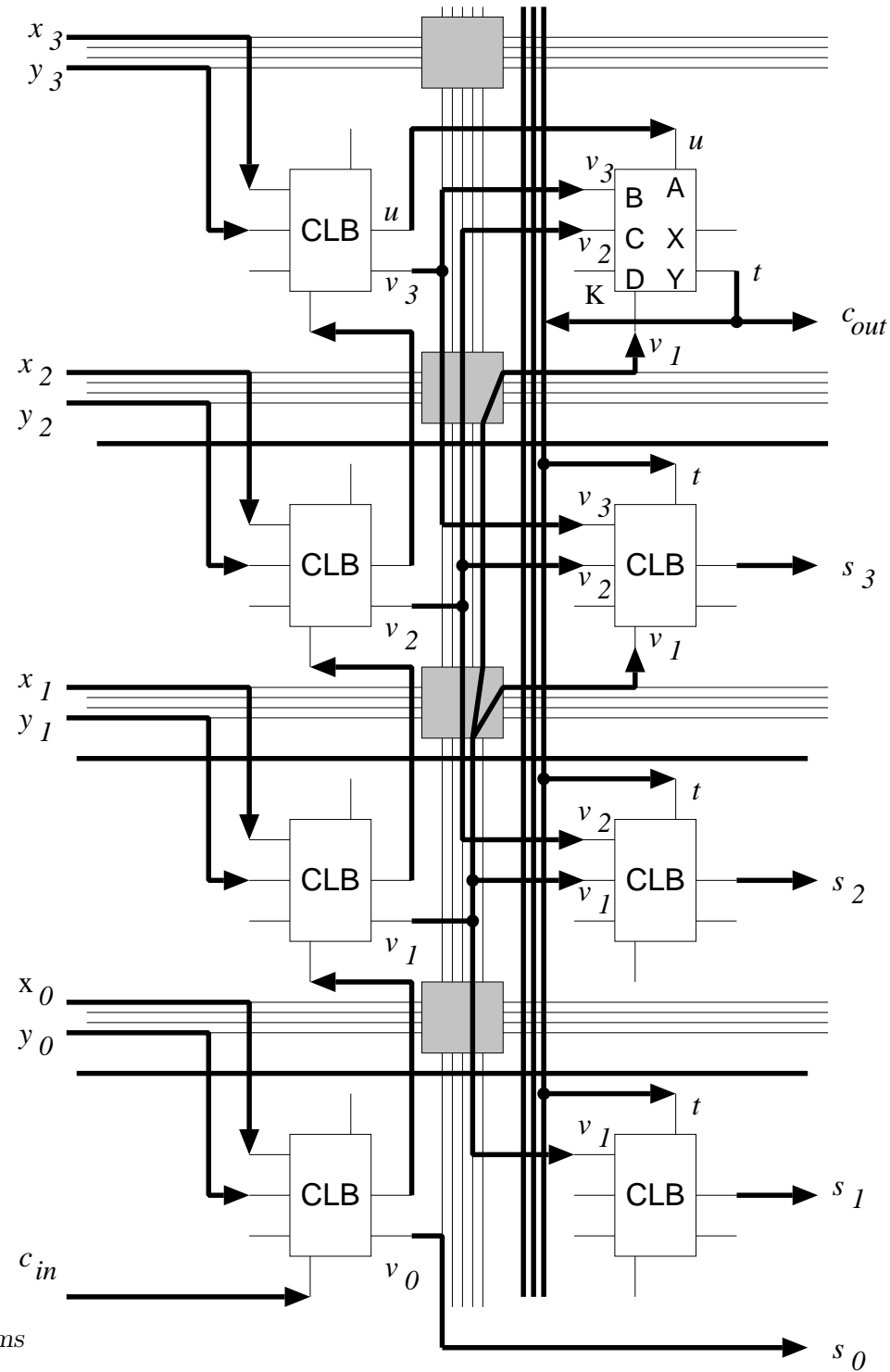

DESIGN WITH FPGAs

INVOLVES INTENSIVE USE OF CAD TOOLS AND MODULE LIBRARIES

Design entry : A SCHEMATIC ENTRY OR A BEHAVIORAL DESCRIPTION

Implementation :

- PARTITION OF DESIGN INTO SUBMODULES THAT CAN BE MAPPED ONTO CLBs,
- PLACEMENT OF SUBMODULES ONTO CHIP, AND
- ROUTING OF SIGNALS TO CONNECT THE SUBMODULES

Design verification :

- IN-CIRCUIT TESTING
- SIMULATION, AND
- TIMING ANALYSIS