

- 
- REPRESENTATION OF BINARY VARIABLES AT THE PHYSICAL LEVEL
  - BASIC SWITCH. STRUCTURE OF GATES AND THEIR OPERATION
  - REALIZATION OF GATES USING CMOS CIRCUITS
  - CHARACTERISTICS OF CIRCUITS: LOAD FACTORS AND FANOUT FACTORS, PROPAGATION DELAYS, TRANSITION TIMES, AND EFFECT OF LOAD

- 
- THREE-STATE GATES (DRIVERS) AND BUSES
  - NOISE AND NOISE MARGINS
  - EVOLUTION OF ICs. VLSI CIRCUIT-LEVEL DESIGN STYLES
  - PACKAGING LEVELS: CHIPS, BOARDS AND CABINETS.

- REPRESENTATION OF 0 AND 1 BY ELECTRICAL SIGNALS
  - VOLTAGES
  - CURRENTS
  - ELECTRICAL CHARGES
- REALIZATION OF CIRCUITS THAT OPERATE ON THESE SIGNALS TO IMPLEMENT DESIRED SWITCHING FUNCTIONS

## TYPICAL VALUES FOR A 3.3V CMOS TECHNOLOGY

|            |      |            |      |
|------------|------|------------|------|
| $V_{Hmax}$ | 3.3V | $V_{Lmax}$ | 0.8V |
| $V_{Hmin}$ | 2.0V | $V_{Lmin}$ | 0.0V |

# VOLTAGE REGIONS

---

4

 


Figure 3.1: VOLTAGE REGIONS.

# POSITIVE AND NEGATIVE LOGIC

5

 


Figure 3.2:

## *POSITIVE LOGIC*

$$V_H \longleftrightarrow 1$$



$$V_L \longleftrightarrow 0$$

## *NEGATIVE LOGIC*


$$V_H \longleftrightarrow 0$$

$$V_L \longleftrightarrow 1$$

| Input voltages |       | Output voltage | Positive logic   |     | Negative logic  |     |
|----------------|-------|----------------|------------------|-----|-----------------|-----|
| $x$            | $y$   | $z$            | $x$              | $y$ | $z$             | $z$ |
| $V_L$          | $V_L$ | $V_L$          | 0                | 0   | 0               | 1   |
| $V_L$          | $V_H$ | $V_L$          | 0                | 1   | 0               | 1   |
| $V_H$          | $V_L$ | $V_L$          | 1                | 0   | 0               | 1   |
| $V_H$          | $V_H$ | $V_H$          | 1                | 1   | 1               | 0   |
|                |       |                | $f = \text{AND}$ |     | $f = \text{OR}$ |     |

 
 


(a)

 



NMOS transistor

logical symbol

  

PMOS transistor

logical symbol

  

(b)

Figure 3.3: a) N-TYPE AND P-TYPE CONTROLLED SWITCHES. b) NMOS AND PMOS TRANSISTORS.

## SWITCH AND MOS TRANSISTORS

### **N-TYPE:**

OPEN (OFF) if  $V_{CA} < V_{Tn}$

CLOSED (ON) if  $V_{CA} > V_{Tn}$

$V_{Tn}$  – THE THRESHOLD VOLTAGE FOR N-TYPE SWITCH

### **P-TYPE:**

OPEN (OFF) if  $V_{BC} < V_{Tp}$

CLOSED (ON) if  $V_{BC} > V_{Tp}$

$V_{Tp}$  – THE THRESHOLD VOLTAGE FOR P-TYPE SWITCH

# CMOS NOT GATE

- COMPLEMENTARY MOS CIRCUIT

 


Figure 3.4: CIRCUIT, I/O CHARACTERISTIC, AND SYMBOL



# OPERATION OF NOT GATE

---

$$V_{BC} = V_{DD} - v_{in} \quad (V_{DD} = V_{BC} + v_{in})$$

$$1. \quad v_{in} < V_{Tn} \implies V_{CA} < V_{Tn}$$

$\implies$  N-SWITCH OPEN

If  $V_{DD} > V_{Tn} + V_{Tp}$  then  $V_{BC} > V_{Tp}$

$\implies$  P-SWITCH CLOSED AND  $v_{out} = V_{DD}$

$$2. \quad v_{in} > V_{DD} - V_{Tp} \implies V_{BC} < V_{Tp}$$

$\implies$  P-SWITCH IS OPEN

If  $V_{DD} > V_{Tn} + V_{Tp}$  then  $V_{CA} > V_{Tn}$

$\implies$  N-SWITCH IS CLOSED AND  $v_{out} = 0$

CIRCUIT OPERATES AS NOT GATE IF


$$V_{Lmax} < V_{Tn}$$

$$V_{Hmin} > V_{DD} - V_{Tp}$$

$$V_{DD} > V_{Tn} + V_{Tp}$$

# COMPLEMENTARY LOGIC

11


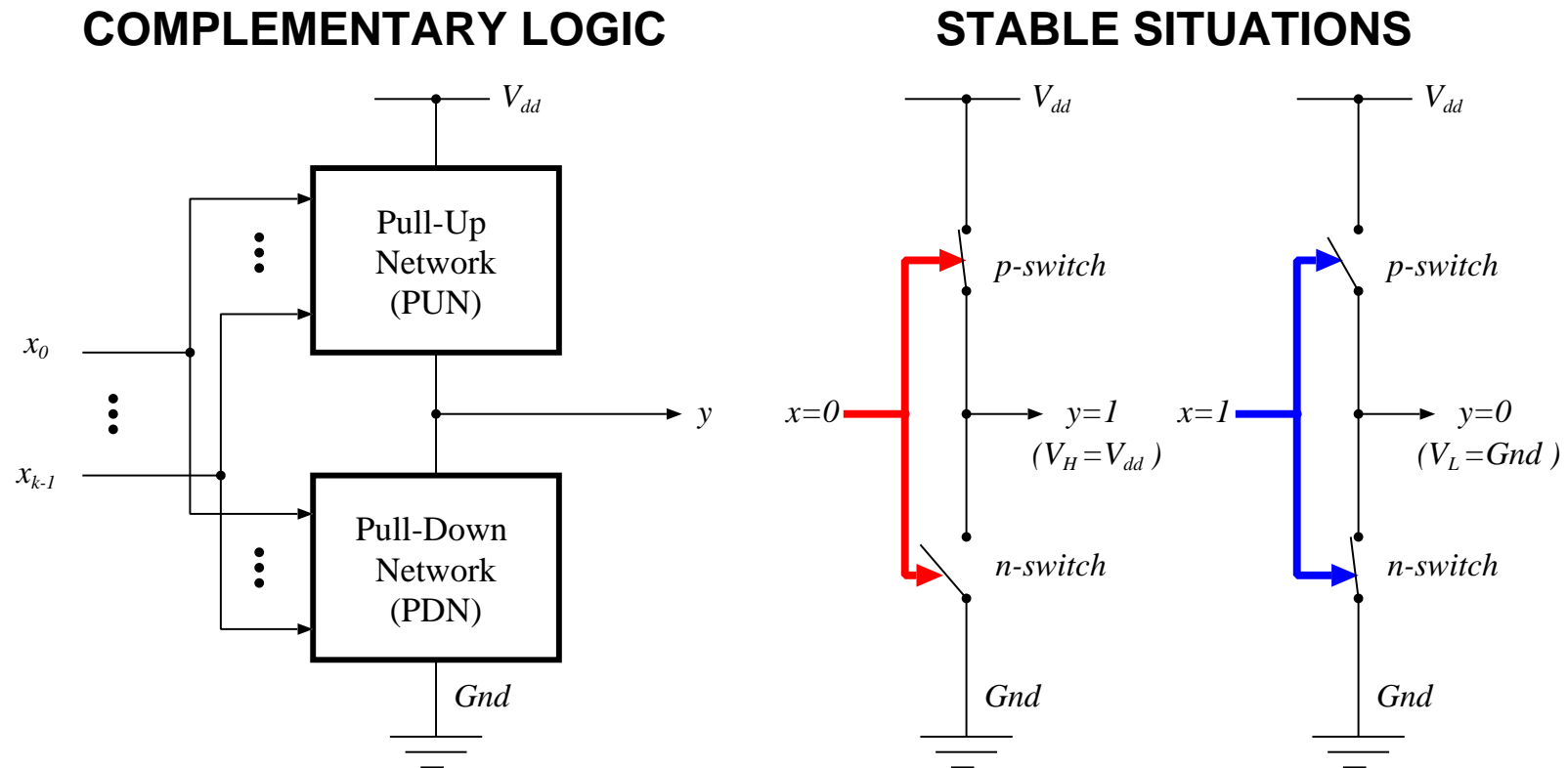


- ° no static current in stable state  
=> low power dissipation
- ° faster transitions

Figure 3.5:

# NAND and NOR GATES

Circuit 1: NAND

  

Circuit 2: NOR

 
 


Figure 3.5: CIRCUITS FOR NAND and NOR GATES.

# NAND and NOR GATES (cont.)

---

|     |     | Circuit 1 | Circuit 2 |
|-----|-----|-----------|-----------|
| $x$ | $y$ | $z$       | $z$       |
| 0   | 0   | 1         | 1         |
| 0   | 1   | 1         | 0         |
| 1   | 0   | 1         | 0         |
| 1   | 1   | 0         | 0         |

# AND and OR GATES


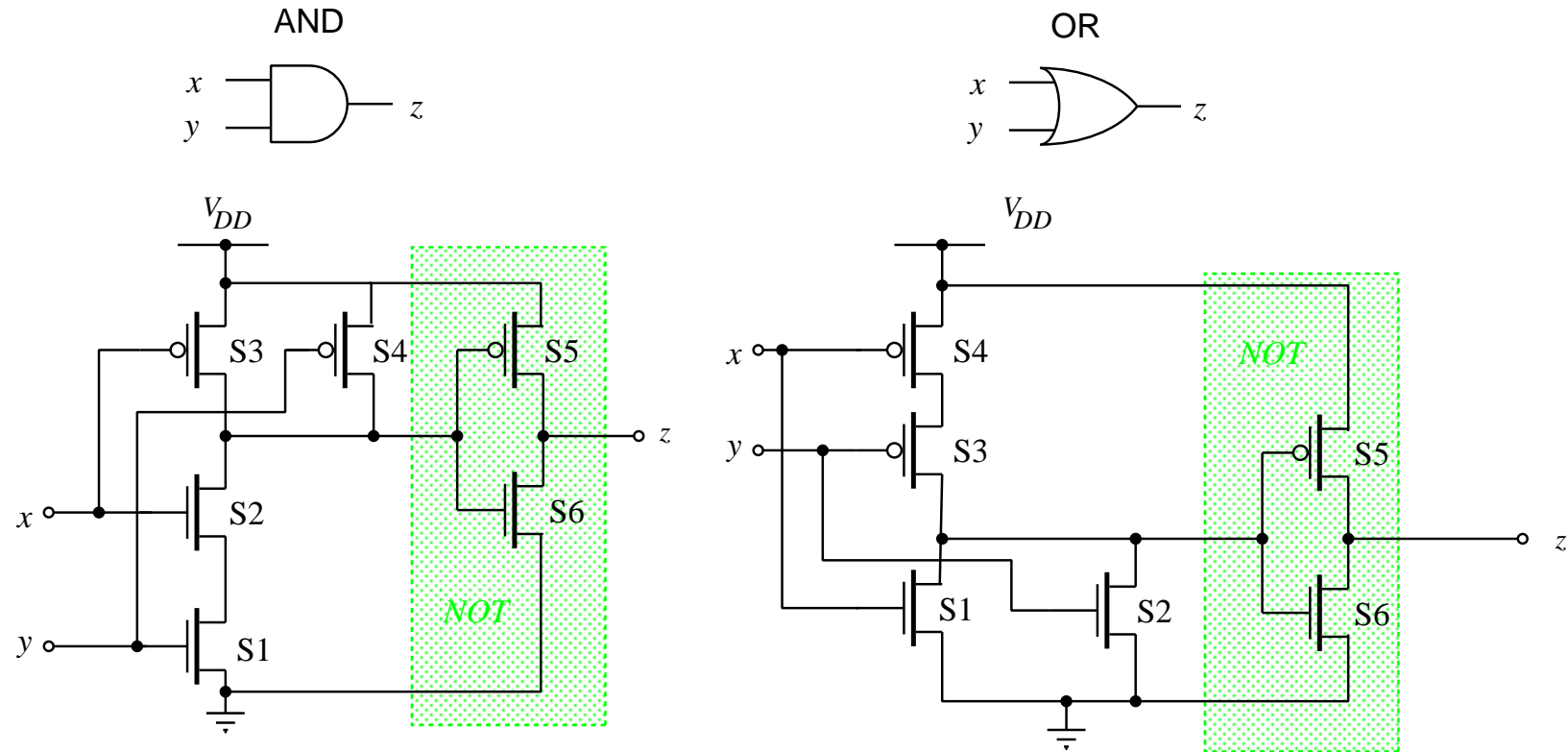



Figure 3.6: CIRCUITS FOR AND and OR GATES.

## AND-OR-INVERT (AOI)

 

$$z = (uv + xy)'$$

## OR-AND-INVERT (OAI)

 

$$z = [(u+v)(x+y)]'$$

Figure 3.7: COMPLEX GATES.

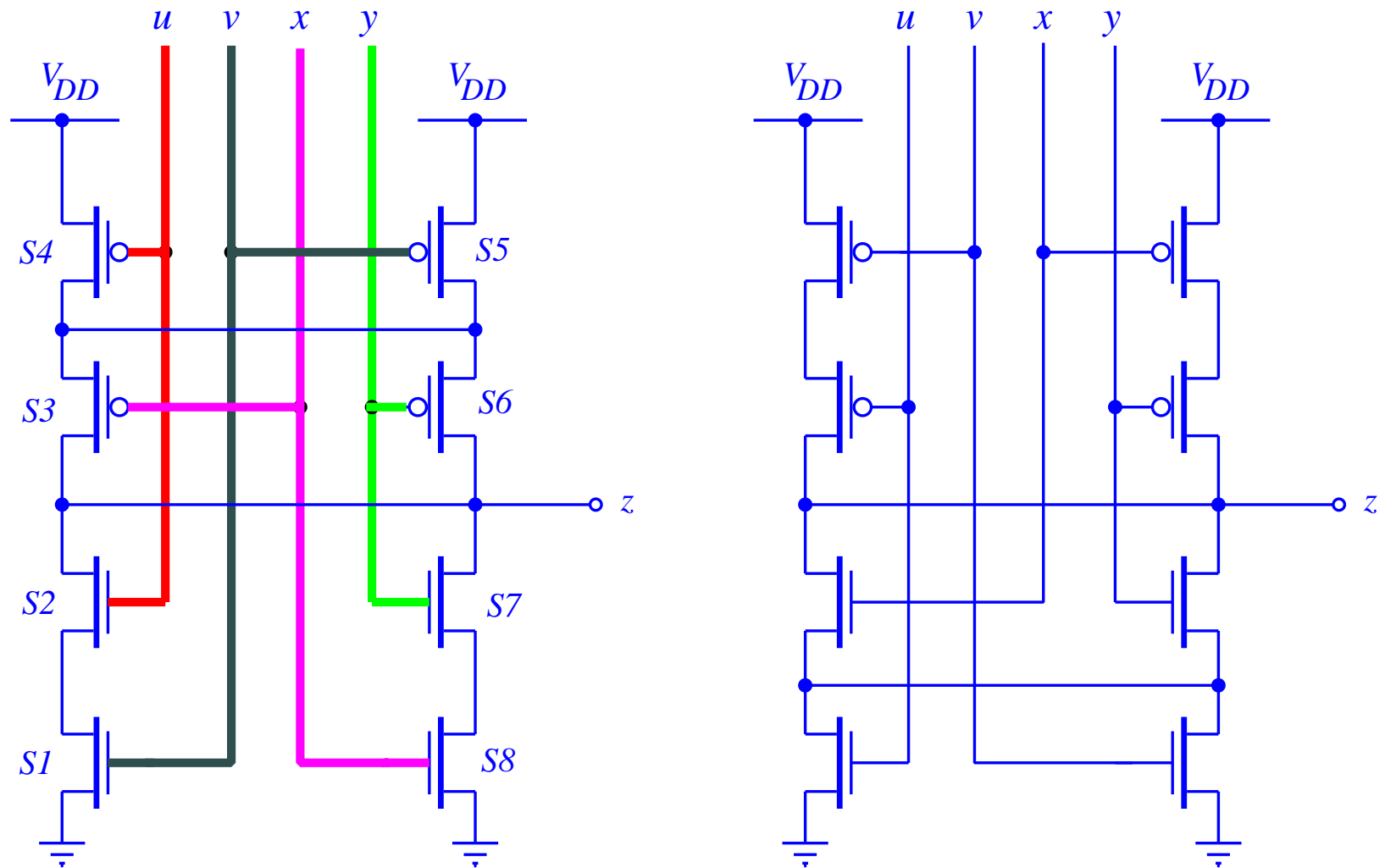


Figure 3.7: EXAMPLES OF COMPLEX GATES.



# TRANSMISSION GATE

17


 
 


Figure 3.8: a) TRANSMISSION GATE

# XOR WITH TRANSMISSION GATES

 


(b)

Figure 3.8: b) XOR GATE

| $y$ | $TG1$ | $TG2$ | $z$  |
|-----|-------|-------|------|
| 0   | ON    | OFF   | $x$  |
| 1   | OFF   | ON    | $x'$ |

# MUX WITH TRANSMISSION GATES

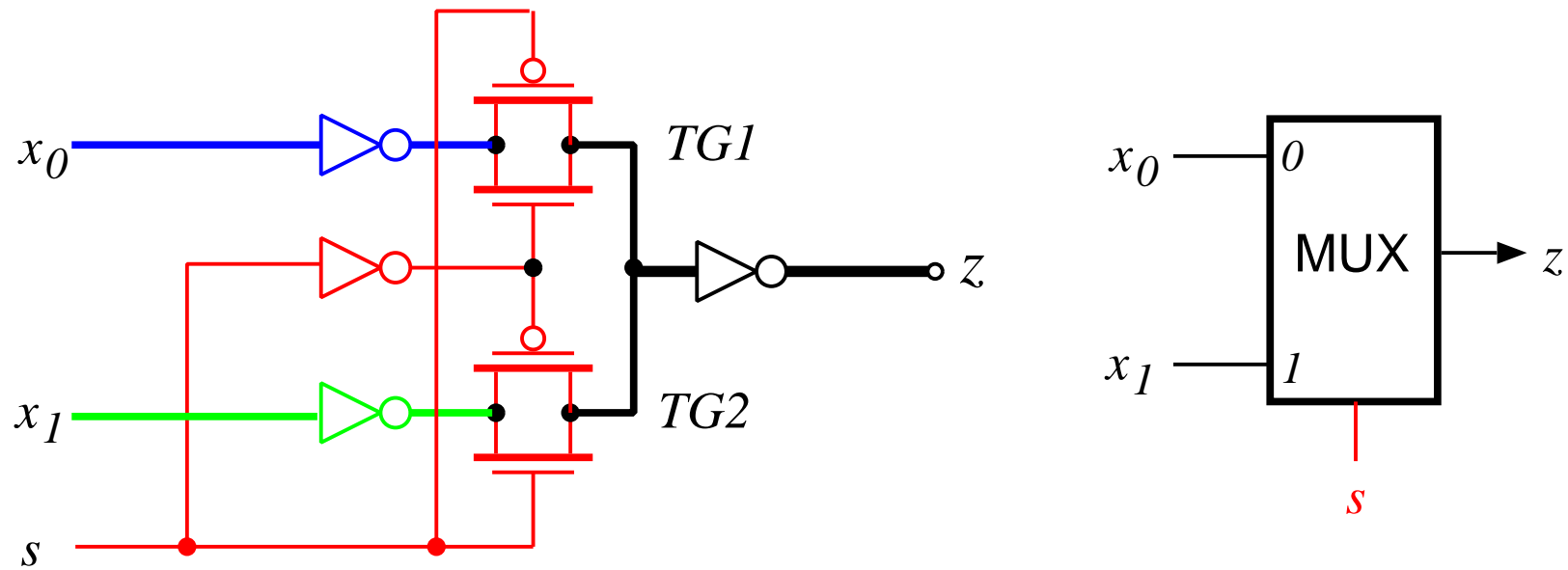

(c)

Figure 3.8: c) 2-INPUT MUX.

$$z = \text{MUX}(x_1, x_0, s) = x_1s + x_0s'$$

| $s$ | $TG1$ | $TG2$ | $z$   |
|-----|-------|-------|-------|
| 0   | ON    | OFF   | $x_0$ |
| 1   | OFF   | ON    | $x_1$ |

# TIMING PARAMETERS

 


Figure 3.9: a) PROPAGATION DELAY. b) RISE AND FALL TIMES.

# EFFECT OF LOAD

 


Figure 3.10: A GATE NETWORK

 


Figure 3.11: EQUIVALENT CIRCUIT FOR GATE INPUT.

# EFFECT OF LOAD ON PROPAGATION DELAY

22

 


Figure 3.12: EFFECT OF LOAD ON PROPAGATION DELAY.

# LOAD FACTOR AND TOTAL LOAD

---

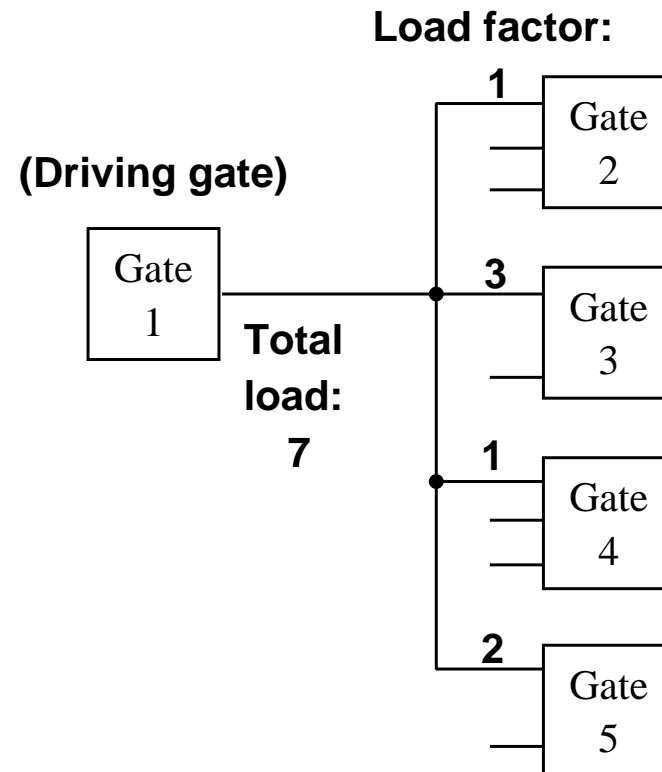


Figure 3.13: OUTPUT LOAD OF GATE 1.

# VOLTAGE VARIATIONS AND NOISE MARGINS

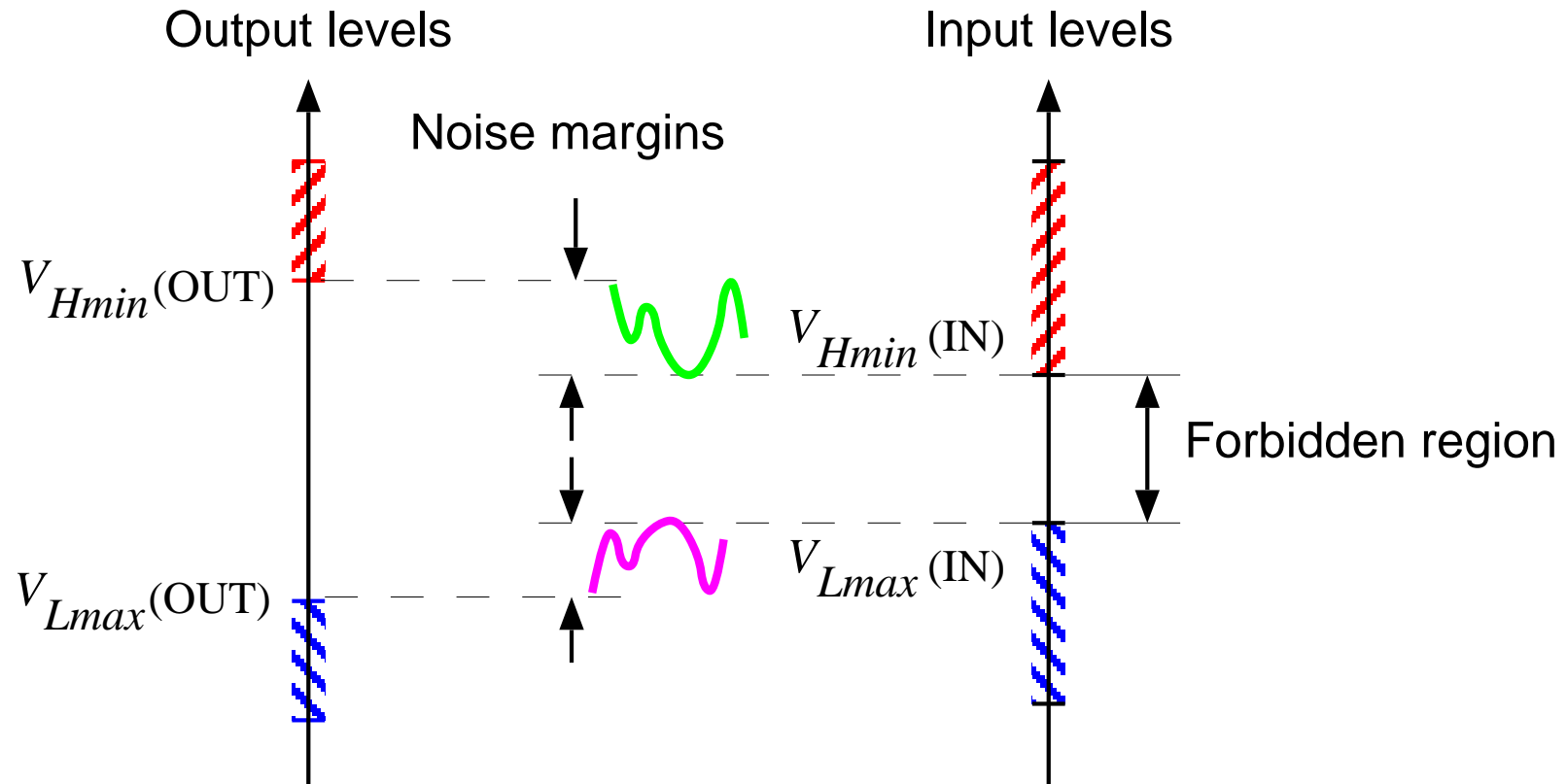


Figure 3.14: NOISE MARGINS.



# NOISE MARGINS: EXAMPLE

---

| LEVELS |                              | NOISE MARGIN |
|--------|------------------------------|--------------|
| HIGH   | $V_{Hmin}(\text{OUT})$ 2.4 V | 0.4 V        |
|        | $V_{Hmin}(\text{IN})$ 2.0 V  |              |
| LOW    | $V_{Lmax}(\text{OUT})$ 0.4 V | 0.4 V        |
|        | $V_{Lmax}(\text{IN})$ 0.8 V  |              |

# CONNECTING MODULES TO A BUS

---


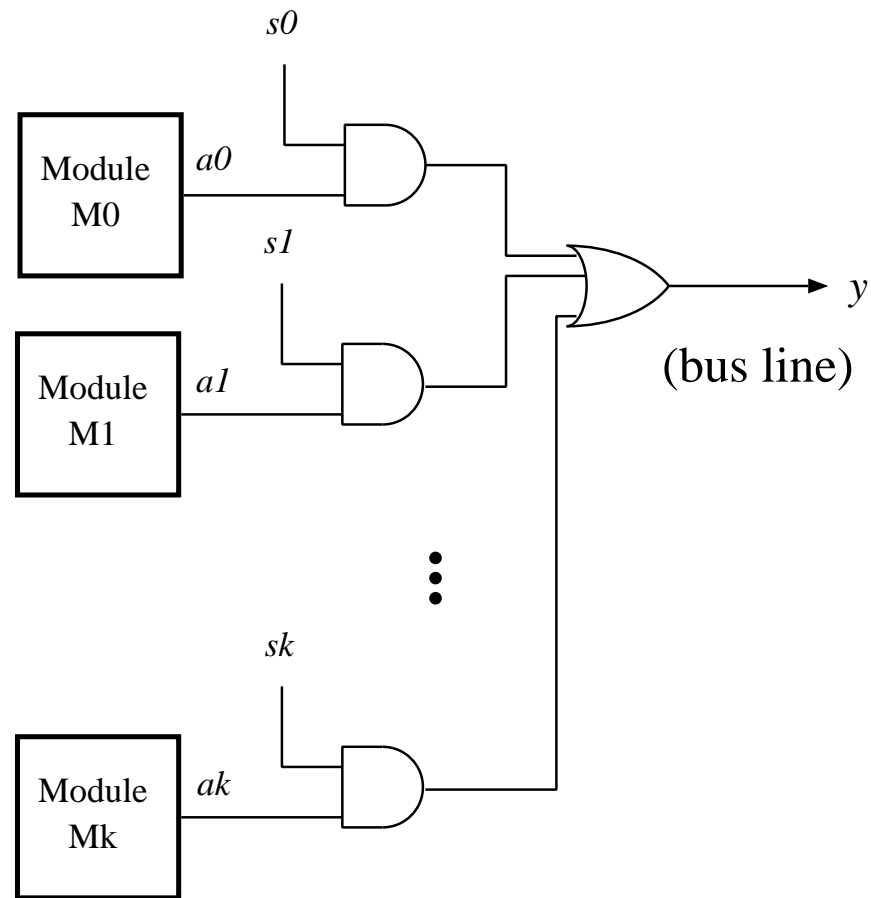


Figure 3.15: GATE NETWORK FOR SELECTING A MODULE OUTPUT.

# THREE-STATE DRIVER (BUFFER)

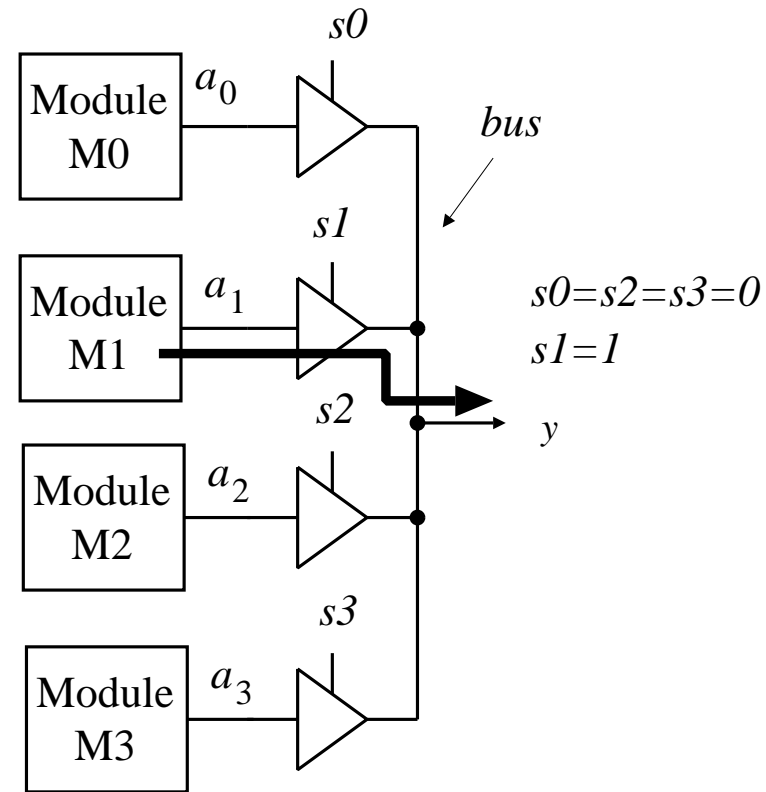

(c)

Figure 3.16: c) EXAMPLE OF USE OF THREE-STATE DRIVERS

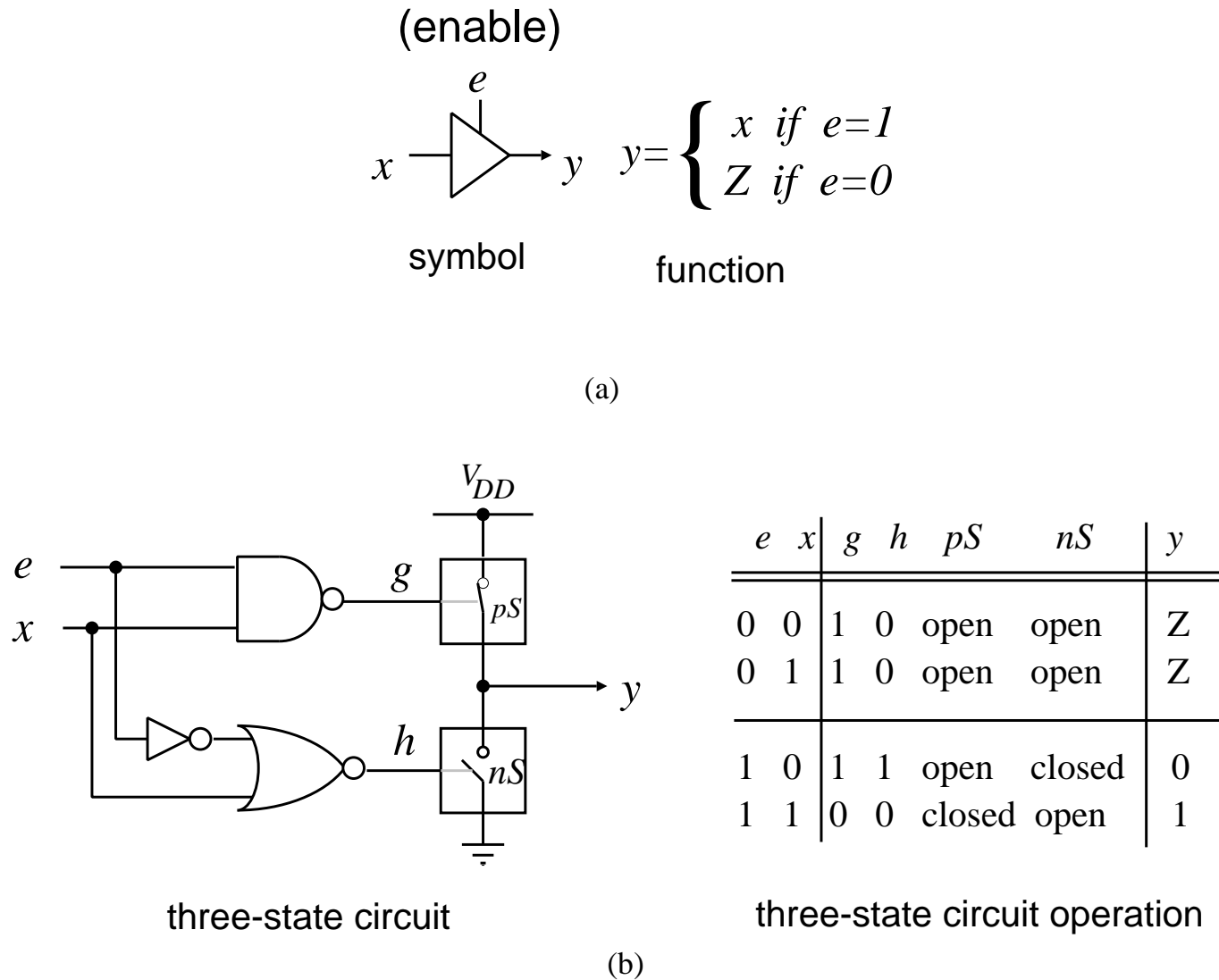


Figure 3.16: a) THREE-STATE GATE: SYMBOL AND FUNCTION. b) CIRCUIT AND OPERATION.

Table 3.2: Characteristics of a family of CMOS gates

| Gate type  | Fan-in | Propagation delays |                   | Load factor      | Size           |
|------------|--------|--------------------|-------------------|------------------|----------------|
|            |        | $t_{pLH}$<br>[ns]  | $t_{pHL}$<br>[ns] | [standard loads] | [equiv. gates] |
| AND        | 2      | $0.15 + 0.037L$    | $0.16 + 0.017L$   | 1.0              | 2              |
| AND        | 3      | $0.20 + 0.038L$    | $0.18 + 0.018L$   | 1.0              | 2              |
| OR         | 2      | $0.12 + 0.037L$    | $0.20 + 0.019L$   | 1.0              | 2              |
| OR         | 3      | $0.12 + 0.038L$    | $0.34 + 0.022L$   | 1.0              | 2              |
| NOT        | 1      | $0.02 + 0.038L$    | $0.05 + 0.017L$   | 1.0              | 1              |
| NAND       | 2      | $0.05 + 0.038L$    | $0.08 + 0.027L$   | 1.0              | 1              |
| NAND       | 3      | $0.07 + 0.038L$    | $0.09 + 0.039L$   | 1.0              | 2              |
| NAND       | 8      | $0.24 + 0.038L$    | $0.42 + 0.019L$   | 1.0              | 6              |
| NOR        | 2      | $0.06 + 0.075L$    | $0.07 + 0.016L$   | 1.0              | 1              |
| NOR        | 3      | $0.16 + 0.111L$    | $0.08 + 0.017L$   | 1.0              | 2              |
| NOR        | 8      | $0.54 + 0.038L$    | $0.23 + 0.018L$   | 1.0              | 6              |
| XOR        | 2*     | $0.30 + 0.036L$    | $0.30 + 0.021L$   | 1.1              | 3              |
|            |        | $0.16 + 0.036L$    | $0.15 + 0.020L$   | 2.0              |                |
| XOR        | 3*     | $0.50 + 0.038L$    | $0.49 + 0.027L$   | 1.1              | 6              |
|            |        | $0.28 + 0.039L$    | $0.27 + 0.027L$   | 2.4              |                |
|            |        | $0.19 + 0.036L$    | $0.17 + 0.025L$   | 2.1              |                |
| XNOR       | 2*     | $0.30 + 0.036L$    | $0.30 + 0.021L$   | 1.1              | 3              |
|            |        | $0.16 + 0.036L$    | $0.15 + 0.020L$   | 2.0              |                |
| XNOR       | 3*     | $0.50 + 0.038L$    | $0.49 + 0.027L$   | 1.1              | 6              |
|            |        | $0.28 + 0.039L$    | $0.27 + 0.027L$   | 2.3              |                |
|            |        | $0.19 + 0.036L$    | $0.17 + 0.025L$   | 1.3              |                |
| 2-OR/NAND2 | 4      | $0.17 + 0.075L$    | $0.10 + 0.028L$   | 1.0              | 2              |
| 2-AND/NOR2 | 4      | $0.17 + 0.075L$    | $0.10 + 0.028L$   | 1.0              | 2              |

# VLSI CIRCUIT-LEVEL DESIGN STYLES

---

- FULL-CUSTOM
- SEMI-CUSTOM (standard cells)
- GATE-ARRAY; FIELD-PROGRAMMABLE GATE ARRAY (FPGA)

FPGAs DISCUSSED IN CHAPTER 12

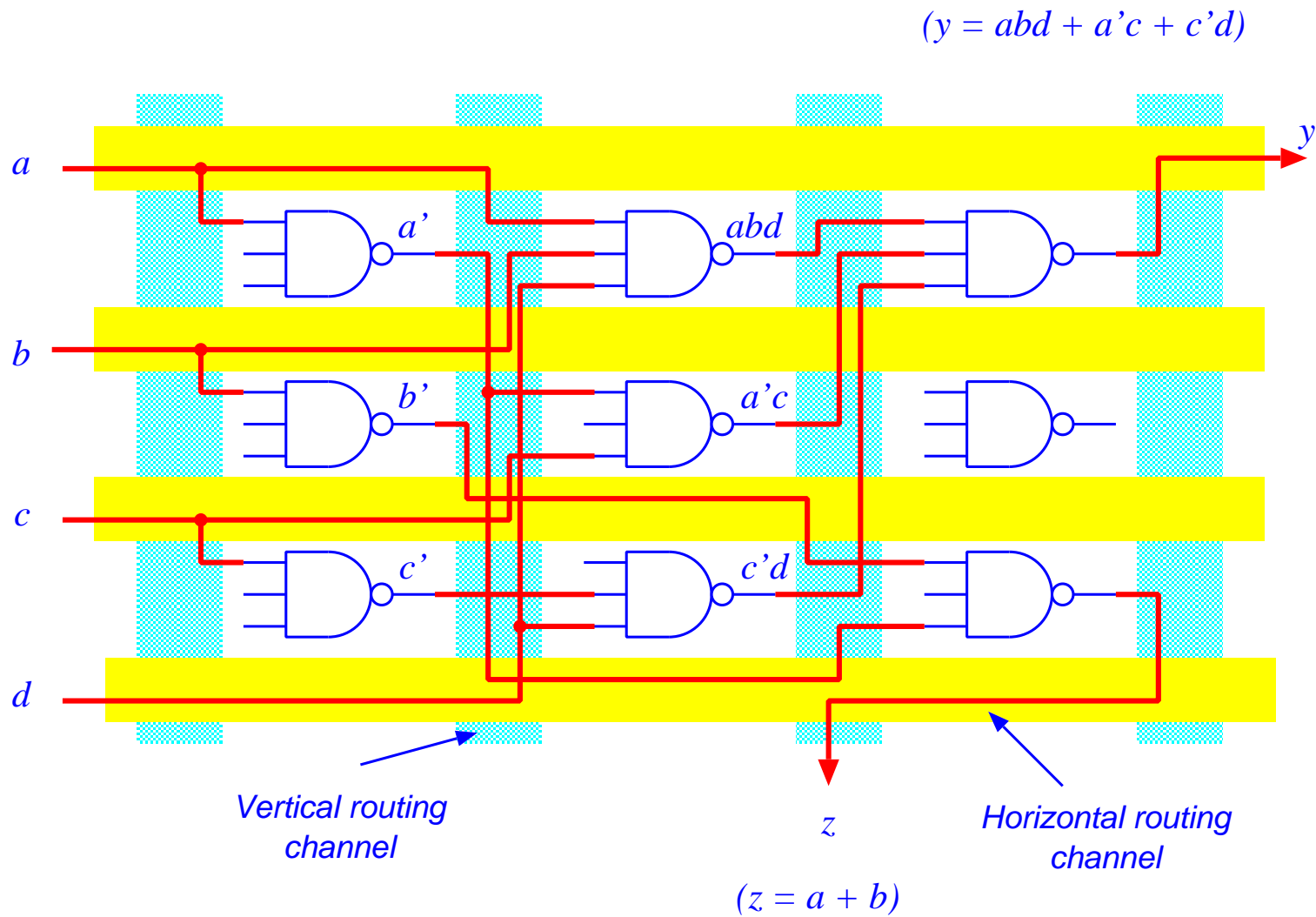


Figure 3.17: EXAMPLE OF GATE ARRAY.

# PACKAGING LEVEL: CHIPS, BOARDS, AND CABINETS

---

32

 


Figure 3.18: SILICON WAFER, CHIP AND INTEGRATED CIRCUIT PACKAGE



 


Figure 3.19: PACKAGING LEVELS

## PACKAGING LEVELS: EXAMPLE

---

IBM 3081 central processing unit:

| Level of Packaging    | Number of Components | Size [mm×mm] |
|-----------------------|----------------------|--------------|
| Module                | 100–133 chips        | 90 × 90      |
| PC Board              | 6 – 9 modules        | 600 × 700    |
| Subsystem (processor) | 3 boards             |              |
| System (CPU)          | 2 subsystems         |              |