

[CS M51A F14] SOLUTION TO QUIZ 2


Date: 10/31/14

TA: Hyunjin Kim (roykim78@cs.ucla.edu)

Quiz Problems (50 points total)

 Problem 1 (20 points)

The following pull-up network is part of a complex CMOS gate that we wish to implement.



1. **(10 points)** Write the expression for the pull-up network. From this, derive the expression for the pull-down network using switching algebra. Make sure the inverters are on the correct variables.

Solution From the given network we can directly write for the pull-up network


$$z = (a'c' + b'(d' + e') + (f' + g'))h'$$

Therefore, the expression for the pull-down network is

$$\begin{aligned} z' &= [(a'c' + b'(d' + e') + (f' + g'))h']' \\ &= (a'c' + b'(d' + e') + (f' + g'))' + h \\ &= (a + c)(b + (d' + e')')fg + h \\ &= (a + c)(b + de)fg + h \end{aligned}$$

 2. **(10 points)** Draw the pull-down network of NMOS transistors that correspond to the expression and completes the CMOS gate that drives output z . To keep it minimal, only use one NMOS transistor for each input variable.

Solution Using the expression for z' , we can create the circuit as shown.



Problem 2 (10 points)

Answer the following questions on the given switching expression.

$$E(x, y, z) = \sum m(1, 2, 3, 6)$$

1. (5 points) Using K-maps, find all the prime implicants for $E(x, y, z)$.

Solution

		z		
x		0	1	1
		0	0	1
		y		


The equivalent product terms are $x'z$, $x'y$, and yz' .

2. (5 points) Which of these prime implicants are **not** essential?

Solution $x'y$ does not have any squares that it covers alone, therefore it is not essential.

Problem 3 (20 points)

Given the circuit shown below,

 

show the items below for the worst case path.

The necessary gate characteristics are listed in the following table.

Gate Type	Fan-in	Propagation Delays (ns)		Load Factor I
		t_{pLH}	t_{pHL}	
AND	2	$0.20 + 0.038L$	$0.18 + 0.018L$	1.0
NOT	1	$0.02 + 0.038L$	$0.05 + 0.017L$	1.0
NAND	2	$0.05 + 0.038L$	$0.08 + 0.027L$	1.0
NOR	2	$0.06 + 0.075L$	$0.07 + 0.016L$	1.0

1. (20 points) For $t_{pLH}(x \rightarrow z)$, fill in the blanks with the appropriate information. For the Delay section, write down the equation from the table with the proper L value shown. You do not need to obtain the final delay value for full credit.

Solution Looking at the circuit, we can get:

Gate type G1: NAND2 \rightarrow G2: NAND2 \rightarrow G6: AND2 \rightarrow G7: NAND2 \rightarrow G9: NOR2

& fan-in

LH / HL G1: HL \rightarrow G2: LH \rightarrow G6: LH \rightarrow G7: HL \rightarrow G9: LH

Total load G1: 3 \rightarrow G2: 1 \rightarrow G6: 2 \rightarrow G7: 1 \rightarrow G9: 3

Delay G1: $0.08 + 0.027 \times 3 \rightarrow$ G2: $0.05 + 0.038 \times 1 \rightarrow$ G6: $0.20 + 0.038 \times 2 \rightarrow$
 G7: $0.08 + 0.027 \times 1 \rightarrow$ G9: $0.06 + 0.075 \times 3$