

- GATE NETWORKS: DEFINITION
- SETS OF GATES: (AND OR NOT), NAND NOR XOR
- ANALYSIS AND DESCRIPTION OF GATE NETWORKS

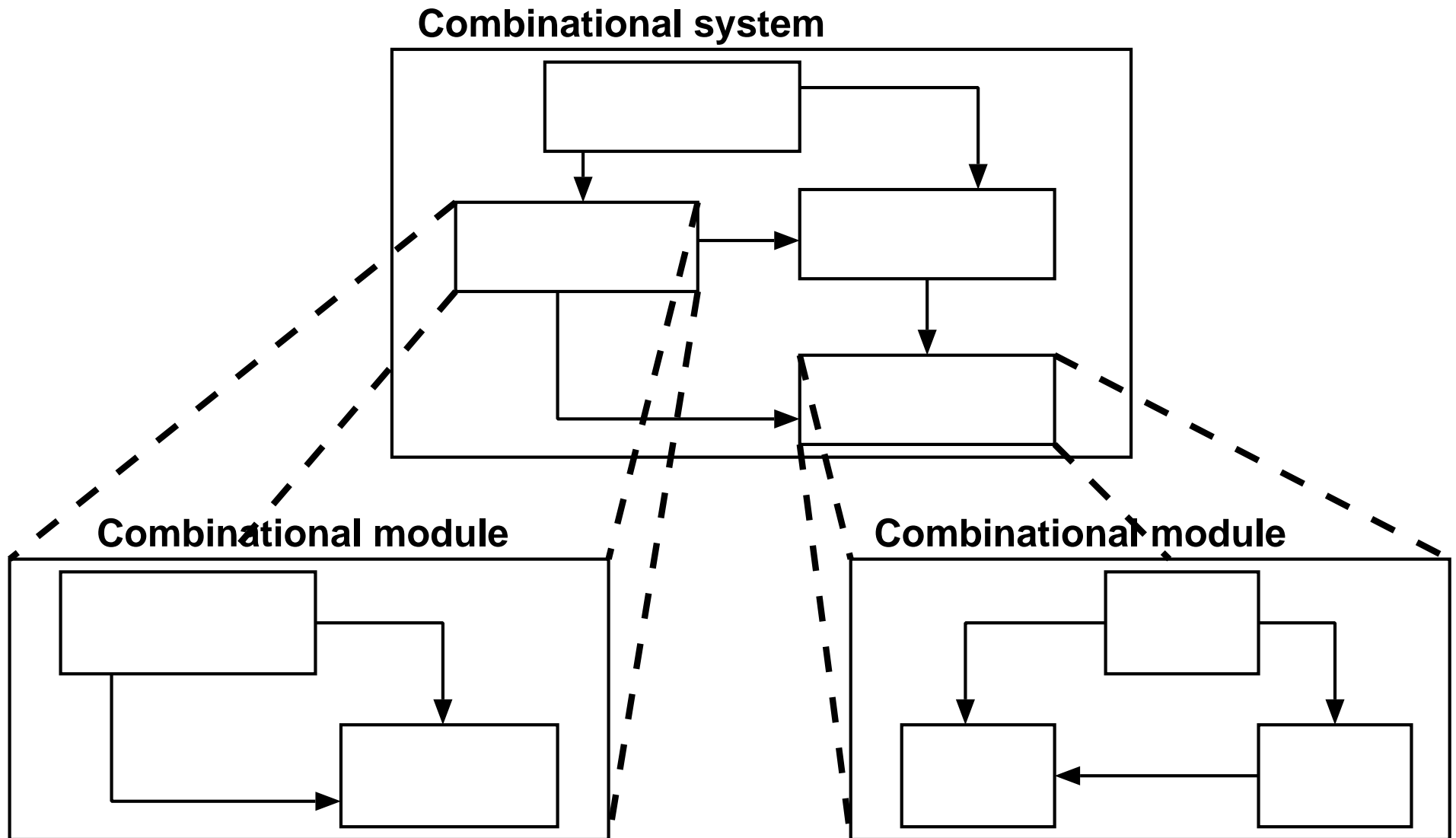


Figure 4.1: HIERARCHICAL IMPLEMENTATION OF A MODULE

 


Figure 4.2: A GATE NETWORK

- GATES
- EXTERNAL INPUTS AND OUTPUTS
- CONNECTIONS

# GATE NETWORKS (cont.)

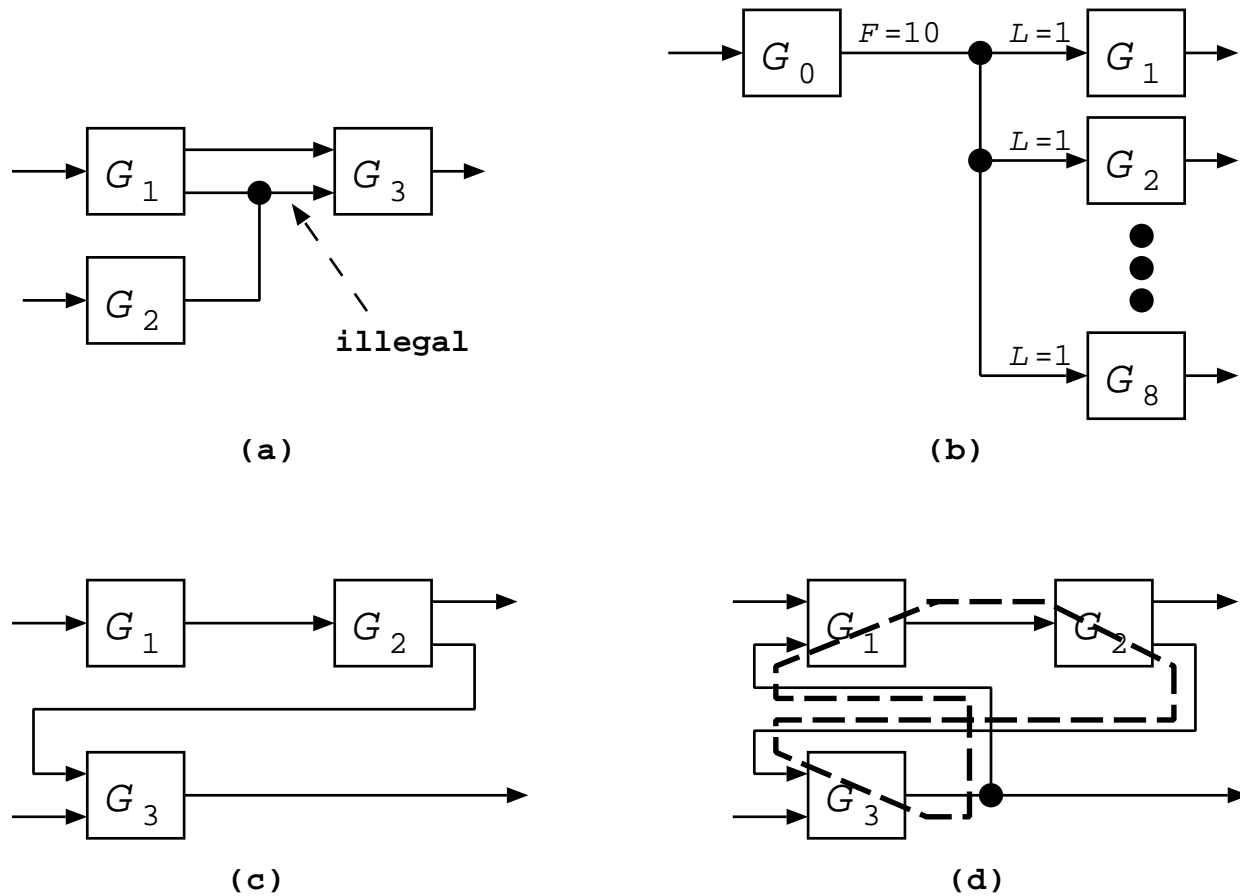


Figure 4.3: a) ILLEGAL NETWORK CONNECTION. b) ACCEPTABLE OUTPUT LOAD. c) LOOP-FREE NETWORK. d) LOOP NETWORK

- LOGIC DIAGRAM (GRAPHICAL REPRESENTATION)
- NET LIST (TABULAR REPRESENTATION)
- HDL DESCRIPTION (PROGRAM)

 


Figure 4.4: a) GRAPHICAL REPRESENTATION (LOGIC DIAGRAM)

Gate	Type	Inputs	Output
A	AND – 2	$A_1$	$A_3$
B	AND – 3	$A_2$	
		$B_1$	$B_4$
		$B_2$	
		$B_3$	
C	OR – 2	$C_1$	$C_3$
		$C_2$	

Gates

From	To
$x_3$	$A_1$
$x_2$	$A_2$
$x_2$	$B_1$
$x_1$	$B_2$
$x_0$	$B_3$
$A_3$	$C_1$
$B_4$	$C_2$
$C_3$	$z$

Connections

(b)

$$A\_3 \leq x_3 \text{ and } x_2;$$

$$B\_4 \leq x_2 \text{ and } x_1 \text{ and } x_0;$$

$$C\_3 \leq A\_3 \text{ or } B\_4;$$

$$z \leq C\_3;$$

(c)

- FUNCTIONAL SPECIFICATION
- INPUT LOAD FACTORS OF THE NETWORK INPUTS;
- FAN-OUT FACTOR OF THE NETWORK OUTPUTS (ONLY FOR SOME TECHNOLOGIES); AND
- PROPAGATION DELAYS THROUGH THE NETWORK

- Set {AND,OR,NOT}

$$z = (((x_0 + x_1)x_2)' + x_2x_3 + x_4)'$$

 


Figure 4.4: CORRESPONDENCE AMONG SWITCHING EXPRESSION AND AND-OR-NOT NETWORK



# UNIVERSAL SETS OF GATES (cont.)

- Sets  $\{\text{AND}, \text{NOT}\}$  and  $\{\text{OR}, \text{NOT}\}$

$$x_{n-1} + x_{n-2} + \dots x_i + \dots x_0 = (x'_{n-1} x'_{n-2} \dots x'_i \dots x'_0)'$$

 


Figure 4.5: AND-NOT IMPLEMENTATION OF AN OR GATE

# UNIVERSAL SETS OF GATES (cont.)

---

- Sets {NAND} and {NOR}

$$x' = (xx)'$$

$$NOT(x) = NAND(x, x)$$

$$x_1x_0 = ((x_1x_0)')' = ((x_1x_0)'(x_1x_0)')'$$

$$AND(x_1, x_0) = NAND(NAND(x_1, x_0), NAND(x_1, x_0))$$

# UNIVERSAL SETS OF GATES (cont.)

---

11


 



Figure 4.6: IMPLEMENTATIONS WITH NAND GATES: a) NOT; b) AND

# MIXED-LOGIC NOTATION

---

 


$$z = (x_{n-1} \dots x_1 x_0)'$$

 


$$z = x'_{n-1} + \dots + x'_1 + x'_0$$

(a)

 

$$z = (x_{n-1} + \dots + x_1 + x_0)'$$

 

$$z = x'_{n-1} \dots x'_1 x'_0$$

(b)

Figure 4.7: MIXED-LOGIC NOTATION: a) NAND GATE b) NOR GATE

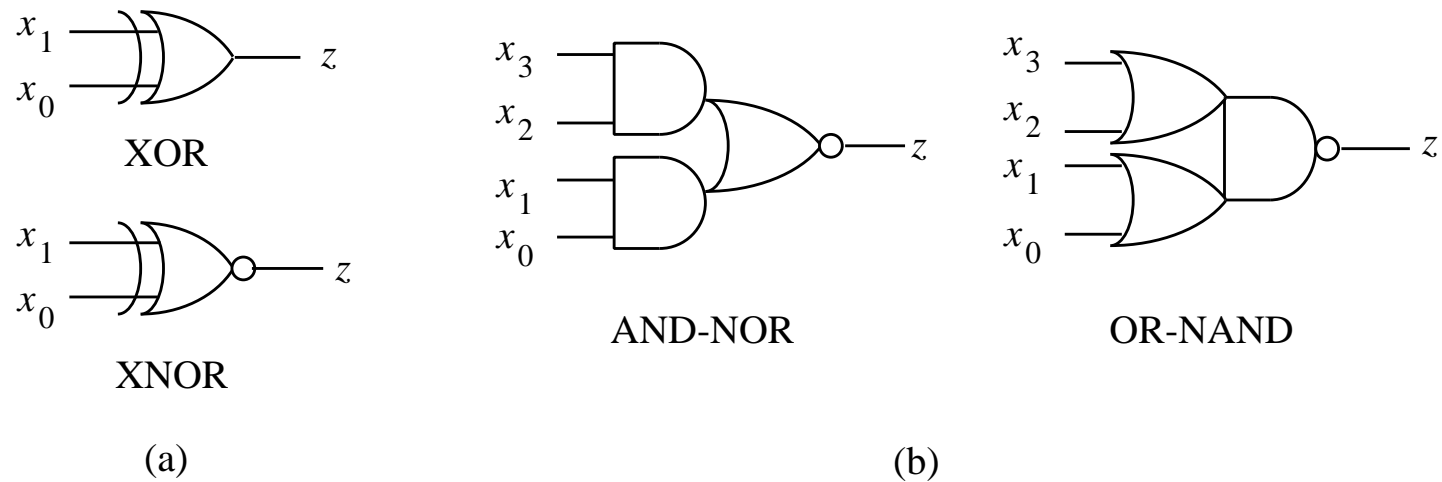


Figure 4.8: ADDITIONAL GATES IN CMOS a) XOR and XNOR, b) COMPLEX GATE STRUCTURES: AND-OR and OR-AND

- FUNCTIONAL ANALYSIS:
  1. OBTAIN I/O SWITCHING EXPRESSIONS
  2. OBTAIN A TABULAR REPRESENTATION OF THE (BINARY) FUNCTION (IF FEW VARIABLES)
  3. DEFINE HIGH-LEVEL INPUT AND OUTPUT VARIABLES; USE CODES TO RELATE THESE VARIABLES WITH THE BIT-VECTORS
  4. OBTAIN A HIGH-LEVEL SPECIFICATION OF THE SYSTEM
  
- NETWORK CHARACTERISTICS:  
INPUT LOAD FACTORS, FAN-OUT FACTORS, AND DELAYS

## OBTAIN SWITCHING EXPRESSIONS

---

- ASSIGN NAMES TO EACH CONNECTION IN THE NETWORK
- WRITE SWITCHING EXPRESSIONS FOR EACH GATE OUTPUT
- SUBSTITUTE ALL INTERNAL NAMES TO OBTAIN EXTERNAL OUTPUTS IN TERMS OF EXTERNAL INPUTS

# Example

16

 


Figure 4.9: GATE NETWORK FOR ANALYSIS



## EXAMPLE (cont.)

---

### OUTPUT EXPRESSIONS:

$$\begin{aligned}
 z_0 &= T_2 + T_3 \\
 &= x'_0 x'_1 x_2 + x_0 T_1 \\
 &= x'_0 x'_1 x_2 + x_0 (x'_2 + x_3) \\
 &= x'_0 x'_1 x_2 + x_0 x'_2 + x_0 x_3
 \end{aligned}$$

$$\begin{aligned}
 z_1 &= T_5 + T_6 \\
 &= x_1 x_2 x_3 + T'_4 \\
 &= x_1 x_2 x_3 + (T_1 x'_0 x_1)' \\
 &= x_1 x_2 x_3 + T'_1 + x_0 + x'_1 \\
 &= x_1 x_2 x_3 + x_2 x'_3 + x_0 + x'_1
 \end{aligned}$$

## REDUCED EXPRESSIONS:

$$\begin{aligned} z_0 &= x'_0 x'_1 x_2 + x_0 x'_2 + x_0 x_3 && \text{(no reduction possible)} \\ z_1 &= x_0 + x'_1 + x_2 \end{aligned}$$

# HIERARCHICAL APPROACH

---

- DECOMPOSE THE NETWORK INTO SUBNETWORKS (MODULES)
- ANALYZE EACH SUBNETWORK SEPARATELY
- USE SUBSTITUTION TO OBTAIN THE NETWORK FUNCTION

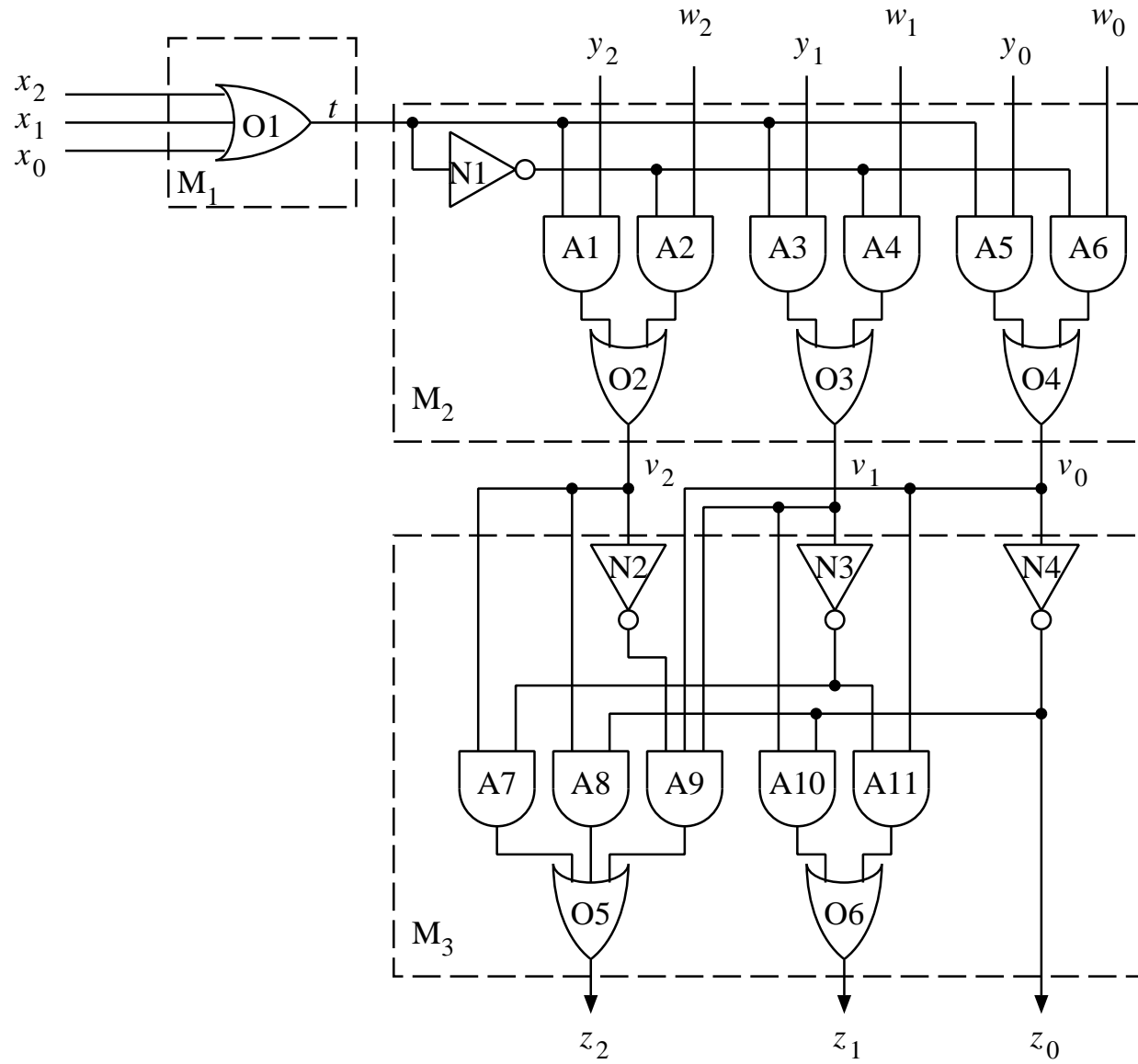


Figure 4.10: NETWORK FOR HIERARCHICAL ANALYSIS

## EXAMPLE cont.

---

VERIFY THAT THE NETWORK SATISFIES THE SPECIFICATION:

Inputs:  $x, y, w \in \{0, 1, \dots, 7\}$

Output:  $z \in \{0, 1, \dots, 7\}$

Function:  $z = \begin{cases} (y + 1) \bmod 8 & \textbf{if } x \neq 0 \\ (w + 1) \bmod 8 & \textbf{if } x = 0 \end{cases}$

- SUBNETWORKS

$M_1$ :

$$t = x_2 \mathbf{+} x_1 \mathbf{+} x_0$$

$$t = \begin{cases} 1 & \mathbf{if} \ x \neq 0 \\ 0 & \mathbf{otherwise} \end{cases}$$

$M_2$ :

$$v_i = y_i t \mathbf{+} w_i t' \quad (i = 0, 1, 2)$$

$$\underline{v} = \begin{cases} \underline{y} & \mathbf{if} \ t = 1 \\ \underline{w} & \mathbf{if} \ t = 0 \end{cases}$$

$$v = \begin{cases} y & \mathbf{if} \ t = 1 \\ w & \mathbf{if} \ t = 0 \end{cases}$$

$M_3$ :

$$z_2 = v_2' v_1 v_0 \mathbf{+} v_2 v_1' \mathbf{+} v_2 v_0'$$

$$z_1 = v_1 v_0' \mathbf{+} v_1' v_0$$

$$z_0 = v_0'$$

## EXAMPLE (cont.)

---

- HIGH-LEVEL SPECIFICATION:

$v_2$	$v_1$	$v_0$	$z_2$	$z_1$	$z_0$	$v$	$z$
0	0	0	0	0	1	0	1
0	0	1	0	1	0	1	2
0	1	0	0	1	1	2	3
0	1	1	1	0	0	3	4
1	0	0	1	0	1	4	5
1	0	1	1	1	0	5	6
1	1	0	1	1	1	6	7
1	1	1	0	0	0	7	0

FROM TABLE, WE GET

$$z = (v + 1) \bmod 8$$

## SECOND LEVEL OF ANALYSIS:

$$z = \begin{cases} (y + 1) \bmod 8 & \mathbf{if} \ x \neq 0 \\ (w + 1) \bmod 8 & \mathbf{if} \ x = 0 \end{cases}$$

THIS CORRESPONDS TO THE ORIGINAL SPECIFICATION  
OF THE FUNCTION



# ANALYSIS OF NETWORKS WITH NOT, NAND and NOR

25

 


Figure 4.11: a) NAND NETWORK; b) NETWORK REDRAWN IN MIXED-LOGIC NOTATION

## ANALYSIS (cont.)

---

- USE MIXED-LOGIC TRANSFORMATIONS

$$\begin{aligned} z &= x'_5 + (x_4 + x'_3)(x'_2 + x_1x'_0) \\ &= x'_5 + x_4x'_2 + x_3x'_2 + x_4x_1x'_0 + x'_3x_1x'_0 \end{aligned}$$

 
 
 


Figure 4.12: a) NOR NETWORK; b) NETWORK REDRAWN IN MIXED-LOGIC NOTATION

## ANALYSIS (cont.)

---

$$\begin{aligned} z &= ((x_2 + x'_1)(x'_2 + x_1) + x_0)(x'_2 + x'_1 + x'_0) \\ &= (x_2 + x'_1 + x_0)(x'_2 + x_1 + x_0)(x'_2 + x'_1 + x'_0) \\ &= (x_2x_1 + x'_2x'_1 + x_0)(x'_2 + x'_1 + x_0) \\ &= x'_2x'_1 + x_0 \end{aligned}$$

# ANALYSIS OF CHARACTERISTICS

---

- LOAD FACTOR OF A NETWORK INPUT
- FAN-OUT FACTOR OF A NETWORK OUTPUT
- SIZE OF THE NETWORK
- NETWORK (PROPAGATION) DELAY
- NUMBER OF LEVELS OF A NETWORK
- DYNAMIC CHARACTERISTICS

Table 4.3: Characteristics of a family of CMOS gates (partial)

Gate type	Fan-in	Propagation delays		Load factor	Size [equiv. gates]
		$t_{pLH}$ [ns]	$t_{pHL}$ [ns]	[standard loads]	
AND	2	$0.15 + 0.037L$	$0.16 + 0.017L$	1.0	2
AND	3	$0.20 + 0.038L$	$0.18 + 0.018L$	1.0	2
OR	2	$0.12 + 0.037L$	$0.20 + 0.019L$	1.0	2
OR	3	$0.12 + 0.038L$	$0.34 + 0.022L$	1.0	2
NOT	1	$0.02 + 0.038L$	$0.05 + 0.017L$	1.0	1

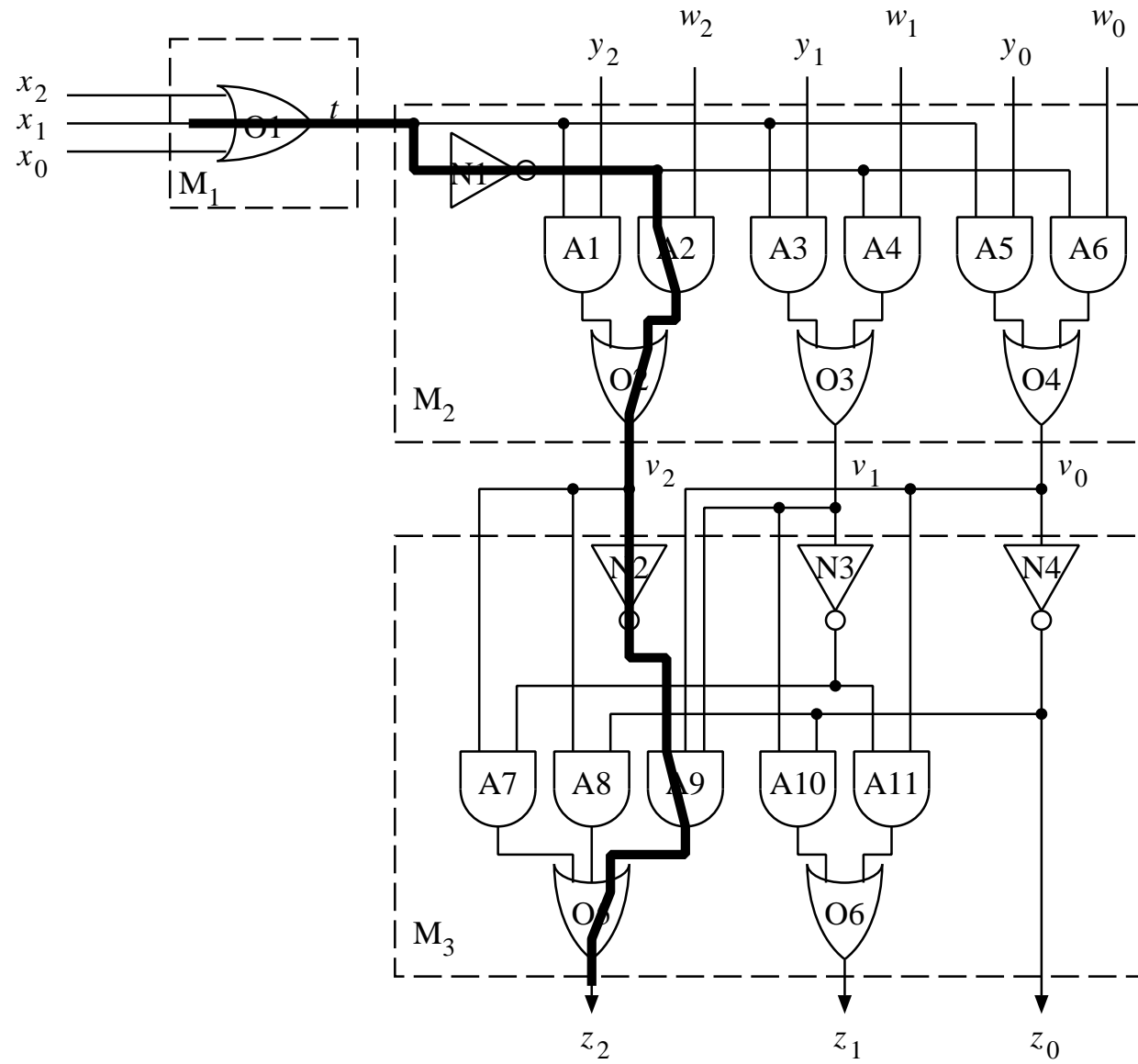


Figure 4.13: NETWORK FOR HIERARCHICAL ANALYSIS

## EXAMPLE (cont.)

---

**TYPES OF GATES USED:** 2-input AND, 3-input AND, etc.

**LOAD FACTORS:** NETWORK INPUTS: 1; GATE INPUTS: 1

**FANOUT FACTORS:**  $F = 12$  (assumed)

$$F(z_2) = F(z_1) = 12, \quad F(z_0) = 12 - 2 = 10$$

**NETWORK SIZE :** 38 [equiv. gates] 21 [actual]

**NUMBER OF LEVELS:** 7



# NETWORK DELAY Example of path delay calculation:

$$O_1 \rightarrow N_1 \rightarrow A_2 \rightarrow O_2 \rightarrow N_2 \rightarrow A_9 \rightarrow O_5$$

$$T_{pLH}(x_1, z_2) = t_{pLH}(O_1) + t_{pHL}(N_1) + t_{pHL}(A_2) + t_{pHL}(O_2) \\ + t_{pLH}(N_2) + t_{pLH}(A_9) + t_{pLH}(O_5)$$

$$T_{pHL}(x_1, z_2) = t_{pHL}(O_1) + t_{pLH}(N_1) + t_{pLH}(A_2) + t_{pLH}(O_2) \\ + t_{pHL}(N_2) + t_{pHL}(A_9) + t_{pHL}(O_5)$$

Gate	Identifier	Output load	$t_{pLH}$ [ns]	$t_{pHL}$ [ns]
OR3	$O_1$	4	0.27	0.43
NOT	$N_1$	3	0.13	0.10
AND2	$A_2$	1	0.19	0.18
OR2	$O_2$	3	0.23	0.26
NOT	$N_2$	1	0.06	0.07
AND3	$A_9$	1	0.24	0.20
OR3	$O_5$	$L$	$0.12 + 0.038L$	$0.34 + 0.022L$

$$T_{pLH}(x_1, z_2) = 0.27 + 0.10 + 0.18 + 0.26 + 0.06 \\ + 0.24 + 0.12 + 0.038L = 1.23 + 0.038L \text{ [ns]}$$

$$T_{pHL}(x_1, z_2) = 0.43 + 0.13 + 0.19 + 0.23 + 0.07 \\ + 0.20 + 0.34 + 0.022L = 1.59 + 0.022L \text{ [ns]}$$

# TIMING DIAGRAM

---

 


Figure 4.14: TIMING DIAGRAM FROM NETWORK ANALYSIS