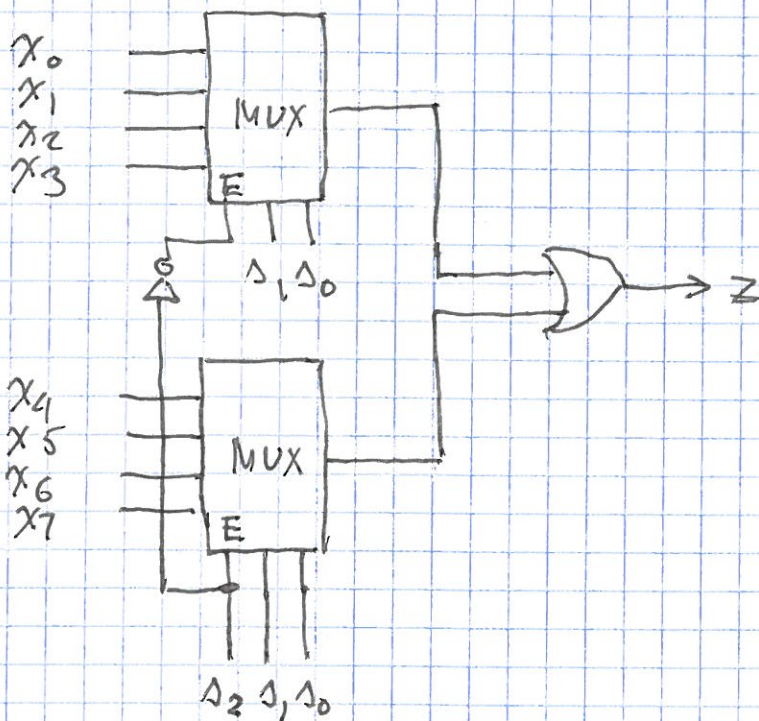


MULTIPLEXER NETWORKS: EXAMPLES

8-TO-1 MUX



64-TO-1 MUX (WITH DECODER + 8-1 MUXES WITH 3-STATE OUTPUTS)

