

- DESIGN OF TWO-LEVEL NETWORKS:  
**AND-OR** and **OR-AND** NETWORKS
- MINIMAL TWO-LEVEL NETWORKS  
KARNAUGH MAPS  
MINIMIZATION PROCEDURE AND TOOLS  
LIMITATIONS OF TWO-LEVEL NETWORKS
- DESIGN OF TWO-LEVEL **NAND-NAND** and  
**NOR-NOR** NETWORKS
- PROGRAMMABLE LOGIC: **PLAs** and **PALs**

## IMPLEMENTATION:

Level 1: NOT GATES (optional)

Level 2: AND GATES

Level 3: OR GATES

## LITERALS

(uncomplemented and complemented variables)

NOT GATES (IF NEEDED)

PRODUCTS: AND gates

SUM: OR gate

MULTIOUTPUT NETWORKS: ONE OR GATE USED FOR EACH OUTPUT

# PRODUCT OF SUMS NETWORKS - SIMILAR

3

# MODULO-64 INCREMENTER

---

Input:  $0 \leq x \leq 63$

Output:  $0 \leq z \leq 63$

Function:  $z = (x + 1) \bmod 64$

$$\begin{array}{c|c} x & 010101 \\ \hline z & 010110 \end{array} \quad \begin{array}{c|c} x & 001111 \\ \hline z & 010000 \end{array}$$

## ● RADIX-2 REPRESENTATION

$$z_i = \begin{cases} 1 & \text{if } (x_i = 1 \text{ and there exists } j < i \text{ such that } x_j = 0) \\ & \text{or } (x_i = 0 \text{ and } x_j = 1 \text{ for all } j < i) \\ 0 & \text{otherwise} \end{cases}$$

$$\begin{aligned} z_5 &= x_5(x'_4 + x'_3 + x'_2 + x'_1 + x'_0) + x'_5 x_4 x_3 x_2 x_1 x_0 \\ &= x_5 x'_4 + x_5 x'_3 + x_5 x'_2 + x_5 x'_1 + x_5 x'_0 + x'_5 x_4 x_3 x_2 x_1 x_0 \\ z_4 &= x_4 x'_3 + x_4 x'_2 + x_4 x'_1 + x_4 x'_0 + x'_4 x_3 x_2 x_1 x_0 \\ z_3 &= x_3 x'_2 + x_3 x'_1 + x_3 x'_0 + x'_3 x_2 x_1 x_0 \end{aligned}$$

$$z_2 = x_2x_1' + x_2x_0' + x_2'x_1x_0$$

$$z_1 = x_1x_0' + x_1'x_0$$

$$z_0 = x_0'$$

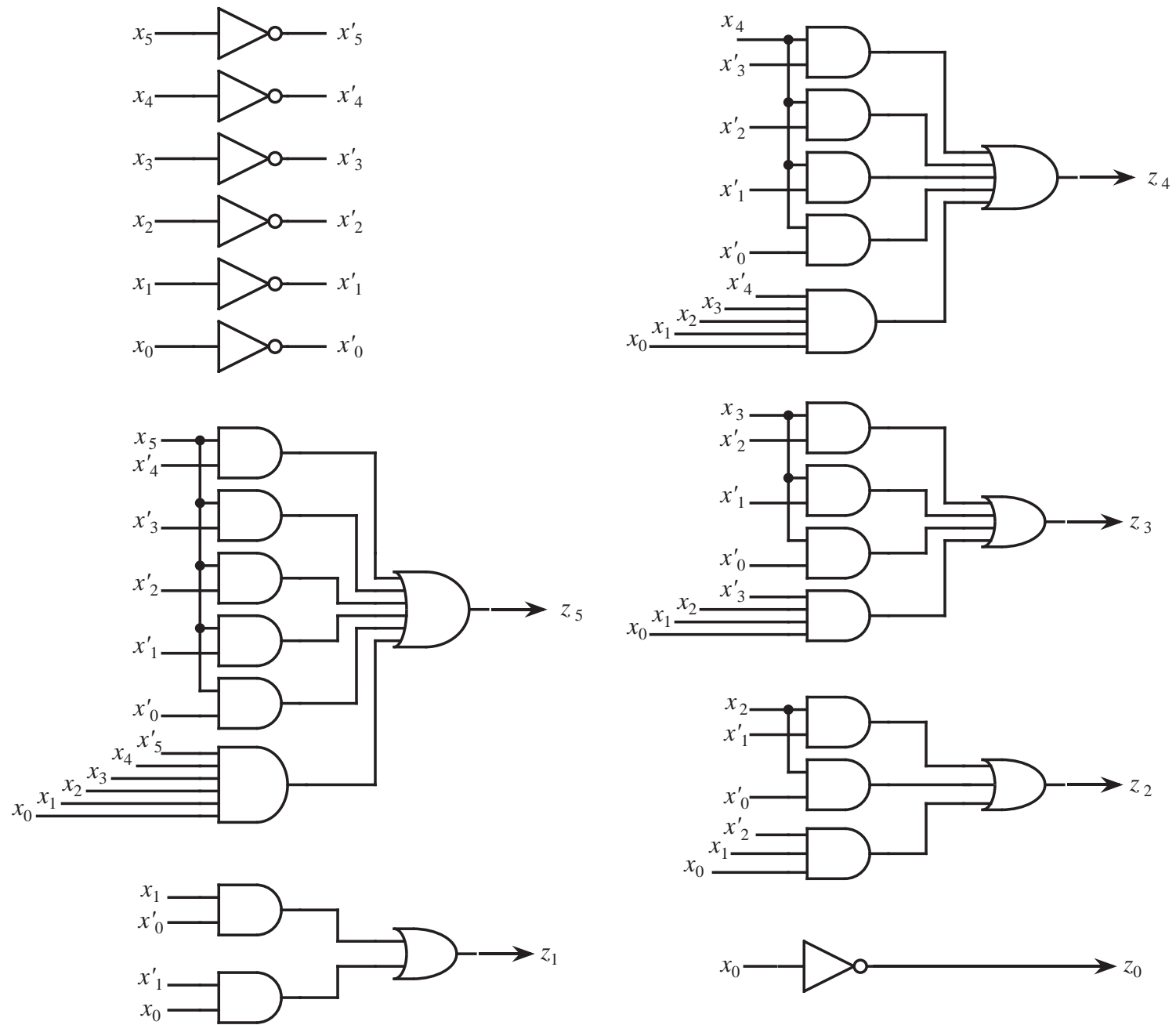


Figure 5.1: NOT-AND-OR MODULO-64 INCREMENTER NETWORK.

# UNCOMPLEMENTED AND COMPLEMENTED INPUTS AVAILABLE

---

7

- TWO TYPES OF TWO-LEVEL NETWORKS:

**AND-OR NETWORK**  $\Leftrightarrow$  SUM OF PRODUCTS (**SP**)  
easily transformed into **NAND-NAND NETWORK**

$$E(x_2, x_1, x_0) = x'_2 x'_1 x_0 + x_2 x_1 + x_1 x'_0$$

**OR-AND NETWORK**  $\Leftrightarrow$  PRODUCT OF SUMS (**PS**)  
(**NOR-NOR NETWORK**)

$$E(x_2, x_1, x_0) = (x'_2 + x_1)(x_1 + x'_0)(x_2 + x'_1 + x_0)$$


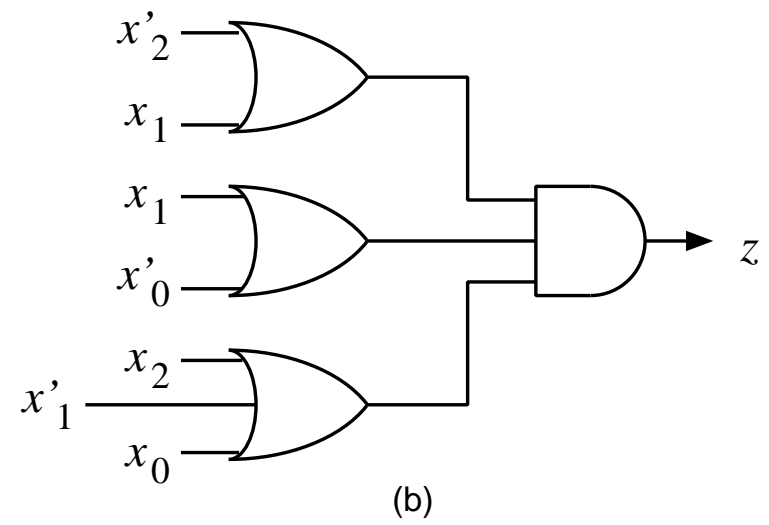


Figure 5.2: AND-OR and OR-AND NETWORKS.

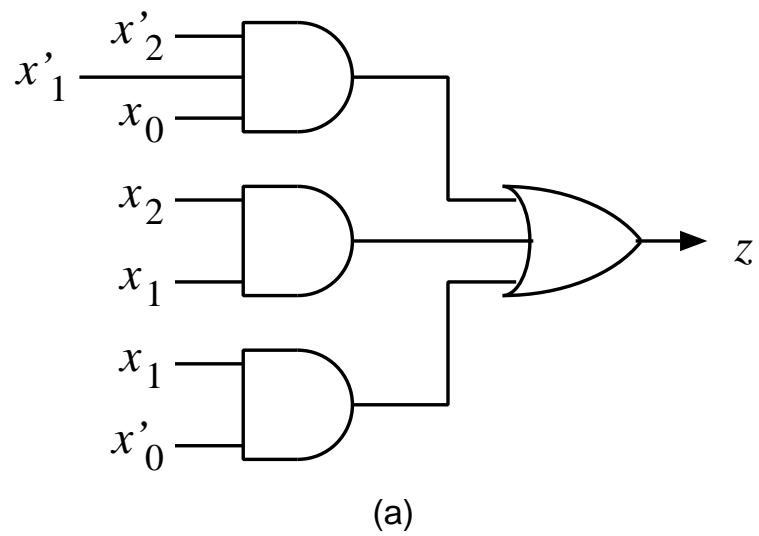

1. INPUTS: UNCOMPLEMENTED AND COMPLEMENTED

2. FANIN UNLIMITED

3. SINGLE-OUTPUT NETWORKS


4. MINIMAL NETWORK:

MINIMUM NUMBER OF GATES WITH MINIMUM NUMBER  
OF INPUTS


(minimal expression: min. number of terms with min. number  
of literals)

# NETWORKS WITH DIFFERENT COST

---

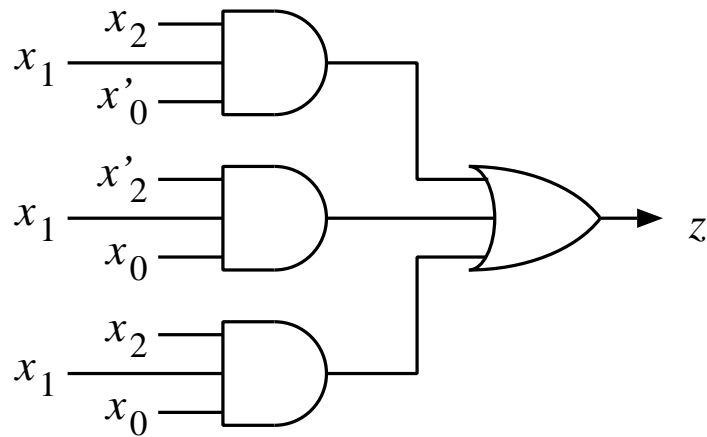

Network A

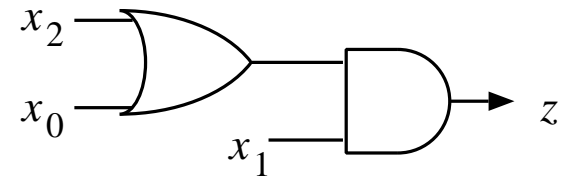

Network B

Figure 5.3: NETWORKS WITH DIFFERENT COST TO IMPLEMENT  $f(x_2, x_1, x_0) = \text{one-set}(3, 6, 7)$ .

- EQUIVALENT BUT DIFFERENT COST

$$E_1(x_2, x_1, x_0) = x'_2x_1x'_0 + x'_1x_0 + x_2x_0$$

$$E_2(x_2, x_1, x_0) = x_2x_1x_0 + x'_2x_1x'_0 + x'_2x'_1x_0 + x_2x'_1x_0$$

- BOTH MINIMAL SP AND PS MUST BE OBTAINED AND COMPARED
- BASIS:

$$ab + ab' = a \quad (\text{for sum of products})$$

$$(a + b)(a + b') = a \quad (\text{for product of sums})$$

# GRAPHICAL REPRESENTATION OF SWITCHING FUNCTIONS: KARNAUGH MAPS

---

- 2-DIMENSIONAL ARRAY OF CELLS
- $n$  VARIABLES  $\longrightarrow 2^n$  CELLS
- cell  $i \longleftrightarrow$  ASSIGNMENT  $i$

## *ADJACENCY CONDITION*

ANY SET OF  $2^r$  ADJACENT ROWS (COLUMNS):  
ASSIGNMENTS DIFFER IN  $r$  VARIABLES

- REPRESENTING SWITCHING FUNCTIONS
- REPRESENTING SWITCHING EXPRESSIONS
- GRAPHICAL AID IN SIMPLIFYING EXPRESSIONS

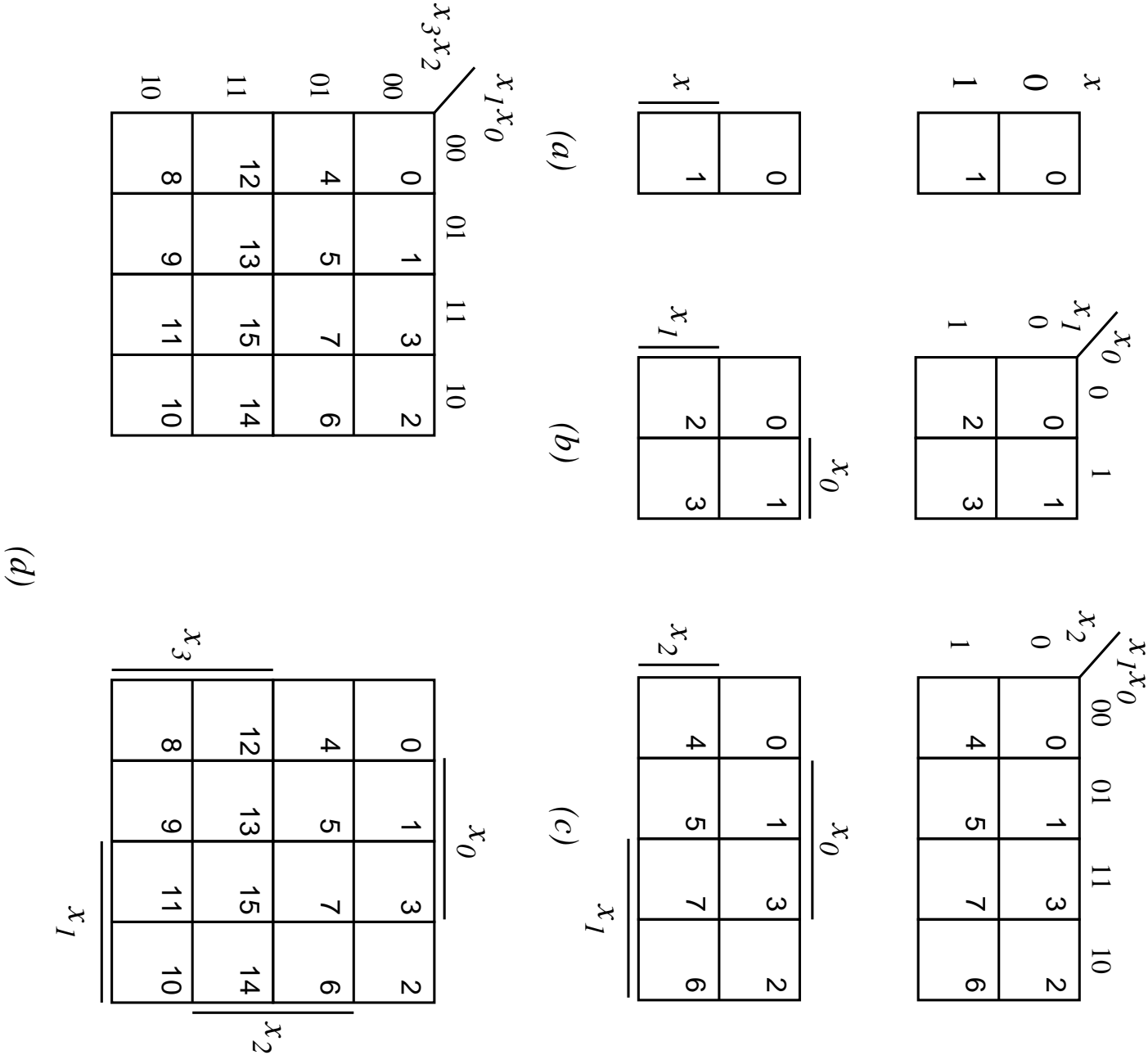


Figure 5.4: K-Maps

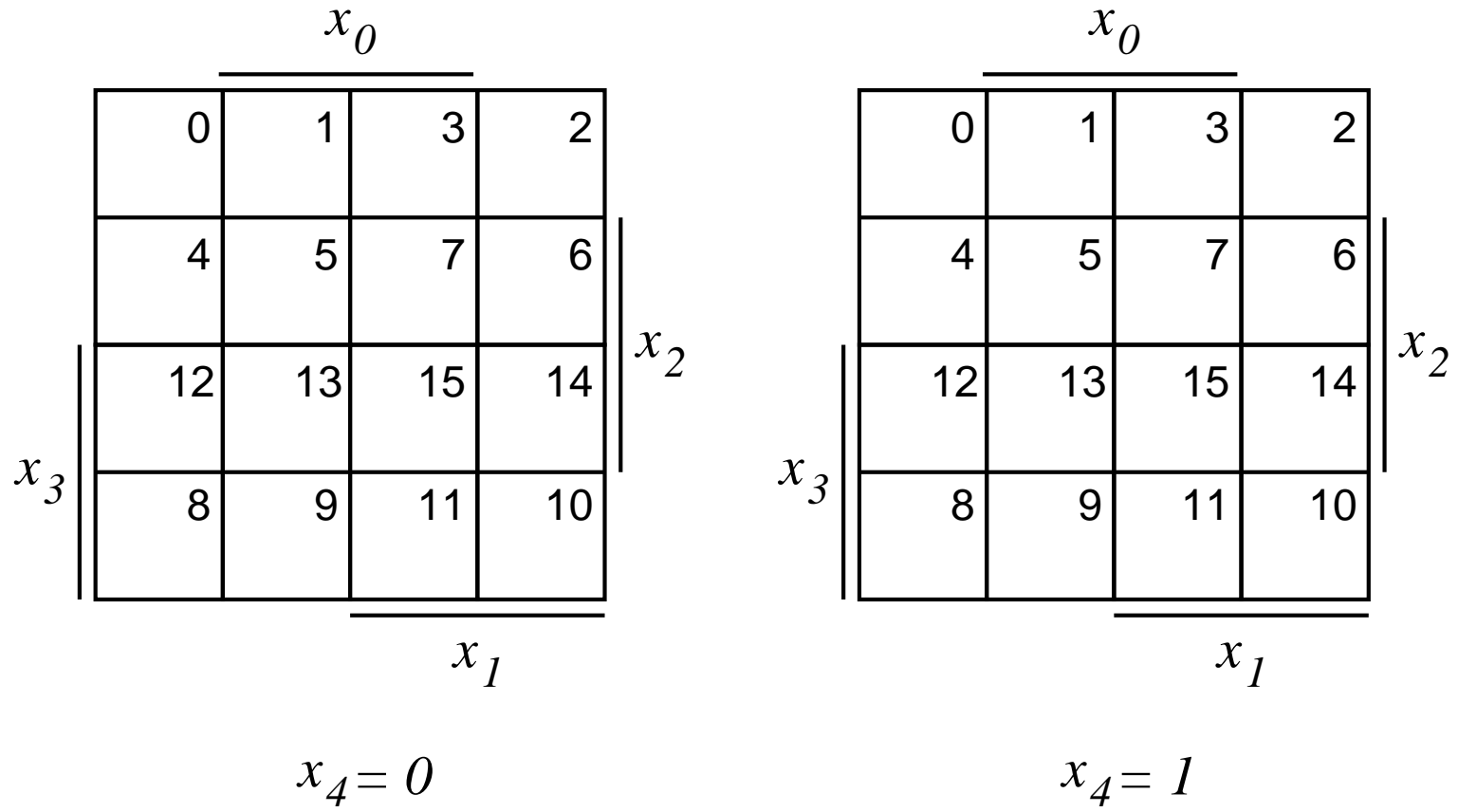


Figure 5.5: K-map FOR FIVE VARIABLES

# REPRESENTATION OF SWITCHING FUNCTIONS

---

15

$$f(x_2, x_1, x_0) = \text{one-set}(0, 2, 6)$$

	$x_0$			
	1	0	0	1
$x_2$	0	0	0	1
	$x_1$			

$$f(x_3, x_2, x_1, x_0) = \text{zero-set}(1, 3, 4, 6, 10, 11, 13)$$

		$x_0$			
		1	0	0	1
		0	1	1	0
$x_3$	1	0	1	1	1
	1	1	0	0	0
		$x_1$			
		$x_2$			

$$f(x_2, x_1, x_0) = [\text{one-set}(0, 4, 5), \quad \text{dc-set}(2, 3)]$$

	$x_0$			
	1	0	-	-
$x_2$	1	1	0	0
	$x_1$			

# RECTANGLES OF 1-CELLS AND SUM OF PRODUCTS

16

1. MINTERM  $m_j$  CORRESPONDS TO 1-CELL WITH LABEL  $j$ .
2. PRODUCT TERM OF  $n - 1$  LITERALS  $\longleftrightarrow$  RECTANGLE OF TWO ADJACENT 1-CELLS

$$\begin{aligned}
 x_3 x_1' x_0 &= x_3 x_1' x_0 (x_2 + x_2') \\
 &= x_3 x_2 x_1' x_0 + x_3 x_2' x_1' x_0 \\
 &= m_{13} + m_9
 \end{aligned}$$

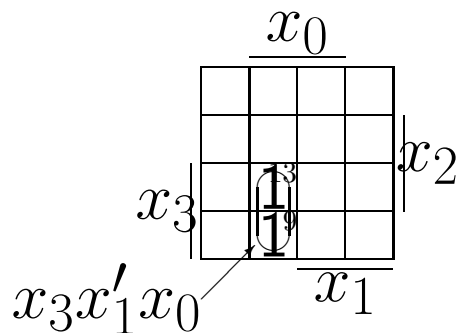


Figure 5.6



# RECTANGLES OF 1-CELLS AND SUM OF PRODUCTS (cont.)<sup>17</sup>

---

## 3. PRODUCT TERM OF $n - 2$ LITERALS $\longleftrightarrow$ RECTANGLE OF FOUR ADJACENT 1-CELLS

$$\begin{aligned}
 x_3x_0 &= x_3x_0(x_1 + x'_1)(x_2 + x'_2) \\
 &= x_3x'_2x'_1x_0 + x_3x'_2x_1x_0 + x_3x_2x'_1x_0 + x_3x_2x_1x_0 \\
 &= m_9 + m_{11} + m_{13} + m_{15}
 \end{aligned}$$

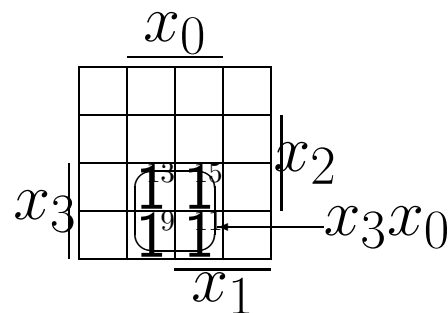


Figure 5.6

## 4. PRODUCT TERM OF $n - s$ LITERALS $\longleftrightarrow$ RECTANGLE OF $2^s$ ADJACENT 1-CELLS

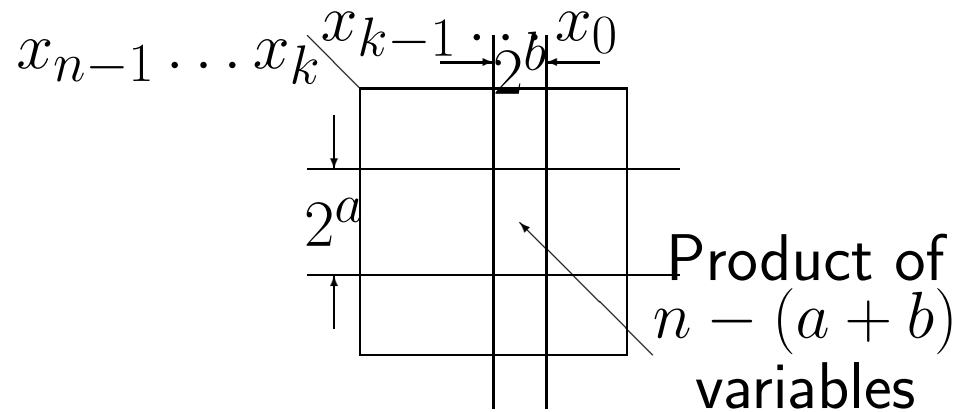
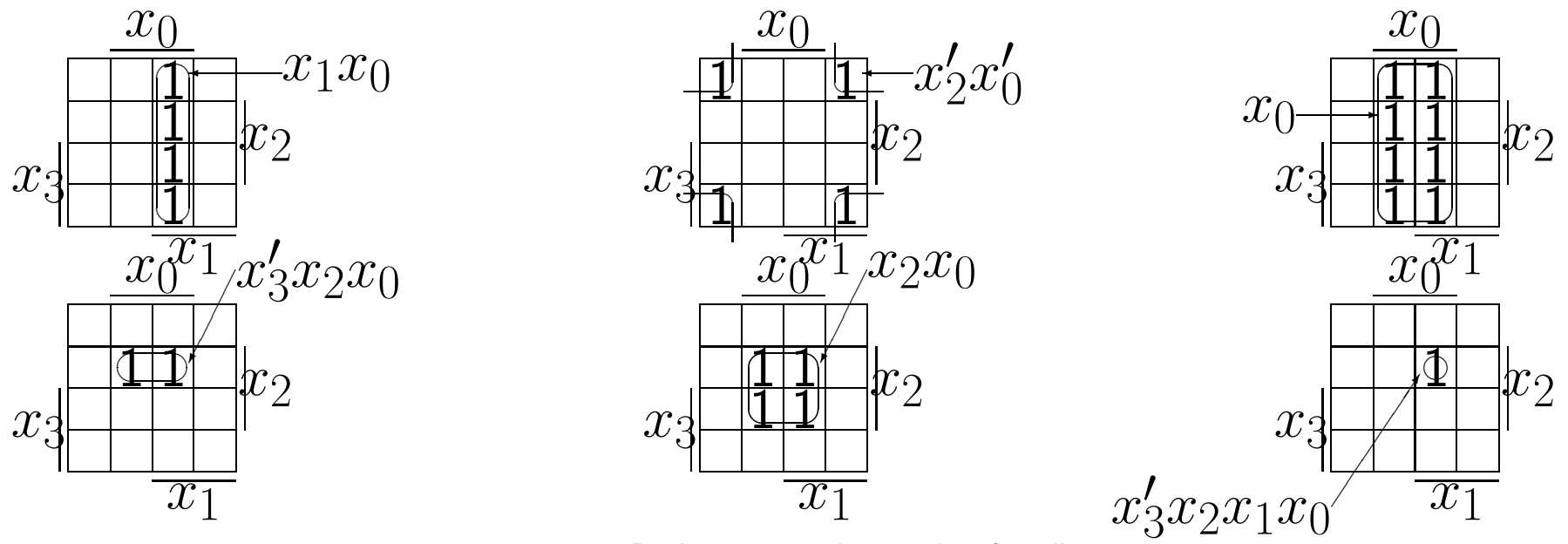
Figure 5.7: Representation of product of  $n - (a + b)$  variables.

Figure 5.8: Product terms and rectangles of 1-cells.

## SUM OF PRODUCTS

represented in a K-map by the union of rectangles

$$E(x_3, x_2, x_1, x_0) = x'_3 x_2 x_1 + x'_2 x_1 x_0 + x'_0$$

$$E(a, b, c) = ab + ac + b'c'$$

$$a \mid \begin{array}{|c|c|c|c|} \hline \textcircled{1} & \textcircled{0} & \textcircled{0} & \textcircled{0} \\ \hline \textcircled{1} & \textcircled{1} & \textcircled{1} & \textcircled{1} \\ \hline \end{array} \begin{array}{c} \overline{c} \\ \overline{b} \end{array}$$

# RECTANGLES OF 0-CELLS AND PRODUCT OF SUMS

---

20

0-cell 13 CORRESPONDS TO THE MAXTERM

$$M_{13} = x'_3 + x'_2 + x_1 + x'_0$$

RECTANGLE OF  $2^a \times 2^b$  0-cells  $\longleftrightarrow$  SUM TERM OF  $n - (a + b)$   
LITERALS

**IMPLICANT:** PRODUCT TERM FOR WHICH  $f=1$

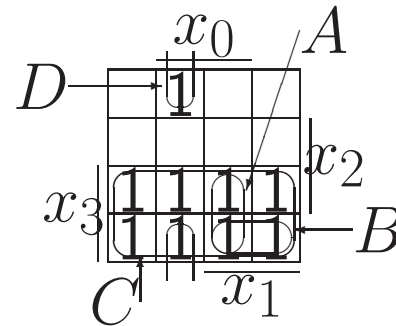


Figure 5.9: Implicant representation.

IMPLICANTS:  $x'_3x'_2x'_1x_0$ , ALL PRODUCT TERMS WITH  $x_3$

**PRIME IMPLICANT:** IMPLICANT NOT COVERED BY ANOTHER IMPLICANT

PRIME IMPLICANTS:  $x'_2x'_1x_0$ ,  $x_3$

# FIND ALL Pls

---

a)  $f(x_2, x_1, x_0) = \text{one-set}(2,4,6)$

	$x_0$			
	0	0	0	1
$x_2$	1	0	0	1
	$x_1$			

Pls:  $x_2x'_0$  and  $x_1x'_0$

b)  $f(x_2, x_1, x_0) = \text{one-set}(0,1,5,7)$

	$x_0$			
	1	1	0	0
$x_2$	0	1	1	0
	$x_1$			

Pls:  $x'_2x'_1$ ,  $x_2x_0$ , and  $x'_1x_0$

c)  $f(x_3, x_2, x_1, x_0) = \text{one-set}(0,3,5,7,11,12,13,15)$

		$x_0$				
		1	0	1	0	
		0	1	1	0	
$x_3$		1	1	1	0	$x_2$
		0	0	1	0	
		$x_1$				

Pls:  $x_2x_0$ ,  $x_1x_0$ ,  $x_3x_2x'_1$ , and  $x'_3x'_2x'_1x'_0$

# MINIMAL SUM OF PRODUCTS CONSISTS OF PRIME IMPLICANTS

---

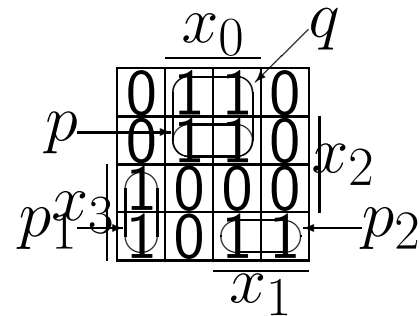



Figure 5.10: MINIMAL SUM OF PRODUCTS AND PRIME IMPLICANTS.


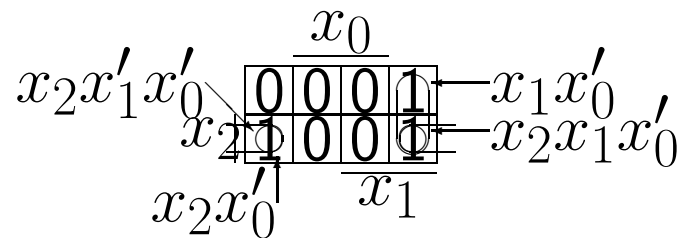
## Example 5.9

---

$$E(x_2, x_1, x_0) = x_2x'_1x'_0 + x_2x_1x'_0 + x_1x'_0$$



not PIs:  $x_2x'_1x'_0$  and  $x_2x_1x'_0$

PI:  $x_2x'_0$ ,  $x_1x'_0$

REDUCED SP:  $E(x_2, x_1, x_0) = x_2x'_0 + x_1x'_0$

# ESSENTIAL PRIME IMPLICANTS (EPI)

---

$p_e(\underline{a}) = 1$  and  $p(\underline{a}) = 0$  FOR ANY OTHER PI  $p$

	$x_0$			
$x_2$	1		1	
	1		0	1
	1		0	1
	$x_1$			

EPIs:  $x_1'x_0'$  and  $x_1x_0$

NON-ESSENTIAL:  $x_2x_1$ ,  $x_2x_0'$ .

- ALL EPIs ARE INCLUDED IN A MINIMAL SP

## PROCEDURE FOR FINDING MIN SP


---

1. DETERMINE ALL PIs
2. OBTAIN THE EPIs
3. IF NOT ALL 1-CELLS COVERED, CHOOSE A COVER FROM THE REMAINING PIs

## EXAMPLE 5.10

FIND A MINIMAL SP:

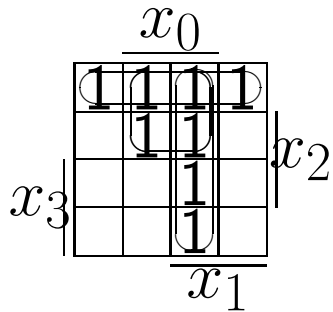a)  $E(x_3, x_2, x_1, x_0) = x'_3x'_2 + x'_3x_2x_0 + x_1x_0$



- Pls:  $x'_3x'_2$ ,  $x'_3x_0$ , and  $x_1x_0$
- ALL EPIs
- UNIQUE MIN SP:  $x'_3x'_2 + x'_3x_0 + x_1x_0$

b)  $E(x_2, x_1, x_0) = \Sigma m(0, 3, 4, 6, 7)$

	$x_0$	
$x_2$	1	1
	1	1
$x_1$	1	1
	1	1

- Pls:  $x'_1x'_0$ ,  $x_1x_0$ ,  $x_2x'_0$ , and  $x_2x_1$
- EPIs:  $x'_1x'_0$  and  $x_1x_0$
- EXTRA COVER:  $x_2x'_0$  or  $x_2x_1$
- TWO MIN SPs:

$$x'_1x'_0 + x_1x_0 + x_2x'_0 \quad \text{and} \quad x'_1x'_0 + x_1x_0 + x_2x_1$$

c)  $E(x_2, x_1, x_0) = \sum m(0, 1, 2, 5, 6, 7)$

	$x_0$			
$x_2$	1	1		1
		1	1	1
	$x_1$			

- Pls:  $x'_2x'_1$ ,  $x'_2x'_0$ ,  $x_2x_0$ ,  $x_2x_1$ ,  $x'_1x_0$ , and  $x_1x'_0$
- No EPIs
- TWO MIN SPs

$$x'_2x'_1 + x_2x_0 + x_1x'_0 \quad \text{and} \quad x'_2x'_0 + x'_1x_0 + x_2x_1$$

# MINIMAL SPs FOR INCOMPLETELY SPECIFIED FUNCTIONS<sup>31</sup>

---

		$x_0$				
		1	1	1	0	
		0	-	1	0	
$x_3$	1	-	0	-		$x_2$
	1	0	-	-		
		$x_1$				

A minimal SP

$$E(x_3, x_2, x_1, x_0) = x_3x'_0 + x'_3x_0 + x'_3x'_2x'_1$$

# MINIMIZATION OF PRODUCTS OF SUMS

---

**IMPLICATE:** SUM TERM FOR WHICH  $f = 0$ .

**PRIME IMPPLICATE:** IMPLICATE NOT COVERED BY AN-OTHER IMPPLICATE

**ESSENTIAL PRIME IMPPLICATE:** AT LEAST ONE "CELL" NOT INCLUDED IN OTHER IMPPLICATE

$$f(x_3, x_2, x_1, x_0) = \text{zero-set}(7, 13, 15)$$

		$x_0$				
		1	1	1	1	
		1	1	0	1	
		1	0	0	1	
		1	1	1	1	
		$x_1$				
$x_3$						$x_2$

THE PRIME IMPPLICATES:  $(x'_3 + x'_2 + x'_0)$  and  $(x'_2 + x'_1 + x'_0)$

BOTH ESSENTIAL



## PROCEDURE FOR FINDING MIN PS

---

1. DETERMINE ALL PRIME IMPLICATES
2. DETERMINE THE ESSENTIAL PRIME IMPLICATES
3. FROM SET OF NONESSENTIAL PRIME IMPLICATES, SELECT COVER OF REMAINING 0-CELLS

	$x_0$				
	1	1	1	0	
	1	0	0	1	
	1	0	0	1	$x_2$
$x_3$	1	1	1	1	
	$x_1$				

- THE PRIME IMPLICATES:  $(x'_0 + x'_2)$  and  $(x_0 + x_2 + x'_1)$
- BOTH ESSENTIAL, THE MINIMAL PS IS  $(x'_0 + x'_2)(x_0 + x_2 + x'_1)$

# MINIMAL TWO-LEVEL GATE NETWORK DESIGN: EXAMPLE<sup>34</sup>

## 5.14

Input:  $x \in \{0, 1, 2, \dots, 9\}$ , coded in BCD as

$$\underline{x} = (x_3, x_2, x_1, x_0), \quad x_i \in \{0, 1\}$$

Output:  $z \in \{0, 1\}$

Function:  $z = \begin{cases} 1 & \text{if } x \in \{0, 2, 3, 5, 8\} \\ 0 & \text{otherwise} \end{cases}$

THE VALUES  $\{10,11,12,13,14,15\}$  ARE “DON'T CARES”

MIN SP:  $z = x_2'x_1 + x_2'x_0 + x_2x_1'x_0$

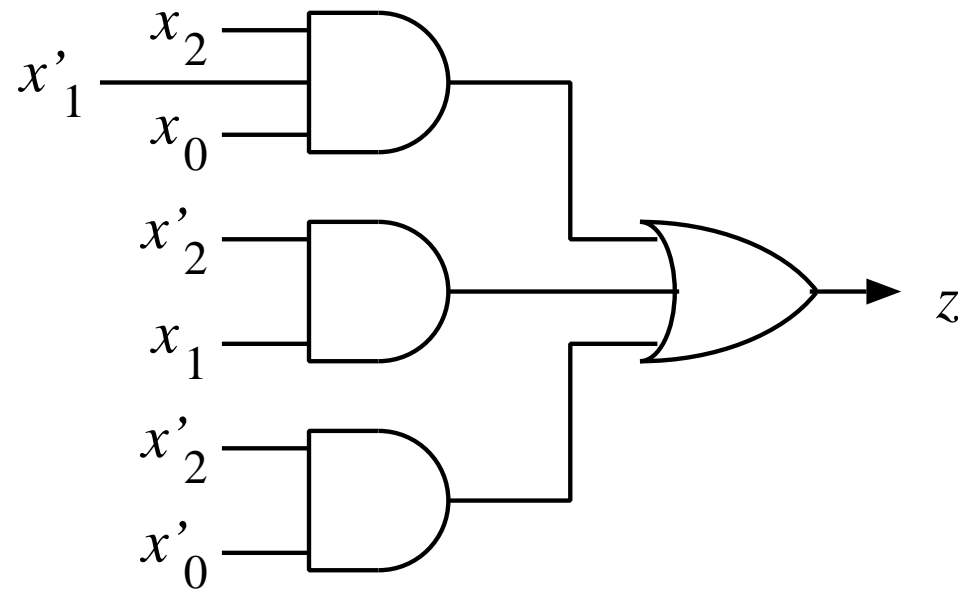


Figure 5.11: MINIMAL AND-OR NETWORK

MIN PS:  $z = (x'_2 + x'_1)(x'_2 + x_0)(x_2 + x_1 + x'_0)$

Input:  $x \in \{0, 1, 2, \dots, 15\}$   
 represented in binary code by  $\underline{x} = (x_3, x_2, x_1, x_0)$   
 Output:  $z \in \{0, 1\}$

Function:  $z = \begin{cases} 1 & \text{if } x \in \{0, 1, 3, 5, 7, 11, 12, 13, 14\} \\ 0 & \text{otherwise} \end{cases}$

## THE K-MAP:

$$\text{min SP: } z = x'_3x_0 + x'_3x'_2x'_1 + x_2x'_1x_0 + x_3x_2x'_0 + x'_2x_1x_0$$

$$\text{min PS: } z = (x'_3 + x_2 + x_1)(x_3 + x'_2 + x_0)(x_2 + x'_1 + x_0)(x'_3 + x'_2 + x'_1 + x'_0)$$

$$\text{COST}(\text{PS}) < \text{COST}(\text{SP})$$

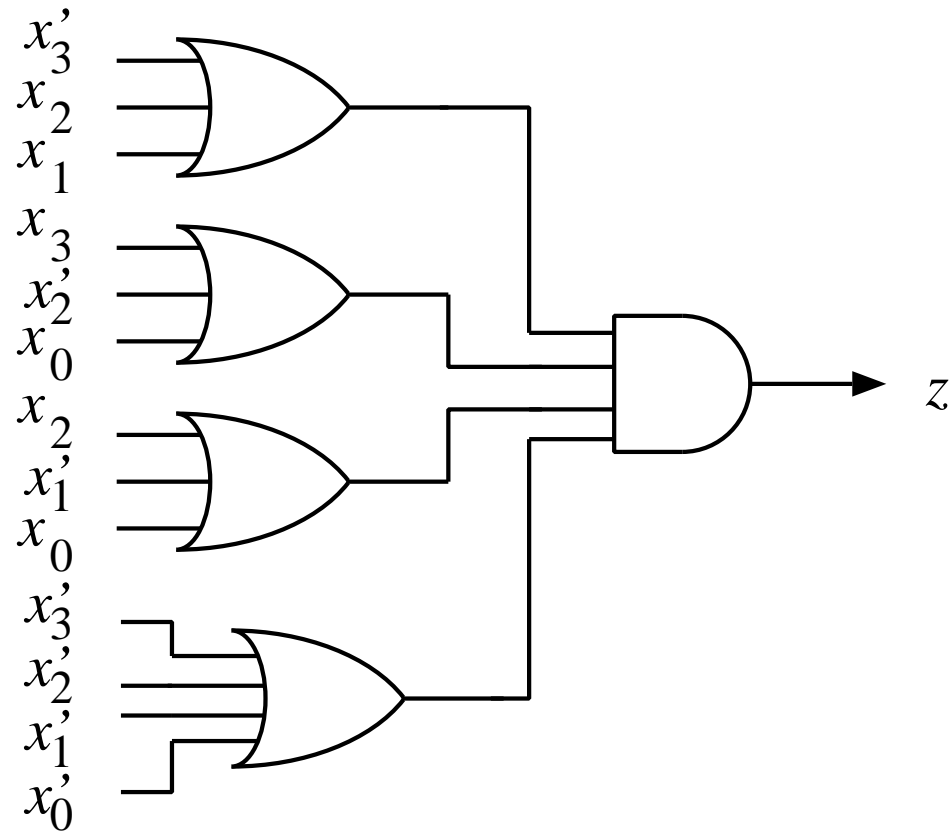


Figure 5.12: MINIMAL OR-AND NETWORK

# QUINE-McCLUSKEY TABULAR METHOD

---

- Intended for minimizing s-expressions of more than 4 variables
- Suitable for computer-based methods
- Part 1: Determine the prime implicants (prime implicates) of the function. Use  $Xy + Xy' = X$  (or  $(X+y)(X+y') = X$  for min POS)
- Part 2: Select a set of prime implicants (prime implicates) that covers the function and has the minimum cost: construct PI chart
- The number of prime implicants is usually very large: obtaining a minimum cover is time-consuming

## TABULAR FINDING OF PRIME IMPLICANTS

---

- Given a function  $f$  of  $n$  variables, determine the prime implicants
- **Column 1:** list all the minterms according to the number of 1's in the binary representation
- **Column 2:** list implicants with  $n - 1$  literals by pairing elements of Column 1 that differ in the value of one variable; mark the variable in which they differ with "-". Mark elements of Column 1 which form such a pair with  $N$  ("Not prime implicants")  
1011 and 1001 produce 10-1
- **Column 3:** list implicants with  $n - 2$  literals by pairing elements of Column 2 which have "-" in the same position and differ only in one variable. Mark as above.  
10-1 and 00-1 produce -0-1
- **Continue** this process until no more elements can be paired

- The prime implicants are elements not marked with  $N$



$$\text{EXAMPLE : } f(x_4, \dots, x_0) = \sum m(1, 3, 4, 6, 9, 11, 12, 14, 16, 18, 21, 23, 24, 26, 29, 31)$$

---

Minterms	4-literal prods	3-literal prods
00001 N	000-1 N	0-0-1
00100 N	0-001 N	0-1-0
10000 N	001-0 N	1-0-0
	0-100 N	
00011 N	100-0 N	1-1-1
00110 N	1-000 N	
01001 N		
01100 N	0-011 N	
10010 N	0-110 N	
11000 N	010-1 N	
	011-0 N	
01011 N	1-010 N	
01110 N	110-0 N	
10101 N		
11010 N	101-1 N	
	1-101 N	
10111 N		
11101 N	1-111 N	

# PRIME IMPLICANT CHART

---

	1	3	4	6	9	11	12	14	16	18	21	23	24	26	29	31	Essential Prime
0-0-1	x	x				x	x										●
0-1-0			x	x				x	x								●
1-0-0									x	x				x	x		●
1-1-1											x	x			x	x	●

$$f(x_4, \dots, x_0) = x'_4 x'_2 x_0 + x'_4 x_2 x'_0 + x_4 x'_2 x'_0 + x_4 x_2 x_0$$

# DESIGN OF MULTIPLE-OUTPUT TWO-LEVEL GATE NETWORKS

---

- SEPARATE NETWORK FOR EACH OUTPUT: NO SHARING
- EXAMPLE 5.16

Inputs:  $(x_2, x_1, x_0), \quad x_i \in \{0, 1\}$

Output:  $z \in \{0, 1, 2, 3\}$

Function:  $z = \sum_{i=0}^2 x_i$

# 1. THE SWITCHING FUNCTIONS IN TABULAR FORM ARE

45

$x_2$	$x_1$	$x_0$	$z_1$	$z_0$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

## EXAMPLE 5.16 (cont.)

---

2. THE CORRESPONDING K-MAPS ARE

$$\begin{array}{c}
 z_1 \\
 \begin{array}{cc} & x_0 \\ \hline x_2 & \begin{array}{|c|c|c|c|} \hline 0 & 0 & 1 & 0 \\ \hline 0 & 1 & 1 & 1 \\ \hline \end{array} \\ & x_1 \\ \hline
 \end{array}
 \end{array}$$

$$\begin{array}{c}
 z_0 \\
 \begin{array}{cc} & x_0 \\ \hline x_2 & \begin{array}{|c|c|c|c|} \hline 0 & 1 & 0 & 1 \\ \hline 1 & 0 & 1 & 0 \\ \hline \end{array} \\ & x_1 \\ \hline
 \end{array}
 \end{array}$$

3. MINIMAL SPs:

$$z_1 = x_2x_1 + x_2x_0 + x_1x_0$$

$$z_0 = x_2'x_1'x_0 + x_2'x_1x_0' + x_2x_1'x_0' + x_2x_1x_0$$

4. MINIMAL PSs:

$$z_1 = (x_2 + x_0)(x_2 + x_1)(x_1 + x_0)$$

$$\begin{aligned}
 z_0 = & (x_2 + x_1 + x_0)(x_2 + x_1' + x_0') \\
 & (x_2' + x_1 + x_0')(x_2' + x_1' + x_0)
 \end{aligned}$$

5. SP AND PS EXPRESSIONS HAVE THE SAME COST

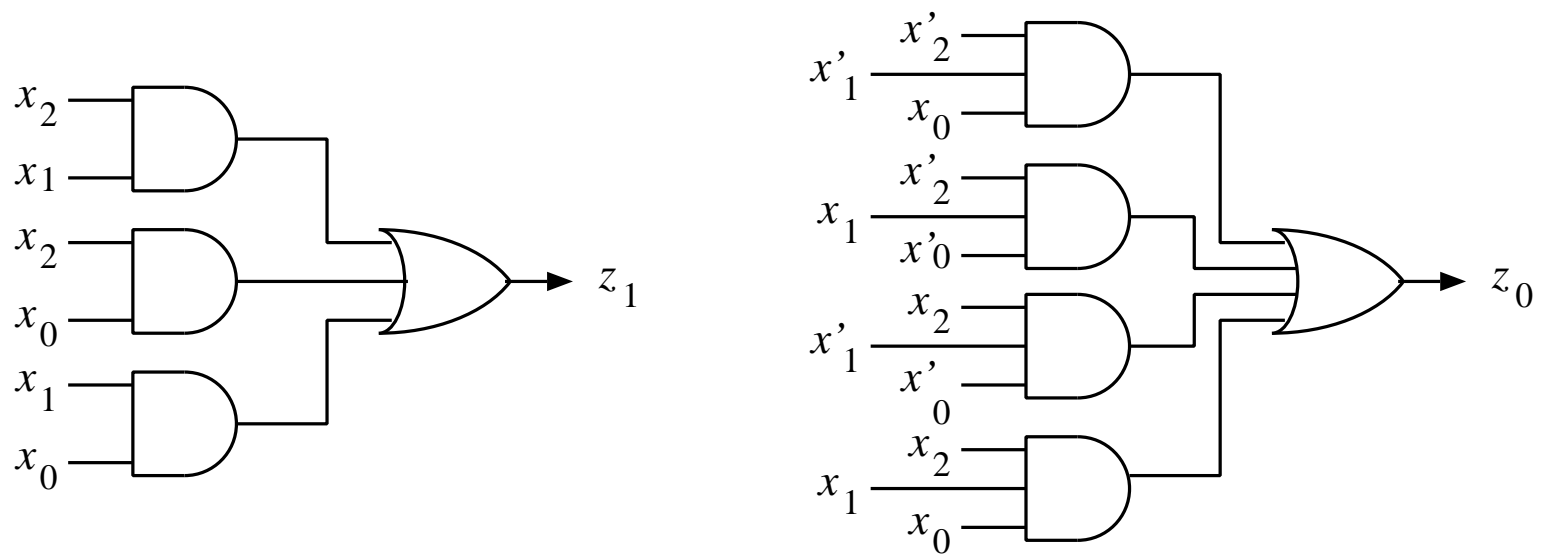


Figure 5.13: MINIMAL TWO-OUTPUT AND-OR NETWORK

$$E = p_1 + p_2 + p_3 + \dots + p_n$$

$p_1, p_2, \dots$  ARE PRODUCT TERMS

$$E = (p'_1 \cdot p'_2 \cdot p'_3 \dots p'_n)'$$

or

$$E = \text{NAND}(\text{NAND}_1, \text{NAND}_2, \text{NAND}_3, \dots, \text{NAND}_n)$$



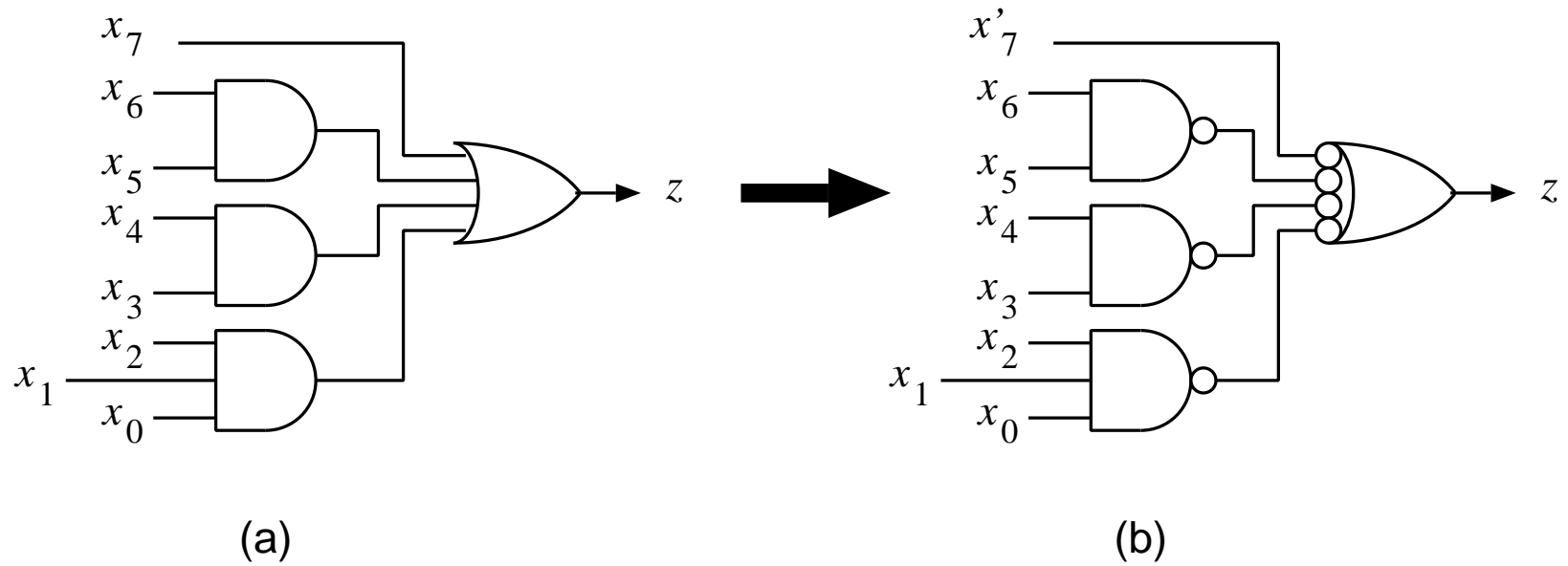


Figure 5.15: TRANSFORMATION OF AND-OR NETWORK INTO NAND-NAND NETWORK

# EXAMPLE: NOR NETWORK

$$z = x'_5(x_4 + x'_3)(x_2 + x_1 + x_0)$$

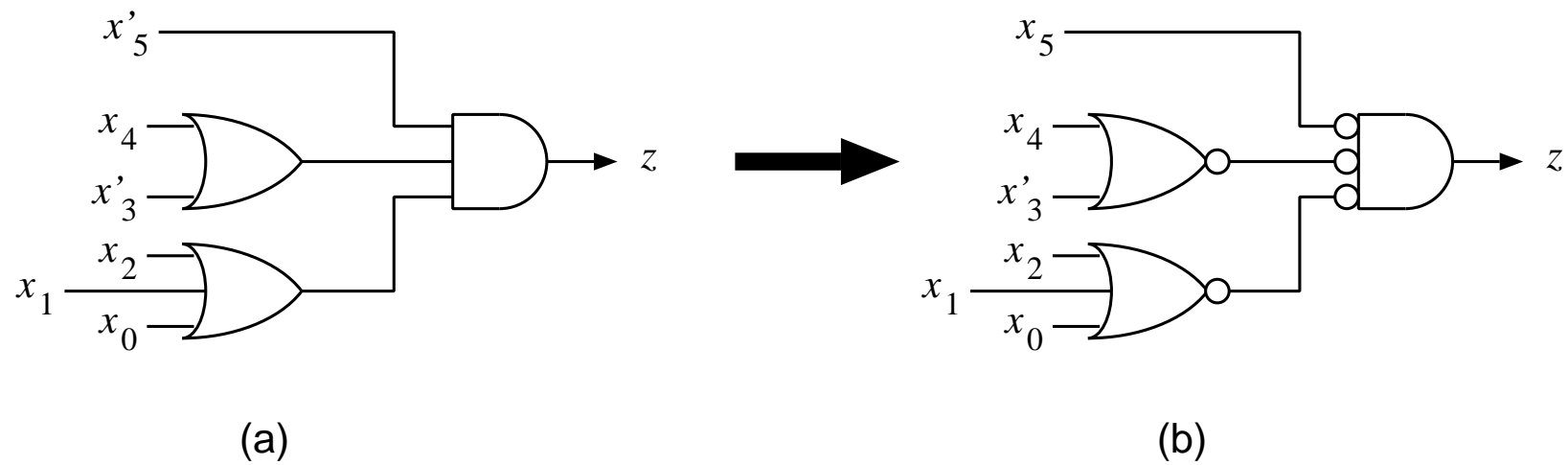


Figure 5.16: EQUIVALENT OR-AND AND NOR-NOR NETWORKS

## LIMITATIONS OF TWO-LEVEL NETWORKS

---

1. THE REQUIREMENT OF UNCOMPLEMENTED AND COMPLEMENTED INPUTS

IF NOT SATISFIED, AN ADDITIONAL LEVEL OF <sub>NOT</sub> GATES NEEDED

2. A TWO-LEVEL IMPLEMENTATION OF A FUNCTION MIGHT REQUIRE A LARGE NUMBER OF GATES AND IRREGULAR CONNECTIONS

3. EXISTING TECHNOLOGIES HAVE LIMITATIONS IN THE FAN-IN OF THE GATES


4. THE PROCEDURE ESSENTIALLY LIMITED TO THE SINGLE-OUTPUT CASE

## 5. THE COST CRITERION OF MINIMIZING THE NUMBER OF GATES IS NOT ADEQUATE FOR MANY MSI/LSI/VLSI DESIGNS
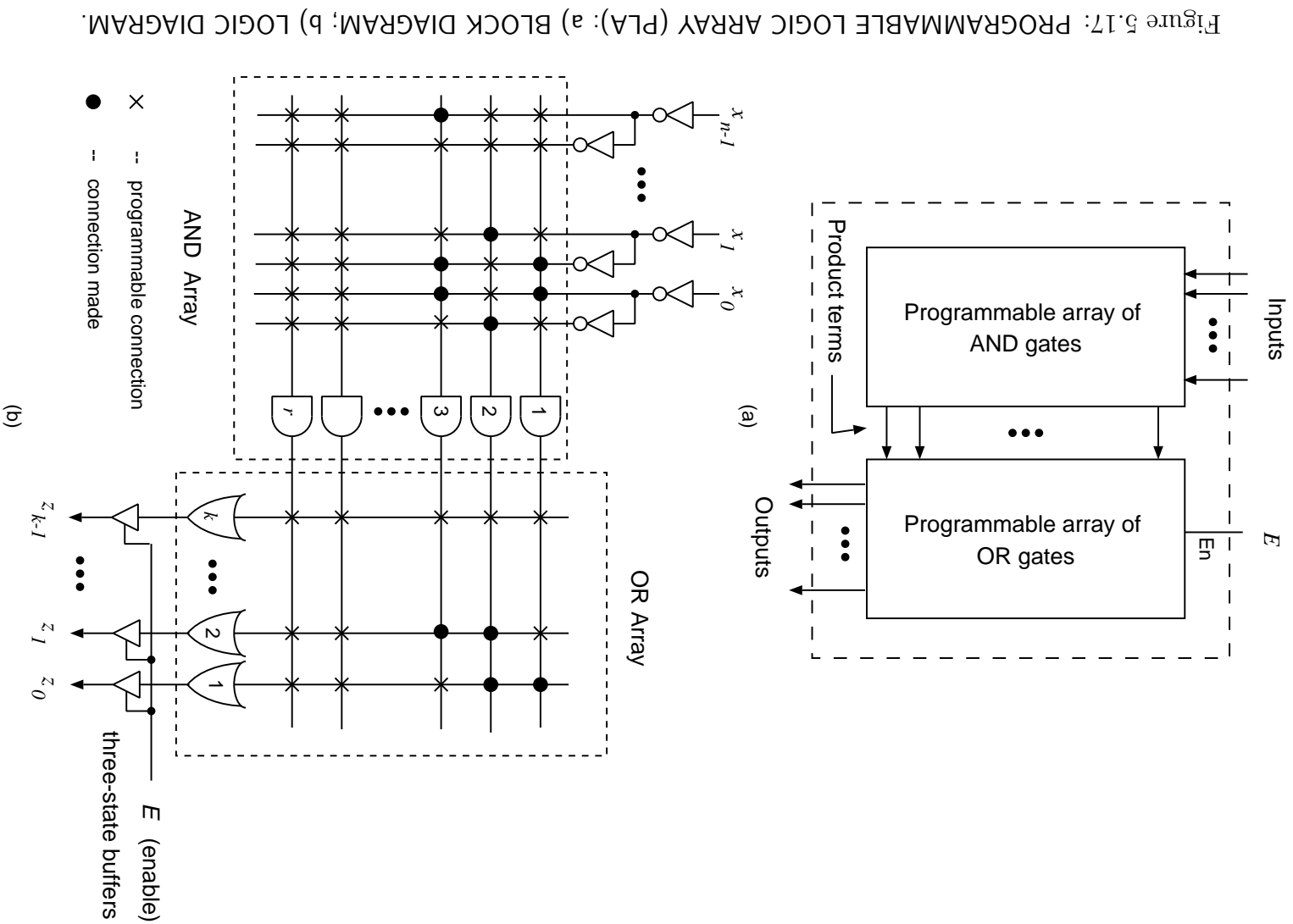
# PROGRAMMABLE MODULES: PLAs and PALs

---

- STANDARD (FIXED) STRUCTURE
- CUSTOMIZED (PROGRAMMED) FOR A PARTICULAR FUNCTION
  - DURING THE LAST STAGE OF FABRICATION
  - WHEN INCORPORATED INTO A SYSTEM
- FLEXIBLE USE
- MORE EXPENSIVE AND SLOWER THAN FIXED-FUNCTION MODULES
- OTHER TYPES DISCUSSED IN Chapter 12



# MOS PLA (OR-AND VERSION)

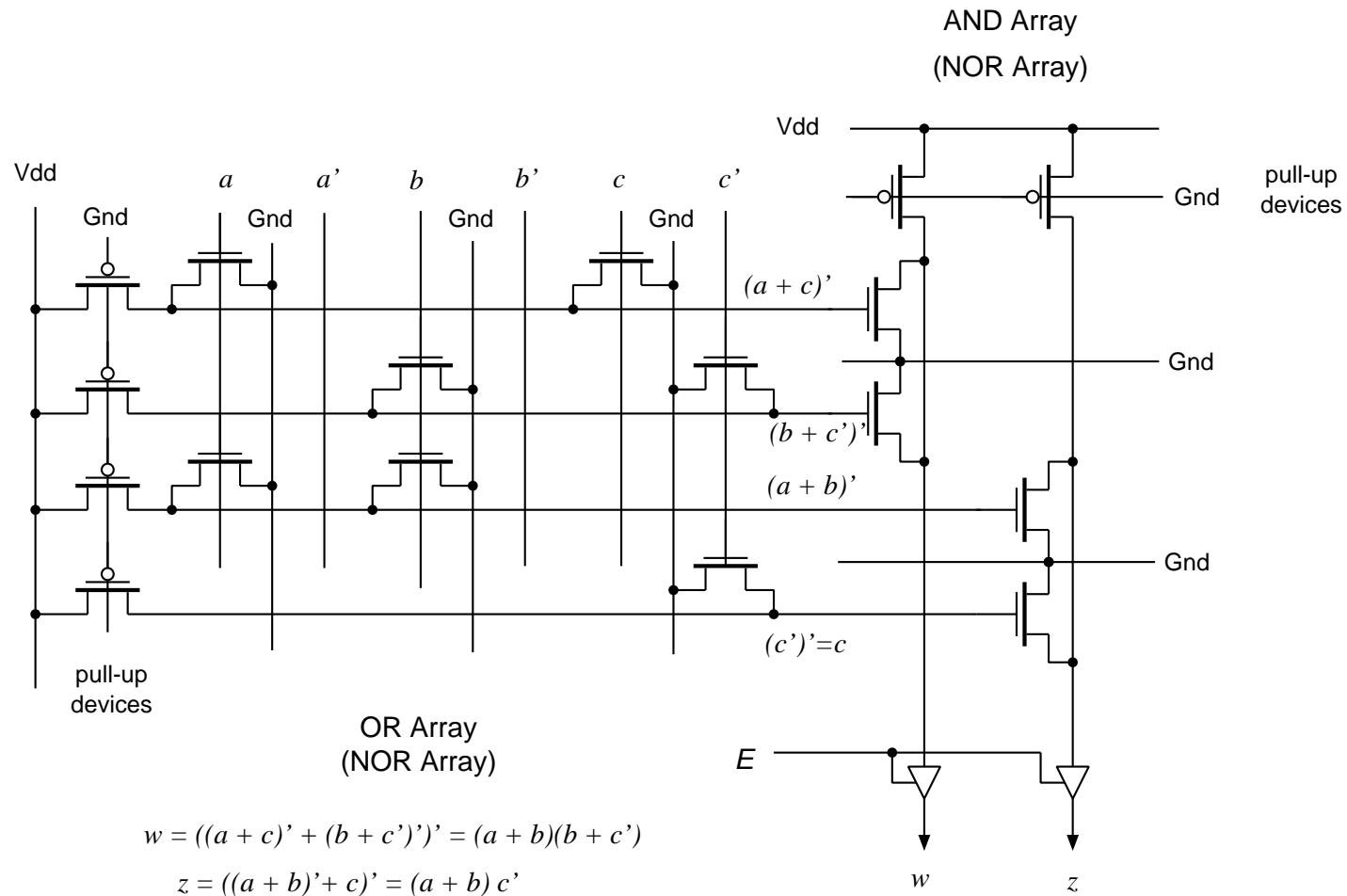


Figure 5.18: EXAMPLE OF PLA IMPLEMENTATION AT THE CIRCUIT LEVEL: FRAGMENT OF A MOS PLA .

# IMPLEMENTATION OF SWITCHING FUNCTIONS USING PLAs

---

## A BCD-to-Gray CONVERTER

Inputs:  $\underline{d} = (d_3, d_2, d_1, d_0), \quad d_j \in \{0, 1\}$

Outputs:  $\underline{g} = (g_3, g_2, g_1, g_0), \quad g_j \in \{0, 1\}$

Function:

$i$	$d_3d_2d_1d_0$	$g_3g_2g_1g_0$
0	0000	0000
1	0001	0001
2	0010	0011
3	0011	0010
4	0100	0110
5	0101	0111
6	0110	0101
7	0111	0100
8	1000	1100
9	1001	1101

EXPRESSIONS:


$$g_3 = d_3$$

$$g_2 = d_3 + d_2$$

$$g_1 = d_2' d_1 + d_2 d_1'$$

$$g_0 = d_1 d_0' + d_1' d_0$$



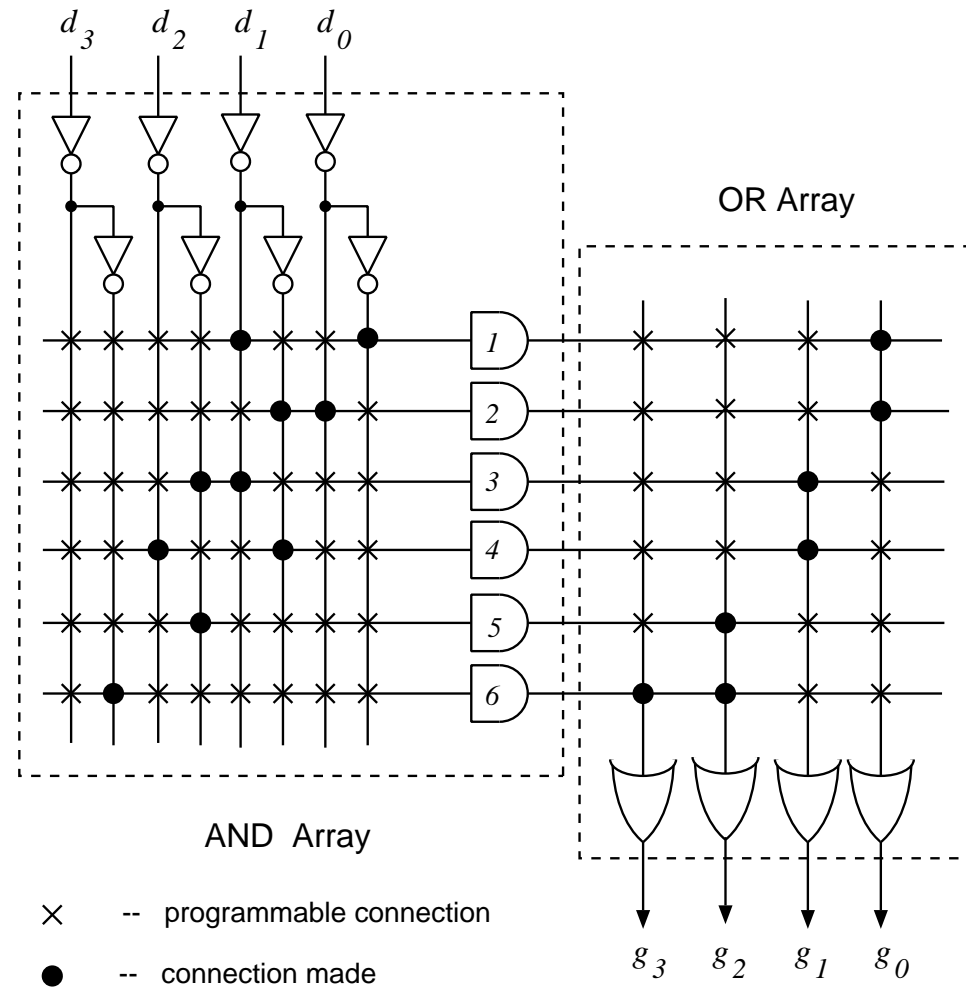

*Note: a PLA chip would have more rows and columns than shown here*

Figure 5.19: PLA IMPLEMENTATION OF BCD-Gray CODE CONVERTER.