

## Chapter 13

### Exercise 13.1

Graphs for cases (a) and (b) are shown in Figure ??.

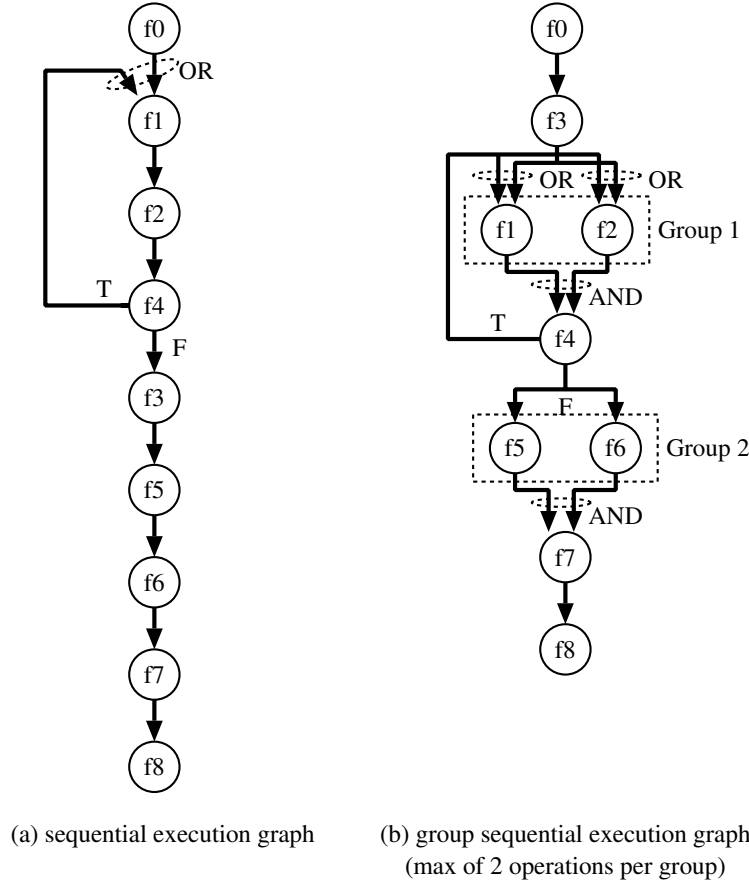


Figure 13.1: Execution Graphs for Exercise 13.1

The execution time for the concurrent graph, considering that the test done by node  $f_4$  results true for  $n$  occurrences (and false after that), is computed as:

$$T_{conc} = 3T + 2nT + 2T = (5 + 2n)T$$

where  $3T$  corresponds to the time to execute the path  $f_0$  to  $f_4$ ,  $f_5$ , and  $f_6$ . Each iteration that results from a True test at  $f_4$  has a duration of  $2T$ , which is also the execution time of the last two tasks to finish the computation ( $f_7$  and  $f_8$ ).

The execution time of the sequential solution shown in Figure ?? (a), for the same loop condition used for the concurrent case is:

$$T_{seq} = 4T + 3nT + 5T = (9 + 3n)T$$

where  $4T$  corresponds to the time to executed the path  $f_0$  to  $f_4$  for the first time. Each iteration takes  $3T$  and the last sequence of tasks takes  $5T$ . **Exercise 13.3**

The algorithm presented in Example 13.7 is based on the recurrence:

$$z_{i+1} = z_i(2 - xz_i)$$

The algorithm stops when  $|z_i x - 1| < 0.5\epsilon$ .

When the inputs for the algorithm are:

$$x = \frac{2}{3} \text{ and } \epsilon = 10^{-5}$$

each variable will have the values shown in the next table:

step $j$	$z_j$	Error
0	1	
1	1.3333333	0.111111
2	1.4814814	0.001234
3	1.4997714	0.000015
4	1.4999999	$2 \times 10^{-8}$

After 4 iterations, the result has an error that is smaller than  $5 \times 10^{-6}$ . **Exercise 13.5**

We want to compute  $z = \sqrt{a}$  using the recurrence equation:

$$z_{i+1} = \frac{1}{2}\left(z_i + \frac{a}{z_i}\right)$$

Since  $z^2 = a$ , the stop condition is defined as  $z^2 - a < \epsilon$ , where  $\epsilon$  is the maximum error in the final result. The execution graph is presented in Figure ??.

The VHDL code for the algorithm is given on Figure ??.

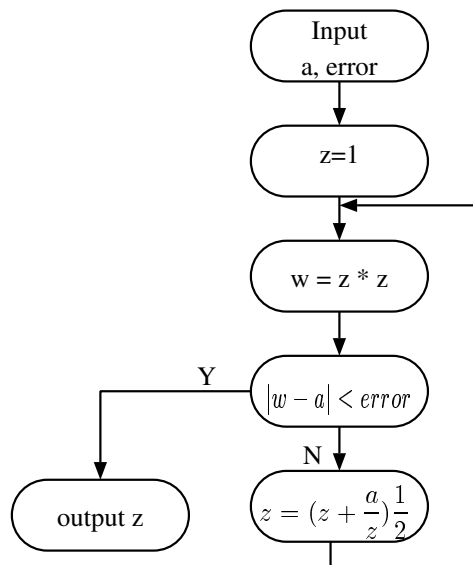


Figure 13.2: Execution graph - Exercise 13.5

**Exercise 13.7**

Execution graph of the algorithm that obtains the maximum value among  $n$  positive integers. All  $n$  integers are stored in a vector  $V$ . The vector is scanned from position 0 to position  $n - 1$ . In this process, the maximal value is obtained. The computation graph is shown in Figure ??.

-- VHDL code for MAX of N integers (in vector V) - Exercise 13.7

```

PACKAGE max_pkg IS
  CONSTANT N: INTEGER := 5;
  TYPE Dataint IS ARRAY (N-1 DOWNT0 0) OF INTEGER;
END max_pkg;
USE work.max_pkg.ALL;
ENTITY max IS
  PORT ( V: IN Dataint := (-10,12,4,-2,34);
        M: OUT INTEGER;
        CLK: IN BIT);
END max;
ARCHITECTURE high_level OF max IS
BEGIN
  PROCESS (CLK)
    VARIABLE maxv: INTEGER;
    VARIABLE i: INTEGER RANGE 0 TO N;
  BEGIN
    IF (CLK'event AND CLK='1') THEN
      maxv := V(0); i:= 1;
      WHILE (i < V'length) LOOP
        IF (maxv < V(i)) THEN maxv := V(i);
        END IF;
        i:=i+1;
      END LOOP;
      M <= maxv;
    END IF;
  END PROCESS;

```

```
-- VHDL code for Square-root computation - Exercise 13.5
LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_arith.all;

ENTITY sqroot IS
PORT (a_in: IN REAL RANGE 0.5 TO 1.0;
      Error: IN REAL RANGE 0.0 TO 0.1;
      z_out: OUT REAL RANGE 0.7 TO 1.0;
      CLK: IN BIT);
END sqroot;

ARCHITECTURE high_level OF sqroot IS
BEGIN
  PROCESS (CLK)
    VARIABLE a,w: REAL RANGE 0.5 TO 1.0;
    VARIABLE z: REAL RANGE 0.7 TO 1.0;
  BEGIN
    IF (CLK'event AND CLK='1') THEN
      z := 1.0;
      a:= a_in;
      w := 1.0;
      WHILE (ABS(w-a) > Error) LOOP
        z:=(a/z+z)/2.0;
        w:=z*z;
      END LOOP;
      z_out <= z;
    END IF;
  END PROCESS;
END high_level;
```

Figure 13.3: VHDL code for SQRT(a) - Exercise 13.5

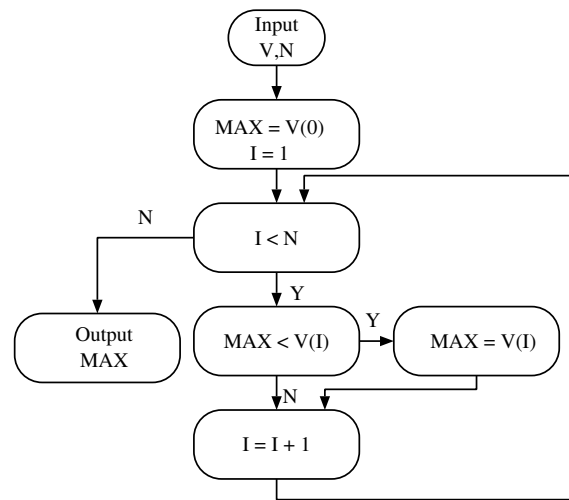


Figure 13.4: Execution graph - Exercise 13.7

END high\_level;

### Exercise 13.9

The networks generated for each case is shown in Figure ??.

### Exercise 13.11

The state diagram for the system operation is shown in Figure ??.

For  $N = 5$  the trace of the computation is shown in the following table:

clock cycle	state	$X$	$I$	$ODD(X)$	$I > 0$
0	0	undef.	undef.	undef.	undef.
1	1	5	3	T	T
2	2	26	2	F	T
3	1	26	2	F	T
4	2	13	1	T	T
5	1	13	1	T	T
6	2	66	0	F	F
7	2	66	0	F	F

Thus the final value is  $X = 66$ .

For  $N = 7$  the trace of the computation is shown in the following table:

clock cycle	state	$X$	$I$	$ODD(X)$	$I > 0$
0	0	undef.	undef.	undef.	undef.
1	1	7	3	T	T
2	2	36	2	F	T
3	1	36	2	F	T
4	2	18	1	F	T
5	1	18	1	F	T
6	2	9	0	T	F
7	2	9	0	T	F

Thus the final value is  $X = 9$ . **Exercise 13.13**

Control: Assume that  $E$  is connected to  $CNT$  input, and  $ldk$  is connected to the  $LOAD$  input of the mod-4 counter. Based on these assumptions and the networks presented in Figure 13.31 of the text we obtain the following expressions:

$$\begin{aligned}
 E &= (ldk)' \\
 ldK &= (A\_7.S\_1) + (c\_out.S\_2) \\
 ldC &= clrB = c\_out.S\_2 \\
 ldA &= K\_1'.K\_0' \\
 S\_1 &= K\_1'.K\_0 \\
 S\_2 &= K\_1.K\_0' \\
 ldB &= K\_1.K\_0
 \end{aligned}$$

The value of  $ldK$  for all possible outputs of the counter is given by the following table. This signal will force the counter to load a zero value.

counter state	ldK
0	0
1	A_7
2	c_out
3	0

Observe that the counter will be forced to zero in state 1 if  $A\_7=1$ , or in state 2 if  $c\_out=1$ . The state diagram for the control part is shown in Figure ??.

The high-level description of the system in VHDL follows. The signals  $A$ ,  $B$ , and  $C$  represent the output of each register.

```

LIBRARY ieee;
USE ieee.std_logic_arith.all;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_unsigned.all;

entity p13_13 is
port (X: in STD_LOGIC_VECTOR (7 downto 0);
      CLK: in STD_LOGIC;
      Y: out STD_LOGIC_VECTOR (7 downto 0));
end p13_13;
architecture arch of p13_13 is
-- process description - Exercise 13.13
SIGNAL A,B,C: STD_LOGIC_VECTOR (7 downto 0):=(OTHERS=>'0');
SIGNAL state: NATURAL RANGE 0 TO 3 := 0;
SIGNAL c_out: STD_LOGIC := '0';
SIGNAL adder_out: STD_LOGIC_VECTOR (8 downto 0);
begin
  adder_out <= ('0'&A) + ('0'&B);
  c_out <= adder_out(8);
  CTR:PROCESS (CLK)
  BEGIN
    IF (CLK'event AND CLK='1') THEN
      CASE state is
        WHEN 0 => A <= X; state <= 1;
        WHEN 1 => IF (A(7)='1')
                    THEN state <= 0;
                    ELSE state <= 2;
                  END IF;
        WHEN 2 => IF (c_out='1')
                    THEN C <= B;
                        B <= "00000000";
                        state <= 0;
                    ELSE state <= 3;
                  END IF;
        WHEN 3 => B <= adder_out(7 downto 0);
                  state <= 0;
      END CASE;
      Y <= C;
    END IF;
  END PROCESS;
end arch;

```

The system accumulates all entries with values less than 128, until the accumulated value cannot absorb another input  $X < 128$  without overflowing. In this case, the internal accumulator value is registered as output and the internal state is reset. The trace of the system operation for a chosen sequence of inputs is shown in Figure ??.

**Exercise 13.15**

The high-level specification of the  $32 \times 32$  serial-parallel multiplier for positive integers is given as follows, for  $n = \log_2 32 = 5$  bits:

Input:  $x, y \in \{0, 1, 2, \dots, 2^n - 1\}$

Output:  $z \in \{0, 1, 2, \dots, 2^{2n} - 2^{n+1} + 1\}$

Function:  $z = x \times y$

A block diagram of the data path for the multiplier is shown in Figure ??. The left multiplexer is used to select among the 4 multiples of  $X$ , that means: 0,  $X$ ,  $2X$ , and  $3X$ . To enable the

generation of the  $3X$  value using the same adder used during the algorithms iterations, some gates were inserted in the path of the selection signals of this multiplexer to force the  $X$  value as an output. Another multiplexer was placed at the other input of the adder to receive the  $2X$  value. After the value  $3X$  is generated, the iterations will be executed.

The VHDL specification of the radix-4 multiplication algorithms is given next:

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_arith.all;
USE ieee.std_logic_unsigned.all;

ENTITY radix4_multiplier IS
  GENERIC (n: NATURAL := 8); -- number of bits in the operands
  PORT (start: IN BIT;
        xin,yin: IN UNSIGNED (n-1 downto 0);
        clk: IN BIT;
        zout: OUT UNSIGNED (2*n-1 downto 0);
        done_out: OUT BIT);
END radix4_multiplier;

ARCHITECTURE behav OF radix4_multiplier IS
  TYPE stateT IS (idle,setup,gen3x,active,done);
  SIGNAL state: stateT := idle;
  SIGNAL x,y: UNSIGNED (n-1 downto 0);
  SIGNAL z: UNSIGNED (2*n-1 downto 0);
  SIGNAL XXX: UNSIGNED (n+1 downto 0);
begin
  PROCESS (clk)
    VARIABLE zero_2n : UNSIGNED (2*n-1 DOWNT0 0); -- constant 0
    VARIABLE scale: UNSIGNED (n-1 DOWNT0 0); -- aligning vector
    VARIABLE add_out: UNSIGNED (n+1 DOWNT0 0); -- adder output
    VARIABLE count: NATURAL RANGE 0 TO n;
  BEGIN
    zero_2n := (OTHERS => '0');
    scale := (OTHERS => '0');
    IF (clk'EVENT AND clk='1') THEN
      CASE state IS
        WHEN idle => done_out <= '0';
          IF (start='1') THEN state <= setup;
            ELSE state <= idle;
              END IF;
        WHEN setup => x <= xin; y <= yin; z <= zero_2n; count:=0;
          state <= gen3x;
        WHEN gen3x => XXX <= ('0'&x(n-1 downto 0)&'0') + ("00"&x);
          state <= active;
        WHEN active => CASE conv_integer(y(count+1 downto count)) IS
          WHEN 0 => add_out:="00"&z(2*n-1 downto n);
          WHEN 1 => add_out:="00"&z(2*n-1 downto n))+x;
          WHEN 2 => add_out:="00"&z(2*n-1 downto n))+('0'&x&'0');
          WHEN 3 => add_out:="00"&z(2*n-1 downto n))+XXX;
          WHEN others => add_out := (others => '0');
        END CASE;
        z <= add_out & z(n-1 downto 2);
        IF (count /= (n-2))
          THEN state <= active;
            count := count + 2;
          ELSE state <= done;
            done_out <= '1';
      END CASE;
    END IF;
  END PROCESS;

```



```

        END IF;
    WHEN done => IF (start='0')
        THEN state <= done;
        ELSE state <= idle;
            done_out <= '0';
        END IF;
    END CASE;
END IF;
END PROCESS;
zout <= z; -- update zout
END behav;

```

A trace of this code execution for two arbitrary inputs is shown in Figure ?? . The values are represented in octal.

For a  $8 \times 8$  case, with the operand values  $x = 135$  and  $y = 115$ , this is the result of the algorithm execution:

clk	state	count	$X$	$Y$	$3X$	$Z$
0	idle	x	xxxxxxxx	xxxxxxxx	xxxxxxxxxx	xxxxxxxxxxxxxxxxxx
1	setup	x	xxxxxxxx	xxxxxxxx	xxxxxxxxxx	xxxxxxxxxxxxxxxxxx
2	gen3x	0	10000111	01110011	xxxxxxxxxx	0000000000000000
3	active	0	10000111	01110011	0110010101	0000000000000000
4	active	2	10000111	00011100	0110010101	0110010101000000
5	active	4	10000111	00000111	0110010101	0001100101010000
6	active	6	10000111	00000001	0110010101	0110101110010100
7	done	6	10000111	00000000	0110010101	0011110010100101

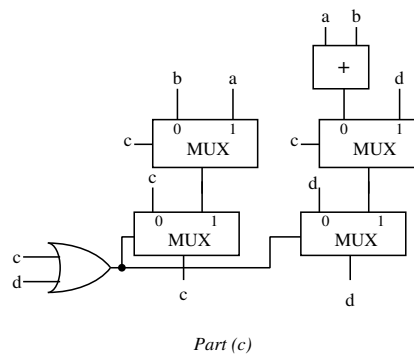
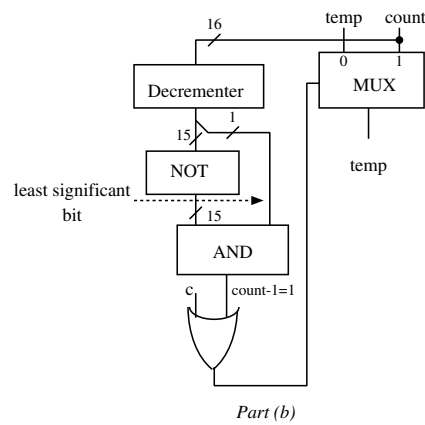
 


Figure 13.5: Networks for Exercise 13.9

 


Figure 13.6: State Diagram for the system in Exercise 13.11


 


Figure 13.7: State diagram for Exercise 13.13

 

Entity:p13\_13 Architecture:arch Date: Mon Nov 22 16:45:36 PST 1999 Row: 1 Page: 1

Figure 13.8: Trace of execution - Exercise 13.13


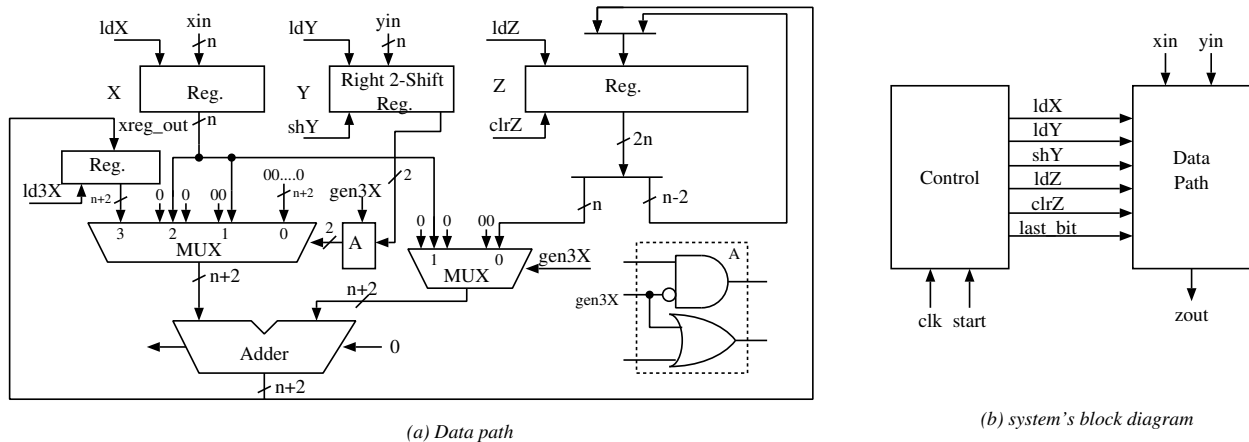


Figure 13.9: Block Diagram for the Data path of the radix-4 multiplier

 

Entity:radix4\_multiplier Architecture:behav Date: Sun Nov 21 20:24:21 PST 1999 Row: 1 Page: 1

Figure 13.10: Trace of execution - 8-bit radix-4 multiplier - Exercise 13.15