

[CS M51A FALL 14] QUIZ 3

Date: 11/21/14

- Please show all your work and write legibly, otherwise no partial credit will be given.
- This should strictly be your own work; any form of collaboration will be penalized.

Name : Teng Xu.

Student ID : _____

Section # : _____

Problem	Points	Score
1	20	
2	40	
Total	60	

Problem 1 (20 points)

Minimize the number of states of the system that corresponds to the table shown below. Show the final minimized table. The input is x and the output is z .

PS	Input	
	$x=0$	$x=1$
A	C,0	F,0
B	J,0	E,0
C	H,0	G,0
D	I,0	G,0
E	E,0	B,1
F	F,0	A,1
G	C,0	G,1
H	E,0	F,0
I	D,0	E,0
J	B,0	G,0
NS,z		

$$P_1 \quad \{A B C D H I J\} \quad \{E F G\}$$

$$P_2 \quad \{A B C D I J\} \quad \{H\} \quad \{E, F\} \quad \{G\}$$

$$P_3 \quad \{A B I\} \quad \{C\} \quad \{D, J\} \quad \{H\} \quad \{E F\} \quad \{G\}$$

$$P_4 \quad \{A\} \quad \{B I\} \quad \{C\} \quad \{D J\} \quad \{H\} \quad \{E F\} \quad \{G\}$$

$$P_5 \quad \{A\} \quad \{B I\} \quad \{C\} \quad \{D J\} \quad \{H\} \quad \{E\} \quad \{F\} \quad \{G\}$$

$$P_6 \quad \{A\} \quad \underbrace{\{B I\}}_B \quad \{C\} \quad \underbrace{\{D J\}}_D \quad \{H\} \quad \{E\} \quad \{F\} \quad \{G\}$$

PS	$x=0$	$x=1$
A	C, 0	F, 0
B	D, 0	E, 0
C	H, 0	G, 0
D	B, 0	G, 0
E	E, 0	B, 1
F	F, 0	A, 1
G	C, 0	G, 1
H	E, 0	F, 0
NS. z.		

Problem 2 (40 points)


1. (20 points) Design a pattern detector that recognizes the pattern 1011, that is:

$$z(t) = \begin{cases} 1 & \text{if } x(t-3, t) = 1011 \\ 0 & \text{otherwise} \end{cases} \quad (1)$$

In addition, your design must meet the following requirements:

- (1) overlap is allowed,
- (2) use no more than 4 states.

Draw the state diagram below.

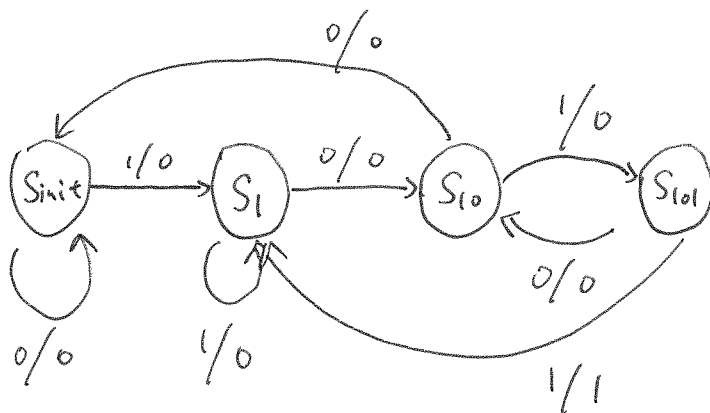

2. (20 points) Suppose you're asked to design a pattern detector that recognizes two patterns, 1011 and 1101.

In addition, your design must meet the following requirements:

- (1) overlap is allowed,
- (2) use no more than 6 states.

Draw the state diagram below.

